



**MAULANA ABUL KALAM AZAD UNIVERSITY OF  
TECHNOLOGY, WEST BENGAL**

**Paper Code :EC(EI)-302**

**ANALOG ELECTRONIC CIRCUIT**

**Time Allotted: 3 Hours**

**Full Marks: 70**

*The figures in the margin indicate full marks.  
Candidates are required to give their answers in their own words  
as far as practicable.*

**Group – A**

**(Multiple Choice Type Questions)**

**I. Choose the correct alternative for any ten of the following:**

**1×10=10**

- (i) The feedback factor  $\beta$  at the frequency of oscillation of a Wien-bridge oscillator is  
(a) 3 (b) 1/3  
(c) 1/29 (d) 3/29
- (ii) The use of crystal in a tunable oscillator  
(a) improves frequency stability (b) increases the gain of the oscillator  
(c) helps to obtain optimum output impedance (d) facilitates generation of wide range of frequencies
- (iii) Which multivibrator is a square wave oscillator?  
(a) monostable (b) astable  
(c) bistable (d) None of the above
- (iv) The function of a bleeder resistor in a power supply is  
(a) the same as that of load resistor  
(b) to ensure a minimum current drain in the circuit  
(c) to increase the output dc voltage  
(d) to increase the output current

**Turn Over**

C50, TezNAE11/04/05/21-3/ECE11-302/2018-19

(vi) If a square wave is fed to a differentiating circuit, the output will be

(a) sine wave

(b) sharp narrow pulses

(c) rectangular wave

(d) triangular wave

### Group - B

(Short Answer Type Questions)

Answer any three of the following.

5×3=15

2. Draw the circuit diagram of a two-stage RC coupled CE transistor amplifier and show how the magnitude and phase angle of its voltage gain vary with frequency.

3. Explain the operation of current mirror circuit. <http://www.makaut.com>

4. Explain the term transistor biasing. What are the factors determining the choice of Q-point? 2+3=5

5. Explain the operation of a series voltage regulator with proper circuit diagram.

6. For the ac equivalent circuit of a Hartley oscillator, determine the frequency of oscillation.

### Group - C

(Long Answer Type Questions)

Answer any three of the following.

15×1=15

7. (a) With necessary h-parameter equivalent circuit of low frequency CE mode transistor amplifier, calculate the following in terms of h-parameters:

(i) input resistance

(ii) power gain

(b) An RC-coupled amplifier employs two identical transistors, each having  $h_{fe} = 100$ ,  $h_{ie} = 2k\Omega$  and  $C_{ob} = 2pF$ . The coupling capacitor has a capacitance  $C = 0.4\mu F$ . The load resistance for each transistor is  $R_L = 8k\Omega$ . Taking the wiring capacitance as  $C_w = 10pF$ , calculate the lower and upper half-power frequencies.

(c) Explain the operation of voltage-to-current converter with

(i) floating load and

(ii) grounded load

(4+3)+4+(2+2)=13

CS/D.Tech/VAEI/2004/SEM-3/EC(EI)-302/2018-19

8. (a) Show that, at the lower half power frequency, the phase angle of an RC-coupled transistor amplifier is  $-225^\circ$ .
- (b) A silicon transistor with  $\beta = 50$ ,  $V_{BE} = 0.6V$ ,  $V_{CC} = 12V$  and  $R_C = 5.6K\Omega$  is used for self-biasing circuit. It is desirable to establish Q-point at  $V_{CE} = 12V$ ,  $I_C = 1.5mA$  and a stability factor  $S \leq 3$ . Find  $R_E = R_1$  and  $R_2$ .  
(The symbols have their usual meanings).
- (c) Explain how temperature compensation can be achieved for analog amplifier using Op-Amp.
- 6+4+5=15

9. (a) Using a suitable diagram, prove that the gain of an RC phase shift oscillator is 29.
- (b) What is the difference between Hartley and Colpitt's oscillator.
- (c) Explain the operation of the following two circuits:
- (i) Differential amplifier
  - (ii) precision rectifier
- 6+3+(3+3)=15

10. (a) What do you mean by multivibrator?
- (b) With detailed circuit diagram, explain the operation of a monostable multivibrator circuit using 555 timer IC.
- (c) Derive the expression of frequency of oscillation for monostable multivibrator circuit using 555 timer IC.
- (d) Determine the positive pulse width, negative pulse width and free-running frequency for an astable multivibrator using 555 timer,  $R_A = 4.7K$ ,  $R_B = 1K$ ,  $C = 1\mu F$ ,  $C_1 = 0.01\mu F$ . What is the duty cycle of output waveform?
- 2+(3+3)+3+4=15

11. Write short notes on any three of the following:

5×3=15

- (i) Phase locked loop
- (ii) Analog amplifier
- (iii) SMPS
- (iv) Crystal oscillator
- (v) Schmitt trigger

http://www.makaut.com

Whatsapp @ 9300930012

Your old paper & get 10/-

पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से