

Name : .....

Roll No. : .....

Invigilator's Signature : .....

**CS/B.Tech (ECE)/SEM-4/EC-401/2010****2010****ANALOG ELECTRONIC CIRCUITS**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.***GROUP - A****( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any ten of the following : 10 × 1 = 10

i) To start the oscillation, the gain of a Wien-bridge oscillator is to be

- |          |          |
|----------|----------|
| a) $> 1$ | b) $> 2$ |
| c) $< 1$ | d) $< 2$ |

ii) The o/p imp. of a series voltage amplifier is

- |                      |                     |
|----------------------|---------------------|
| a) $R_o/(1+\beta A)$ | b) $R_o(1+\beta A)$ |
| c) $\beta R_o/(1+A)$ | d) none of these.   |

iii) Max. phase shift in a two-pole network is

- |                |                |
|----------------|----------------|
| a) $90^\circ$  | b) $150^\circ$ |
| c) $180^\circ$ | d) $270^\circ$ |

4003


[ Turn over



## CS/B.Tech (ECE)/SEM-4/EC-401/2010

- ix) The  $Q$  point in a voltage amplifier is selected in the middle of the active region because
- a) it gives better stability
  - b) the circuit needs a small d.c. voltage
  - c) the biasing circuit then needs less number of resistors
  - d) it gives a distortionless output.
- x) An ideal regulated power supply should have regulation which is
- a) maximum
  - b) 50%
  - c) zero
  - d) 75%.
- xi) To avoid false triggering of the NE 555 timer, the RESET pin ( Pin 4 ) is generally connected to
- a) Pin 8
  - b) Pin 1
  - c) Pin 3
  - d) No connection ( NC ).
- xii) In a logarithmic amplifier, the logarithmic effect of the input is obtained from
- a) non-linear device, like diode or transistor
  - b) negative feed-back
  - c) the Op-Amp itself
  - d) the inverting input terminal.

CS/B.Tech (ECE)/SEM-4/EC-401/2010

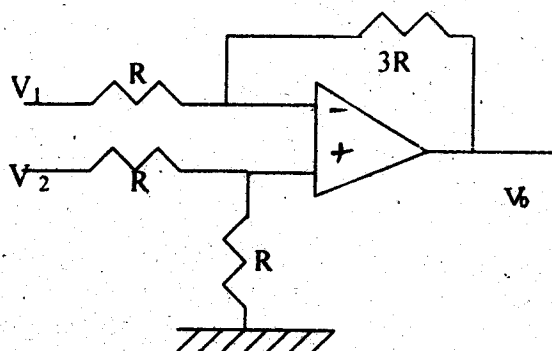xiii) The value of  $V_o$  for the following circuit is given by

- a)  $-3V_1 + 2V_2$                       b)  $-3V_2$   
 c)  $1.5V_2 - 2.55V_1$                   d)  $2V_2 - 3V_1$

xiv) Differential amplifier can be used to amplify

- a) only A.C. signal ( input )  
 b) only D.C. signal ( input )  
 c) both A.C and D.C. signals  
 d) none of these.

xv) Heat sinks are used in power amplifier circuits primarily to increase

- a) the output power  
 b) the voltage gain  
 c) collector dissipation rating of the transistor  
 d) dissipation of energy of free electrons.

CS/B.Tech (ECE)/SEM-4/EC-401/2010

**GROUP - B**

**( Short Answer Type Questions )**

Answer any *three* of the following.  $3 \times 5 = 15$

2. What do you mean by clamping circuit ? Draw its circuit diagram and discuss its operation.
3. What is Common Mode Rejection Ratio ( CMRR ) and Slew rate of Operational Amplifier ?
4. What is the difference between series and shunt regulators ? Draw the circuit diagram of a series regulator.
5. List the three sources of instability of collector current in a transistor. Define three stability factors.

**GROUP - C**

**( Long Answer Type Questions )**

Answer any *three* of the following.  $3 \times 15 = 45$

6. a) Draw the circuit diagram of an emitter follower and explain the nature of feedback in this circuit. What is the feedback topology of the emitter follower ? Derive an expression for the voltage gain of the circuit from the concept of feedback.  $2 + 1 + 3$
- b) Show that negative feedback improves the stability of the gain of an amplifier.  $4$

CS/B.Tech (ECE)/SEM-4/EC-401/2010

- c) The open-loop gain of an amplifier is  $-200$ . A voltage series negative feedback is used with a feedback ratio of  $-0.02$ . The input and the output impedances of the amplifier are  $2\text{ k}\Omega$  and  $40\text{ k}\Omega$ , respectively in the absence of feedback. Determine the closed loop gain, and the input and the output impedances when the feedback circuit is completed.

5

7. a) Draw & explain a circuit which uses a diode to compensate for changes


i) in  $V_{BE}$

ii) in  $I_{CO}$ .

6

- b) Quiescent levels of the network in figure are given as :  $I_{CQ} = 1.1\text{ mA}$  &  $V_{CEQ} = 3.7\text{ V}$ . When  $V_{CC} = 10\text{ V}$ ,  $R_B = 250\text{ k}$  & transistor parameters are  $\beta = 90$  &  $V_{BE} = 0.7\text{ V}$  and at room temperature, find  $R_C$  &  $R_E$ .

5

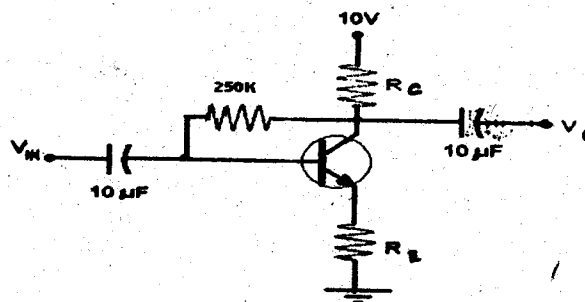

- c) Explain the consequences of Early effect ( base-width modulation ).

4

CS/B.Tech (ECE)/SEM-4/EC-401/2010

8. a) Draw the circuit diagram of a voltage to current converter ( grounded load ) and explain its operation. 5
- b) What is Schmitt trigger ? Explain with circuit diagram. 5
- c) Explain Logarithmic amplifier with circuit diagram. 5
9. a) Draw the a.c. equivalent circuit of dual input balanced output differential amplifier and find out the expression of differential gain (  $A_{id}$  ), input impedance, output impedance. 10
- b) Mention the advantages of active filters over passive filters. 5
10. Write short notes on any *three* of the following :  $3 \times 5 = 15$
- a) Comparator
- b) Astable multivibrator
- c) Schottky diode
- d) Switch Mode Power Supply ( SMPS )
- e) DC load line.
-