



Name :

Roll No. :

Invigilator's Signature :

CS/B.Tech(ECE)/SEM-8/EC-804E/2012

2012

MICROWAVE CIRCUITS & SYSTEMS

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

GROUP – A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *ten* of the following :

10 × 1 = 10

i) Waveguide is a

- | | |
|---------------------|---------------------|
| a) band pass filter | b) high pass filter |
| c) low pass filter | d) all pass filter. |

ii) Magic Tee is

- | | |
|----------------------|-----------------------|
| a) two port network | b) three port network |
| c) four port network | d) one port network. |



iii) In a waveguide the maximum and minimum values of VSWR are

- a) 1 and 0 b) infinity and 0
- c) infinity and 1 d) 10 and 1.

iv) Scattering parameter can be measured with the help of

- a) Spectrum analyzer
- b) Network analyzer
- c) CRO
- d) Bolometer.

v) For matching purpose, waveguide tapers are preferred to transformers because of

- a) low cost b) ease of fabrication
- c) durability d) all of these.

vi) The uplink and downlink frequencies of satellite communication are

- a) 6GHz, 4GHz b) 4GHz, 6GHz
- c) 6GHz, 6GHz d) 3GHz, 4GHz.



vii) Microwave components can be characterized by

- a) h -parameter b) y -parameter
- c) s -parameter d) z -parameter.

viii) For measurement of high values of VSWR, the method to be used is

- a) double the minima method
- b) double the maxima method
- c) single minima method
- d) both (a) and (b).

ix) Cassegrain feed is used with a parabolic reflector to

- a) increase the beam width of the system
- b) increase the gain of the system
- c) allow the feed to be placed at a convenient point
- d) reduce the size of the main reflector.



- x) A micro-strip is analogous to a
- a) co-axial line
 - b) parallel line
 - c) rectangular waveguide
 - d) circular waveguide.
- xi) In a two-hole directional coupler, the distance between two holes in terms of guided wavelength λ_g is
- a) λ_g
 - b) $\lambda_g / 2$
 - c) $\lambda_g / 4$
 - d) $2\lambda_g$.
- xii) If f_c be the cut-off frequency of the waveguide and f be the operating frequency then
- a) $f = f_c$
 - b) $f < f_c$
 - c) $f > f_c$
 - d) $f \ll f_c$.

GROUP - B

(Short Answer Type Questions)

Answer any *three* of the following. $3 \times 5 = 15$

2. Derive the expression for the attenuation of the TE_{10} mode of a rectangular waveguide due to imperfect conducting walls.



3. Show that for a reciprocal network the scattering matrix is symmetric.
4. Prove that for a lossless N-port network, sum of the products of any column or row of s-matrix with its conjugate is unity.
5. Derive the relation between directivity and effective aperture of a Horn antenna.
6. Derive Friis power transmission formula.

GROUP - C

(Long Answer Type Questions)

Answer any *three* of the following. $3 \times 15 = 45$

7. a) Define the term 'coupling factor' and 'directivity' of a directional coupler.
- b) Derive an expression for scattering matrix of a directional coupler.
- c) The input power in a two-hole directional coupler is 1 MW. The coupler has a coupling factor of 15 dB and directivity of 30 dB. Calculate the power in all the ports. $4 + 6 + 5$



8. a) Find an expression for the reflection co-efficient of a truncated periodic structure terminated in a load impedance Z_L .
- b) Derive the design equation in terms of characteristic impedance for band stop and band pass filters using quarter-wave shorted stub resonator.
- c) Derive the expression for image impedance of m -derived filter section by using image parameter method. 4 + 7 + 4
9. a) Determine the expression for fractional bandwidth of Binomial transformer.
- b) Design a three-section binomial transformer to match a 50Ω line to 200Ω load. Also calculate fractional bandwidth of the designed transformer if the maximum tolerable reflection coefficient is 2%. 5 + 10
10. a) Draw a microstrip and transmission line modelling of Wilkinson power divider.
- b) Explain even-mode and odd-mode analysis of Wilkinson power divider. 5 + 10



11. Write short notes on any *three* of the following : 3×5

- a) Industrial applications of microwaves
- b) Tapered lines
- c) Quarter wave transformer
- d) RFMEMS
- e) Chebyshev transformer.

=====