



Name :

Roll No. :

Invigilator's Signature :

CS/B.TECH(EEE/EE-O)/SEM-5/EE-504/2011-12

2011

POWER ELECTRONICS

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

GROUP – A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *ten* of the following :

10 × 1 = 10

- i) For continuous conduction each thyristor pair of a two pulse full converter should conduct for
 - a) π
 - b) $\pi - \alpha$
 - c) α
 - d) $\pi + \alpha$.
- ii) When a power BJT is compared to power MOSFET
 - a) BJT has lower switching losses but higher conduction losses
 - b) BJT has higher switching losses but lower conduction losses
 - c) BJT has lower switching losses and conduction losses
 - d) BJT has higher switching losses and conduction losses.

- 2



vii) A single phase full bridge voltage source inverter has highly inductive load. For a constant source the load current is


- a) square wave b) triangular wave
- c) sine wave d) pulse wave.

viii) Switched mode power supply (SMPS) is preferred over continuous type because SMPS

- a) is suitable for both AC and DC
- b) is suitable for low power circuits
- c) is suitable for high power circuits
- d) provides low power loss.

ix) Bulk power transmission over long HDVC lines are preferred on account of

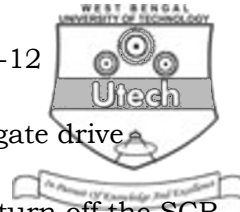- a) low cost HVDC terminals
- b) no harmonic problem
- c) minimum line power losses
- d) simple protection.



- x) When a thyristor gets turned on, the gate drive
- a) should not be removed as it will turn off the SCR
 - b) may or may not be removed
 - c) should be removed
 - d) should be removed to avoid increased losses and higher junction temperature.
- xi) In a 3-phase controlled bridge rectifier, with an increase of overlap angle, the output *dc* voltage
- a) increases
 - b) decreases
 - c) does not change
 - d) depends upon load inductance.
- xii) The advantage of a 180° conduction three phase inverter over a 120° conduction three phase inverter is that
- a) it needs less number of switches
 - b) there is no paralleling of switches
 - c) devices in series are not simultaneous switches
 - d) load terminals are not left open during switching.



GROUP – B

(Short Answer Type Questions)

Answer any *three* of the following

3 × 5 = 15

2. Explain with two transistor analogy of an SCR, how positive feedback action takes place during turn-on of an SCR.
3. Distinguish clearly between voltage communication and current communication in an SCR circuit.
4. What is cyclo-converter ? Explain the operation of a single phase step-up cycloconverter.
5. Explain with the help of circuit diagram, the principle of operation of step-up chopper. Derive the expression of output voltage of such a chopper.
6. a) Define the term 'ripple factor' and 'rectification efficiency' for a converter. 2
 b) Why are freewheeling diode connected in rectifier circuits to cope up with R - L load ? (Give waveforms). 3

GROUP – C

(Long Answer Type Questions)


Answer any *three* of the following.

3 × 15 = 45

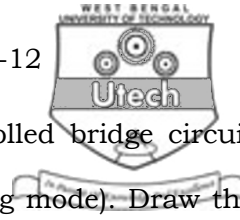7. a) For a 3-phase controlled half-wave rectifier feeding R load, show that the average output voltage is given by

$$V_0 = \frac{3}{2\pi} V_{mp} \left[1 + \cos \left(\alpha + \frac{\pi}{6} \right) \right]; \text{ for } \frac{\pi}{6} < \alpha < \frac{5\pi}{6}$$

where V_{mp} = maximum value of phase voltage, and α = firing angle.



- b) Explain the operation of fully controlled bridge circuit with $R-L$ load (rectifying and inverting mode). Draw the waveform. 7 + 8
8. a) Draw the schematic circuit, the equivalent circuit for at least three modes of conduction, waveforms of gate pulses, phase voltages and line voltage of a three phase inverter with 120° conduction. List the merits and demerits of the circuit compared to 180° conduction.
- b) Explain how the voltage of a single phase inverter is controlled by PWM techniques. 9 + 6
9. a) What is a dc chopper ? Describe the working of type- B chopper. Does it operate as a step-down or step-up chopper ? Explain.
- b) What are the main two control strategies used for obtaining variable voltage from a dc chopper ? Which one of these is preferred over the other and why ?
- c) A step-up chopper operating at 20 kHz has non-conductive time 20 micro-seconds. Calculate output voltage if input voltage is 100 V dc . 6 + 5 + 4



10. a) What is GTO ? Describe its basic structure.
- b) Give the merits and demerits of GTOs as compared to conventional thyristors.
- c) What is UJT ? What is the peak voltage of a UJT ? What is the valley point voltage of a UJT ? What is the intrinsic stand-off ratio of UJT ? What are the advantages of a PUT and a UJT ? 5 + 5 + 5
11. Write short notes on any *three* of the following : 3 × 5
- a) HVDC Transmission
- b) SMPS
- c) Speed control and braking of DC motor using chopper
- d) Resonant Series Converter
- e) Series and Parallel operation of SCRs.

=====