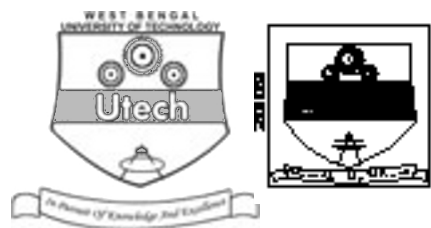


DIGITAL ELECTRONIC CIRCUITS (SEMESTER - 4)

CS/B.TECH (ECE-N)/SEM-4/EC-402/09



1.
Signature of Invigilator

2.
Signature of the Officer-in-Charge

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Roll No. of the
Candidate

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

CS/B.TECH (ECE-N)/SEM-4/EC-402/09
ENGINEERING & MANAGEMENT EXAMINATIONS, JUNE – 2009
DIGITAL ELECTRONIC CIRCUITS (SEMESTER - 4)

Time : 3 Hours]

[Full Marks : 70

INSTRUCTIONS TO THE CANDIDATES :

1. This Booklet is a Question-cum-Answer Booklet. The Booklet consists of **32 pages**. The questions of this concerned subject commence from Page No. 3.
2. a) In **Group – A**, Questions are of Multiple Choice type. You have to write the correct choice in the box provided **against each question**.
b) For **Groups – B & C** you have to answer the questions in the space provided marked 'Answer Sheet'. Questions of **Group – B** are Short answer type. Questions of **Group – C** are Long answer type. Write on both sides of the paper.
3. **Fill in your Roll No. in the box** provided as in your Admit Card before answering the questions.
4. Read the instructions given inside carefully before answering.
5. You should not forget to write the corresponding question numbers while answering.
6. Do not write your name or put any special mark in the booklet that may disclose your identity, which will render you liable to disqualification. Any candidate found copying will be subject to Disciplinary Action under the relevant rules.
7. **Use of Mobile Phone and Programmable Calculator is totally prohibited in the examination hall.**
8. You should return the booklet to the invigilator at the end of the examination and should not take any page of this booklet with you outside the examination hall, **which will lead to disqualification**.
9. Rough work, if necessary is to be done in this booklet only and cross it through.

No additional sheets are to be used and no loose paper will be provided


FOR OFFICE USE / EVALUATION ONLY

Marks Obtained

	Group – A										Group – B					Group – C					Total Marks	Examiner's Signature
Question Number																						
Marks Obtained																						

.....
Head-Examiner/Co-Ordinator/Scrutineer

4463 (08/06)

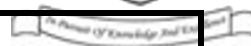


DO NOT WRITE ON THIS PAGE



ENGINEERING & MANAGEMENT EXAMINATIONS, JUNE – 2009

DIGITAL ELECTRONIC CIRCUITS

SEMESTER - 4

 

Time : 3 Hours]

[Full Marks : 70

GROUP – A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *ten* of the following : 10 × 1 = 10

i) Gray code of 1011 (binary) =

a) 0101

b) 1101

c) 1110

d) none of these.

ii) An example of reflected code is

a) BCD

b) ASCII

c) GRAY

d) Hamming code.

iii) If $(212)_x = (23)_{10}$ where x is base (+ ve integer) then the value of x is

a) 2

b) 3

c) 4

d) 5.

iv) Excess-3 code 3d representation of $(19)_{10}$ is

a) 10011

b) 00011001

c) 01001100

d) 11000100.

v) The decimal equivalent of the binary number $(101111.1101)_2$ isa) $(46.8125)_{10}$ b) $(47.8125)_{10}$ c) $(47.8155)_{10}$ d) $(47.8145)_{10}$.

-

-

-

-

-

-

-

-

-


-

$$3 \times 5 = 15$$

6. Implement the full-adder circuit using a 3 to 8 decoder with all active low output and additional logic gates, if required.



6

 GROUP – C**(Long Answer Type Questions)**Answer any *three* of the following questions. $3 \times 15 = 45$

7. a) Draw and explain the circuit of BCD adder using commercially available adder IC 7483 and other necessary logic gates. 7

- b) Simplify the following using Quine McClusky method :

$$F(W, X, Y, Z) = \sum(0, 1, 2, 5, 8, 14) + \sum d(4, 10, 13). \quad 8$$

8. a) What is CLA adder ? Define the terms 'carry propagate' and 'carry generate'. The propagation delay of EX-OR gate is 20ns and that of OR and AND gate is 10ns. Find the propagation delay of a CLA adder. $2 + 3 + 2$

- b) "Excess-3 code is self-complementing." Explain the statement and write its application. 4

- c) Implement the following function using a $3 \times 4 \times 2$ PLA :

$$F_1(A, B, C) = \sum(3, 5, 6, 7)$$

$$F_2(A, B, C) = \sum(0, 2, 4, 7). \quad 4$$

9. a) With the help of necessary circuit diagram, explain the operation of dual slope ADC. 9

- b) A 4-bit binary ladder D/A converter with $R = 10 \text{ k}\Omega$ uses a reference of 5 V. Find the following :

- Ideal scale factor in V/step
- Analog output corresponding to the binary input 0110
- Resolution in %
- Full scale output
- Maximum deviation in volts from the best straight line in order to meet standard linearity. 6



7

10. a) Design a sequential circuit that implement the following state diagram. Use all D-type F/F for the design. 9



dia

- b) Draw and explain the 4 bit bi-directional Shift Register using mode control (M), when M is logic zero then left shift an right shift for M is logic one. 6

11. Write short notes on any *three* of the following : 3 × 5

- a) D.C. noise margin and A.C. noise margin
- b) Hold time and set-up time related to FF
- c) Parity generator and checker
- d) Tri-state gates in TTL family
- e) EPROM.

END