

Name :

Roll No. :

Invigilator's Signature :

CS/B.Tech(EE/NEW)/SEM-6/EE-605C/2013

2013

VLSI AND MICROELECTRONICS

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable*

GROUP – A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *ten* of the following :

10 × 1 = 10

- i) VLSI stands for
 - a) Very Large Scale Integration
 - b) Very Low Scale Integration
 - c) all of these
 - d) none of these.
- ii) In LSI maximum number of transistors per chip is
 - a) 10000
 - b) 1000
 - c) 2000
 - d) none of these.

CS/B.Tech(EE/NEW)/SEM-6/EE-605C/2013

- iii) ASIC stands for
 - a) Application Surface Integral Circuit
 - b) Application Specific Integral Chip
 - c) Application Specific Integrated Circuit
 - d) All of these.
- iv) FPGA is used for
 - a) design verification b) front end design
 - c) design configuration d) none of these.
- v) PLA stands for
 - a) Programmable Logic Array
 - b) Portable Logic Array
 - c) Programmable Linea Array
 - d) all of these
- vi) E-mos is normally
 - a) On device b) Off device
 - c) Can't be said d) all false.
- vii) CMOS inverter requires minimum
 - a) 2 transistors b) 4 transistors
 - c) all of these d) none of these.
- viii) VHDL is a
 - a) language b) hardware
 - c) PLA d) none of these.

CS/B.Tech(EE/NEW)/SEM-6/EE-605C/2013

- ix) 2-input OR gate requires
- a) 2 transistors b) 5 trnsistors
 - c) 1 ransistor d) 4 transistors.
- x) D-MOSFET means
- a) Depletion MOSFET b) Direct MOSFET
 - c) all of these d) none o these.
- xi) Charge inversion can be observed in
- a) BJT b) E MOS
 - c) Diode d) all of these.

GROUP – B

(Short Answer Type Questions)

Answer any *three* of the following. $3 \times 5 = 15$

2. Draw NOR and NAND gates using CMOS. $2 \times 2 \frac{1}{2}$
3. Write the advantages of VLSI technology.
4. Sketch $Y = \overline{(A + B + C)}.D$
5. Sketch a stick diagram of 3-input NAND gate.

CS/B.Tech(EE/NEW)/SEM-6/EE-605C/2013

GROUP – C**(Long Answer Type Questions)**Answer any *three* of the following. $3 \times 15 = 45$

6. a) Draw an inverter circuit using CMOS.
 b) Design a circuit using PAL to implement the following function :

$$F_1 = xyz + x'y'$$

$$F_2 = w'F_1' + wxy'z$$

- c) Write a short note on FPGA. $3 + 7 + 5$
7. a) Write a short note on y -chart.
 b) Sketch a stick diagram of $Y = \overline{(A + B + C)}.D$.
 c) Describe working principle of Enhancement MOSFET.

 $5 + 5 + 5$

8. a) Write a VHDL programme for Full Adder.
 b) Write a VHDL program for X-OR gate.
 c) Write a short note on photo-lithography. $5 + 5 + 5$

9. Write short notes on any *three* of the following : 3×5

- a) PLA
 b) Ion-implantation
 c) ASIC
 d) Depletion MOSFET.

=====