



# ENGINEERING & MANAGEMENT EXAMINATIONS, DECEMBER - 2008

## DIGITAL INTEGRATED CIRCUITS

### SEMESTER - 3

Time : 3 Hours ]

[ Full Marks : 70

#### GROUP - A

#### ( Multiple Choice Type Questions )

1. Choose the correct alternatives for any ten of the following :

10 × 1 = 10

i) Gray code of 1011 ( binary ) =

a) 0101

b) 1101

c) 1110

d) None of these.

ii) An example of reflected code is

a) BCD

b) ASCII

c) GRAY

d) Hamming code.

iii) The minimum number of NAND gates required to design one X-OR gate is

a) 3

b) 4

c) 5

d) 6.

iv) If  $(212)_x = (23)_{10}$ , where  $x$  is base ( +ve integer ), then the value of  $x$  is

a) 2

b) 3

c) 4

d) 5.

v) Full form of FPGA is

a) Full Programmable Gated Array

b) Field Programmable Gated Array

c) Full Peripheral Gated Array

d) Field Peripheral Gated Array.

11/11/2018

- 

- 

- 

- ut.com

ut.com

- ut.com

ut.com

- ut.com

ut.com

- ut.com



xiii) For a  $n$ -bit parallel-in-parallel-out shift register we need

- a) 1    b)  $n$   
c)  $2n + 1$                                 d)  $n + 1$

**clock pulse/pulses.**

xiv) The number of flip-flops required to design a MOD - 18 counter is

- a) 3                      b) 4  
c) 5                      d) 6.

xv) A ring counter consisting of 5 flip-flops will have

- a) 5 states                      b) 10 states
- c) 32 states                     d)  $(2^5 - 1)$  states.

**GROUP - B**

**( Short Answer Type Questions )**

**Answer any three of the following.**

$$3 \times 5 = 15$$

**2. Given the Boolean function  $F = xy + \overline{xy} + \overline{y}z$  :**

- Implement it with only OR and NOT gates.
- Implement it with only AND and NOT gates.

 $2 \times 2 \frac{1}{2}$ 

3. a) If the solution of the equation  $x^2 + 11x + 22 = 0$  are  $x = 3, 6$ , then determine base of  $x$ .

- b) What do you mean by arithmetic overflow ? 4 + 1

4 + 1

**4. Design a 2-input NAND gate using CMOS transistors.**

5

**5. Implement the following function using a Multiplexer :**

$$F(a, b, c) = \sum m(1, 3, 5, 6).$$

5

**6. Use a K-MAP to simplify the following Boolean expression**


$$F(a, b, c, d) = \sum m(0, 2, 6, 8, 12, 13, 15) + d(3, 9, 10)$$

**d = don't care ( i.e. either 1, 0 ).**

5

**GROUP - C****( Long Answer Type Questions )**Answer any *three* questions. $3 \times 15 = 45$ 

 7. a) What do you mean by prime-implicant and essential prime-implicant ?  $1 \frac{1}{2} + 1 \frac{1}{2}$
- b) The four-variable function  $f$  is given in terms of minterm as  
 $f(A, B, C, D) = \sum m(2, 3, 8, 10, 11, 12, 14, 15)$ .  
 Using Quine McCluskey method, minimize the function in the SOP form. Also give the realization using only two-input NAND gate.  $10 + 2$
8. A new clocked X-Y flip-flop is defined with two inputs, X and Y in addition to the clock input. The flip-flop function as flows :  
 If  $XY = 00$  the FF changes state with each clock pulse  
 If  $XY = 01$  the FF states Q become 1 with the next clock pulse  
 If  $XY = 10$  the FF states Q become 0 with the next clock pulse  
 If  $XY = 11$  no changes of state occur with the clock pulse
- a) Write the truth table for the XY flip-flop. 3
- b) Write the excitation table for the XY flip-flop. 3
- c) It is desired to convert a J-K flip-flop into the X-Y flip-flop by adding some extra gates, if necessary. Draw a circuit to show how you will implement the XY flip-flop using a J-K flip-flop. 9
9. a) What are the differences between a latch and a flip-flop ? 2
- b) What is Johnson counter ? State the advantages and disadvantages of Johnson counter. 1 + 2
- c) Design a sequential circuit that implement the following state diagram. Use all D flip-flops for the design. 10





10. a) Design a compactor circuit to output logic-1 when a 4-bit binary number  $X$  satisfies the condition  $4 \leq X \leq 12$ . 8
- b) Design a binary multiplier circuit to multiply two 2-bit numbers. Use a suitable decoder and logic gates. Assume that all the outputs of the decoder are active low. 7
11. a) Implement a 16-to-1 MUX using two 8-to-1 MUXs. 6
- b) Design a Gray code to binary converter using suitable logic gates. 7
- c) How can a decoder be used as a DEMUX ? 2
12. Write short notes on any *three* of the following : 3 × 5
- a) PLD
- b) Even Parity checker and generator
- c) EEROM
- d) Successive Approximation register
- e) Hamming code.

---

END