

Name :

Roll No. :

Invigilator's Signature :

CS/B.Tech (NEW)/SEM-1/ES-101/2011-12

2011

**BASIC ELECTRICAL &
ELECTRONICS ENGINEERING – I**

Time Allotted : 3 Hours

Full Marks : 70

**THIS QUESTION BOOKLET CONSISTS OF 2 PARTS —
PART I & PART II.
TO ANSWER THE QUESTIONS USE SEPARATE ANSWER
BOOKS FOR SEPARATE PARTS.
DO NOT ANSWER BOTH THE PARTS IN THE SAME
ANSWER-BOOK.**

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

PART – I

(Marks : 35)

GROUP – A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *five* of the following :

5 × 1 = 5

- i) The conductance G of a series R - L circuit having a resistance R and inductive reactance X_L is given by

a) $G = \frac{1}{R}$

b) $G = \frac{R}{X_L}$

c) $G = \frac{R}{R^2 + X_L^2}$

d) $G = \frac{R^2}{R^2 + X_L^2}$

- ## GROUP – B

Answer any *two* of the following.

$$2 \times 5 = 10$$

-

2



3. Derive a mathematical expression for r.m.s. value of a sinusoidal voltage $v = V_m \sin \omega t$.
4. Two coils have self inductances L_1 and L_2 and mutual inductance between them is M . Derive a mathematical expression for co-efficient of coupling k for these coils.
5. Determine the value of R in Figure 2 such that 4Ω resistor consumes maximum power.

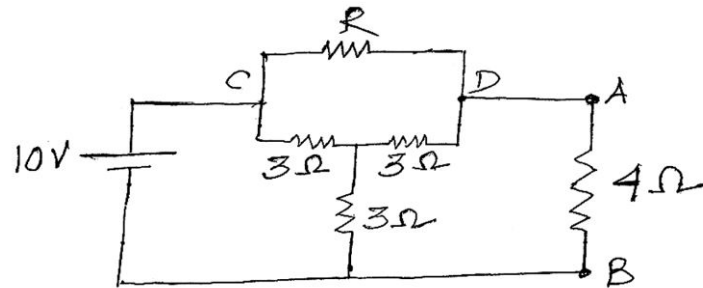


Figure 2

GROUP – C

(Long Answer Type Questions)

Answer any *two* of the following. 2 × 10 = 20

6. a) What is meant by the term “resonance” in a series R.L.C. circuit ? 3
- b) A 20Ω resistor, a choke coil having some inductance and some resistance and a capacitor are connected in series across a 25 V variable frequency source. When frequency is 400 Hz, the current is maximum and its value is 0.5 A and the potential difference across the capacitor is 150 V. Calculate the resistance and the inductance of the choke coil and the capacitance of the capacitor. 7



7. a) A flux of 0.0006 Wb is required in the air-gap of an iron ring of cross-section 5.0 cm^2 and mean length 2.7 m with an air-gap of 4.5 mm . Determine the ampere turns required. Six H values and corresponding B values are noted from the magnetisation curve of iron and given below. 6

$H \text{ (AT/m)}$	200	400	500	600	800	1000
$B \text{ (Wb/m}^2 \text{)}$	0.4	0.8	1.0	1.09	1.17	1.19

- b) A circuit receives 50 A current at a power factor of 0.8 lag from a 250 V , 50 Hz , 1-ph A.C. supply. Calculate the capacitance of the capacitor which is required to be connected across the circuit to make the power factor unity. 4
8. a) State and explain Thevenins theorem. 3
- b) Find the Thevenin equivalent of the circuit of Figure 3 as shown at terminal XY. 7

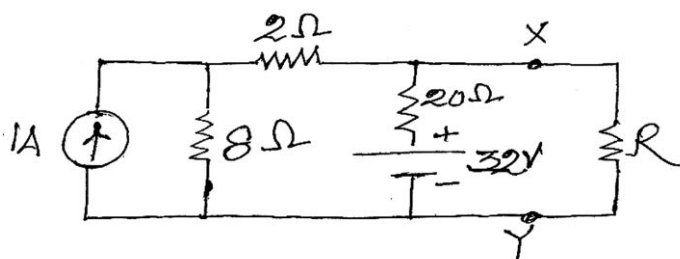


Figure 3


9. a) Derive a mathematical expression for the average real power delivered by a single phase a.c. source with an *e.m.f.* of $e = \sqrt{2} E_m \sin \omega t$ when the source current is $i = \sqrt{2} I_m \sin (\omega t - \theta)$. 6
- b) Define power factor of an a.c. circuit. State the major disadvantages of poor power factor. 4

PART – II

GROUP – A

1. Choose the correct alternatives for any *five* of the following :

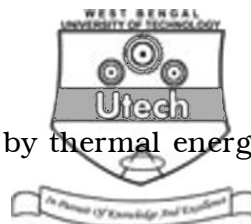- i) Fermi level of an n -type semiconductor lies
 - a) near the conduction band edge
 - b) near the valence band edge
 - c) at the middle of the band gap
 - d) none of these.
- ii) For an $n p n$ transistor, I_{CBO} approximately doubles for temperature rise of every
 - a) 5°C
 - b) 7°C
 - c) 10°C
 - d) none of these.
- iii) If α of a BJT is 0.98, then the value of β is
 - a) 0.99
 - b) 99
 - c) 50
 - d) 49.
- iv) The power rating of a BJT is determined by which of the following ?
 - a) Collector base junction area
 - b) Base width
 - c) Heat sink
 - d) Emitter base junction area.



- v) It is easy to break the covalent bond by thermal energy in case of
- | | |
|------------|--------------|
| a) Carbon | b) Germanium |
| c) Arsenic | d) Silicon. |
- vi) The temperature coefficient of Zener breakdown voltage is
- | |
|---------------------------------|
| a) positive |
| b) negative |
| c) zero |
| d) either positive or negative. |

GROUP – B

(Short Answer Type Questions)

Answer any *two* of the following. $2 \times 5 = 10$

2. What do you mean by an intrinsic semiconductor ? Will it behave as an insulator at any temperature ? Explain. $2 + 3$
3. Explain the mechanism of Zener breakdown in $p-n$ junction and write how it differs from avalanche breakdown. $3 + 2$
4. What is meant by $d.c.$ operating point or Q point in the context of transistor characteristics ? What is load line ? Why is transistor biasing necessary ? $2 + 1 + 2$
5. Explain the principle of operation of a varactor diode. Mention one application. $4 + 1$



GROUP – C

(Long Answer Type Questions)

Answer any *two* of the following.

2 × 10 = 20

6. Consider an intrinsic silicon bar of cross-section 5 cm^2 and length 0.5 cm at room temperature 300K . An average field of 20 V/cm is applied across the ends of the silicon bar.

a) Calculate —

- i) electron and hole component of current density
- ii) total current in the bar
- iii) resistivity of the bar. 6

- b) If now donor impurity to the extent of 1 part in 10^8 atoms of Si is added, find the density of minority carriers and the resistivity. 4

Given :

Electron mobility = $1400 \text{ cm}^2/\text{V-s}$


Hole mobility = $450 \text{ cm}^2/\text{V-s}$

Intrinsic carrier concentration of Si

At room temperature (300K) = $1.5 \times 10^{10} / \text{cm}^3$

No. of Si atoms/ m^3 = 4.99×10^{28} .

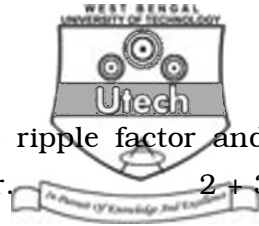7. a) Explain drift and diffusion of charge carrier in semi-conductors. Derive the expression for electric current due to drift and diffusion. 4 + 3
- b) With the help of energy-band diagram, differentiate among conductor, semi-conductor and insulator. 3




8. a) What is ripple factor ? Evaluate the ripple factor and efficiency of a full-wave bridge rectifier. 2 + 3

- b) A silicon diode with internal resistance $R_F = 25 \Omega$ is used for half-wave rectification. The input a.c. voltage is $V_i = 20 \sin \omega t$ and the load resistance is 500Ω .

Find,

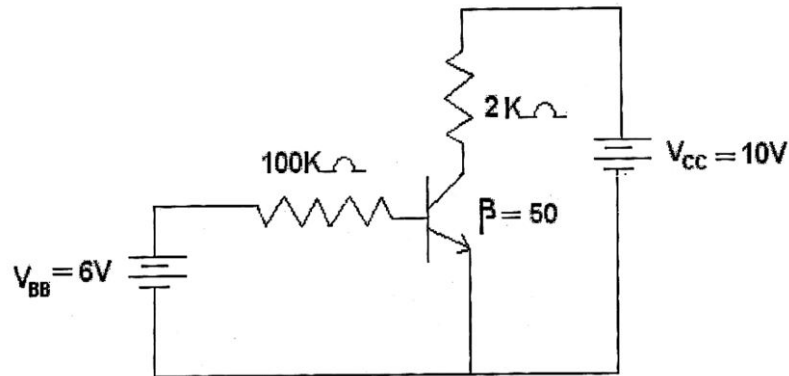- i) d.c. output voltage
 - ii) a.c. input power and
 - iii) efficiency of the rectifier. 2 + 2 + 1
9. a) Draw the circuit diagram for self-biased configuration considering an n-p-n transistor in CE configuration. Derive the expression for its stability factors. 3 + 2
- b) Calculate V_{CE} and I_C in the circuit below. Assume $V_{BE} = 0.7 \text{ V}$. 4



- c) What is the voltage gain of a transmitter circuit in CC configuration ? 1

=====