



Name : .....

Roll No. : .....

Invigilator's Signature : .....

**CS / B.TECH (EE-NEW) / SEM-4 / EC (EE)-402/ 2011**

**2011**

**DIGITAL ELECTRONICS AND INTEGRATED CIRCUITS**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words  
as far as practicable.*

**GROUP – A**

**( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any *ten* of the following :

$$10 \times 1 = 10$$

- i) The carry look ahead adder is frequently used for addition because, it
- |                     |                      |
|---------------------|----------------------|
| a) is faster        | b) has more accuracy |
| c) uses fewer gates | d) costs less.       |
- ii) Which gates are used as an array of a programmes in ROM ?
- |                     |                   |
|---------------------|-------------------|
| a) AND gates        | b) OR gates       |
| c) Both (a) and (b) | d) None of these. |



iii)  $A + A'B + A'B'C + A'B'C'D + \dots =$

a)  $A + B + C + \dots$

b)  $A' + B' + C' + \dots$

c) 1

d) 0.

iv) The decimal number -15 is represented in 8-bit signed 2's complement notation as

a) 11010001

b) 11100111

c) 11110001

d) 10001111.

v) Which of the following IC logic families has extremely low power dissipation ?

a) TTL

b) Schottky TTL

c) Low power Schottky TTL

d) CMOS.

vi) Two  $D$  flip-flops are connected as a synchronous counter that goes through the following  $Q_B Q_A$  sequence 00, 11, 01, 10, 00, .... . The connections to the inputs  $D_A$  and  $D_B$  are

a)  $D_A = Q_B, D_B = Q_A$

b)  $D_A = Q_A', D_B = Q_B'$

c)  $D_A = Q_A Q_B' + Q_A' Q_B, D_B = Q_A$

d)  $D_A = Q_A Q_B + Q_A' Q_B', D_B = Q_B'.$

- [ Turn over



xiii) A flip-flop is called a latch when it is

- a) edge trigger                      b) level trigger
- c) both (a) and (b)              d) without any trigger.

xiv) To add two  $m$ -bit numbers, the number of required half added is


- a)  $2m - 1$                           b)  $2m$
- c)  $2^m$                                   d)  $2m + 1$ .

### GROUP – B

#### ( Short Answer Type Questions )


Answer any *three* of the following.               $3 \times 5 = 15$

 2. Convert the following circuit into a multi-level circuit using all NAND gates. Assume that the three & complement of all variables are available to the circuit.



3. Design a full-subtractor using only NOR gates.
4. Explain the circuit operation of a Master-Slave JK flip-flop using all NAND gates. Write down the corresponding truth table.

3 + 2

 

5. Design a 4 to 16 decoder by using two 3 to 8 decoders. Write down the corresponding truth table. 4 + 1
6. Prove that the NAND gate is called a universal gate. Implement an EX-OR (2-input) logic using NAND gates. 4 + 1
7. Design a circuit using logic gates which will generate the odd parity of 3-bit binary number. What is the function of a parity checker ? 3 + 2

### GROUP – C

#### ( Long Answer Type Questions )

Answer any *three* of the following.  $3 \times 15 = 45$


8. a) What do you mean by Prime implicant ? Simplify the following Boolean expression using K-map :

$$F(A, B, C, D) = \sum m(0, 2, 3, 6, 8, 11, 12, 14) + d(1, 4, 9, 10)$$

- b) Design a full adder using two half adders and necessary gate.
- c) Draw a network using only NAND gate to generate the function  $Y = (\bar{A} + BC)$ . ( 2 + 5 ) + 4 + 4



 9. a) What are the advantages and disadvantages of totem pole ?
- b) What are the output voltages caused by logic 1 in each bit position in an 8-bit ladder if the input level for 0 level is 0 volt and for level 1 is 10 volt ?
- c) Compare the maximum conversion period of an 8-bit Digital ramp ADC and 8-bit successive approximation ADC, if both utilize 1 MHz clock frequency.
- d) With proper circuit diagram, explain the operation of NMOS NAND gate. 3 + 3 + 4 + 5
10. a) Perform the conversion of D flip-flop to JK flip-flop.
- b) What is presettable counter ? Design a MOD-5 counter that counts its natural count sequence from 000 to 100.
- c) Distinguish between a ripple counter and a synchronous counter. 5 + 8 + 2
11. a) What are the differences between the Decoder and Demultiplexer ?
- b) Form a multiplexer tree to give  $4 \times 1$  MUX from two  $2 \times 1$  MUX.



- c) Show how a 16 input MUX is used to generate the function  $F = (A, B, C, D) = \overline{A} \overline{B} \overline{C} D + BCD + A \overline{B} \overline{C} + ABCD$ .

5 + 5 + 5

12. a) What are RAM and ROM ? What is the basic difference between EPROM and EEROM ?
- b) What is the major difference between the two classes of finite state machines and proper state diagram ?
- c) What is Schmitt Trigger ? ( 2 + 3 ) + ( 4 + 4 ) + 2

=====