

**ENGINEERING & MANAGEMENT EXAMINATIONS, JUNE - 2008****POWER ELECTRONICS****SEMESTER - 6**

Time : 3 Hours]

[Full Marks : 70

GROUP - A**(Multiple Choice Type Questions)**1. Choose the correct alternatives for any *ten* of the following : 10 × 1 = 10

i) A single phase full converter supplying a very high inductive load can operate in

- | | |
|----------------|----------------------------------|
| a) 4 quadrants | b) 3 quadrants |
| c) 2 quadrants | d) 1 quadrant, of $V - I$ plane. |
-

ii) A current controlled device is

- | | |
|--------------|--------------|
| a) MOSFET | b) BJT |
| c) Capacitor | d) Inductor. |
-

iii) The main reason for connecting a pulse transformer at the output stage of an SCR firing circuit is to

- | |
|---|
| a) amplify power of the triggering pulse |
| b) provide electric isolation |
| c) reduce the turn-on time of the SCR |
| d) avoid spurious triggering of SCR due to noise. |
-

iv) In a 3-phase full converter, the output voltage pulsates at a frequency equal to

- | | |
|--------------------------|-----------|
| a) supply frequency, f | b) $2f$ |
| c) $3f$ | d) $6f$. |
-



- v) Each diode of a 3-phase half-wave diode rectifier conducts for

 - 60°
 - 120°
 - 180°
 - 90° .

vi) The transformer used in a switched mode power supply is

 - Air core
 - Iron core
 - Ferrite core
 - All of these.

vii) If the gate current of an SCR is increased, the forward breakdown voltage V_{FBR} will .

 - increase
 - decrease
 - not be effected
 - infinite.

viii) In a single phase full converter, if α & β are firing & extinction angles respectively, then the load current as

 - discontinuous if $(\beta - \alpha) < \pi$
 - discontinuous if $(\beta - \alpha) > \pi$
 - discontinuous if $(\beta - \alpha) = \pi$
 - continuous if $(\beta - \alpha) < \pi$.

ix) Which of the following devices exhibits second breakdown phenomenon ?

 - SCR
 - Power MOSFET
 - Power BJT
 - GTO.

x) SCR can be triggered by .

 - positive feedback action
 - negative feedback action
 - both positive & negative feedback action
 - none of these.



- xi) Resonant converter controls the output power by
- varying the switching frequency around resonating frequency
 - varying the on-time of the switch
 - controlling the power loss in the switch
 - none of these.

- xii) Reverse recovery current in a diode depends upon
- forward field current
 - storage current
 - temperature
 - PIV.

GROUP - B

(Short Answer Type Questions)

Answer any *three* of the following.

3 × 5 = 15

- Derive an equation for anode current of an SCR considering two-transistor analogy of SCR.
- In a single phase semi-converter, connected to 100 V, 50 Hz supply, find the average & r.m.s values of the output voltage if the firing angle is 60°.
- What is a current source inverter ? Mention its merits & demerits compared to voltage source inverter.
- Explain briefly why maximum triggering angle available from a resistance triggering circuit is 90°.
- Explain various triggering methods of an SCR.

**GROUP - C****(Long Answer Type Questions)**Answer any *three* questions. $3 \times 15 = 45$

7. a) Why is a three phase bridge controlled rectifier called a six pulse converter ? Explain briefly with circuit diagram and output voltage waveform.
- b) A three phase six pulse converter is operated from a 3-phase star connected 400 V, 50 Hz supply and with R load ($R = 10 \text{ ohm}$).

It is required to obtain an average output voltage equal to 50% of the maximum possible output voltage of the rectifier.

Find out at this condition

- i) the firing angle
 - ii) the average output voltage
 - iii) the average current of each thyristor
 - iv) PIV requirement of each thyristor.
- c) Explain how the above mentioned converter can act as rectifier and inverter.

 $6 + 6 + 3$

8. a) Explain with a neat circuit diagram the operation of a boost converter.
- b) A boost converter has a supply voltage of 250 volts, while the output voltage is 500 V. If the period of converter is $100 \mu\text{sec}$, determine the conduction of the switch.

If the period is reduced to one third for constant frequency operation, find the output voltage.

- c) With a neat circuit diagram explain the operation of CuK converter.
- d) State the advantages of CuK converter over Buck-Boost Converter.

 $4 + 4 + 4 + 3$



9. a) How is the working of a full bridge single phase inverter different from that of half bridge circuit. Explain with the help of diagrams.
- b) Draw and explain the operation of a fly-back converter. How does it differ from forward converter ?
- c) Explain how zero voltage switching can be achieved in a series resonant converter. 5 + 6 + 4
10. a) Explain the operation of IGBT. State the advantages of IGBT.
- b) How are di/dt & dv/dt protections achieved in SCR ?
- c) Define turn-on & turn-off time of an SCR with the help of dynamic characteristics. 6 + 5 + 4
11. Write notes on any *three* of the following : 3 × 5
- a) Electronic ballast
- b) Induction heating
- c) UPS
- d) Active front end converter.
- e) Need for power electronics converter.

END