

Name :

Roll No. :

Invigilator's Signature :

CS/B.TECH(EE)(EEE),(ICE)(N)/SEM-3/EC(EE)-301/2012-13

2012

ANALOG ELECTRONIC CIRCUITS

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

GROUP – A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *ten* of the following :
 $10 \times 1 = 10$

- i) An ideal regulated power supply should have regulation which is
 - a) maximum
 - b) 50%
 - c) zero
 - d) 75%.
- ii) Thermal Runaway in a transistor is due to
 - a) heating of the transistor
 - b) changes in β which increases with temperature
 - c) increase in reverse collector saturation current due to rise in temperature
 - d) none of these.



- iii) In amplifier blocking capacitors are used
- to increase the bandwidth
 - to match the impedance
 - to increase the gain
 - to avoid dc mixing with input or output.
- iv) The condition of oscillation is
- $A\beta = 1$
 - feedback must be regenerative
 - phase angle must be zero or integral multiple of 360°
 - all of these.
- v) The expression of closed loop gain (A_f) for negative feedback amplifier is
- $\frac{A}{1 + A\beta}$
 - $\frac{A}{1 - A\beta}$
 - $\frac{1}{1 + A\beta}$
 - $\frac{1}{1 - A\beta}$
- vi) A Schmitt trigger uses
- Negative feedback
 - Positive feedback
 - Pull up resistor
 - Compensating capacitor.
- vii) Differential amplifier can be used to amplify
- only a.c. signal
 - only d.c. signal
 - both a.c. and d.c. signal
 - none of these.



viii) Most efficient power amplifier is

- a) class A
- b) class B
- c) class C
- d) class AB.

ix) The maximum theoretical efficiency of a push-pull class B power amplifier is

- a) 50%
- b) 78.5%
- c) 60%
- d) 25%.

x) Which one of the following feedback topologies offer high input impedance ?

- a) Voltage series
- b) Voltage shunt
- c) Current series
- d) Current shunt.

xi) In the astable multivibrator the capacitor charges upto

- a) $\frac{1}{3} V_{cc}$
- b) $\frac{2}{3} V_{cc}$
- c) V_{cc}
- d) none of these.

xii) In VCO, the frequency is dependent on the value of

- a) Resistance
- b) Capacitance
- c) Voltage
- d) None of these.



GROUP – B

(Short Answer Type Questions)

Answer any *three* of the following.

3 × 5 = 15

2. a) Explain the need of biasing of a transistor.

b) Draw any one type of transistor biasing arrangement and determine its stability factor. 2 + 3
3. Draw the h -parameter equivalent circuit of low frequency CE mode transistor amplifier and hence calculate the current gain in terms of h -parameters. 2 + 3
4. What is VCO ? What are the basic differences between VCO and fixed frequency oscillator ? 2 + 3
5. What is cross-over distortion ? How does cross-over distortion arise in class B power amplifier ? Suggest one method to avoid cross-over distortion. 1 + 3 + 1
6. Draw the electrical equivalent circuit of a vibrating crystal and state the significance of each component. What are f_s and f_p ? 3 + 2




GROUP - C

(Long Answer Type Questions)

Answer any *three* of the following. $3 \times 15 = 45$

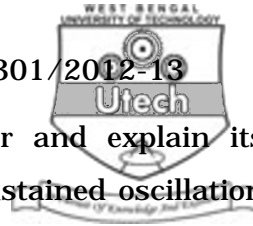7. a) Describe the working principle of π -filter with diagram.
 b) Draw the circuit of a shunt regulator and explain its operation.
 c) What are the merits of switched mode power supply (SMPS) over regulated power supply ? With the help of a neat circuit diagram briefly explain the operation of switched mode power supply. $4 + 5 + (1 + 5)$
8. a) Why voltage divider bias circuit is known as self bias circuit ? A silicon transistor with $\beta = 50$, $V_{BE} = 0.6 \text{ V}$, $V_{CC} = 22.5 \text{ V}$ and $R_C = 5.6 \text{ K}\Omega$ is used for self biasing circuit. It is desired to establish a Q point at $V_{CE} = 12\text{V}$, $I_C = 1.5 \text{ mA}$ and a stability factor $S \leq 3$. Find $R_E = R_1$ and R_2
 (The symbols have their usual meanings).
 b) Find the upper cut-off frequency of a two stage common-emitter RC coupled amplifier. A two stage common-emitter RC coupled amplifier uses transistor of the type BC 149 C of which the h -parameters and the internal capacitances are $h_{fe} = 600$, $h_{ie} = 10 \text{ k}\Omega$, $C_{bc} = 2.5 \text{ pF}$, $C_{be} = 9 \text{ pF}$. If the coupling capacitor is $0.5 \text{ }\mu\text{F}$ and the load resistance is $10 \text{ K}\Omega$. Find the upper cut-off frequency and its gain. $(2 + 5) + (4 + 4)$



9. a) Give the circuit of colpitt's oscillator and explain its operation. Derive the condition for sustained oscillation and the expression for the frequency of oscillation of it.
 - b) What is the difference between Hartley and colpitt's oscillator.
 - c) An Hartle oscillator is designed with $L_1 = 20 \mu\text{H}$, $L_2 = 2\text{mH}$ and a variable capacitor. Determine the range of capacitance values if the frequency is varied between 950 2050 kHz. (5 + 5) + 2 + 3
10. a) What is power amplifier ? How does it differ from a voltage amplifier ?
 - b) Explain with circuit diagram the operation of a transformer coupled class A power amplifier and calculate its maximum power efficiency.
 - c) Two transistor operate in class B push pull circuit with a collector supply voltage $V_{cc} = 15$ volt. The turns ratio of the output transformer is 3 : 1 and the load resistance is 9 ohm. Determine maximum dc power supplied and the maximum output power. Also find out efficiency. 3 + 7 + 5
11. a) What are the criteria of a good instrumentation amplifier ? Describe the steps for building an instrumentation amplifier starting from the basic differential amplifier.



- b) Draw the circuit diagram of an astable multivibrator using 555 timer and derive the expression of its frequency of oscillation.
- c) For an astable multi-vibrator using 555 timer, $R_A = 6.8 \text{ K}\Omega$, $R_B = 3.3 \text{ K}\Omega$ and $C = 0.1 \text{ }\mu\text{F}$, calculate
- t_{HIGH}
 - t_{LOW}
 - free running frequency
 - duty cycle, D. (2 + 5) + 5 + 3

12. Write short notes on any *three* of the following : 3 × 5

- PLL
- Phase-shift oscillator
- Tuned amplifier
- Current mirror circuit
- Trans-conductance multiplier.

=====