



makautonline.com

**MAULANA ABUL KALAM AZAD UNIVERSITY OF  
TECHNOLOGY, WEST BENGAL**

**Paper Code : ES-201 ( PART-II )**

**BASIC ELECTRICAL & ELECTRONIC  
ENGINEERING - II**

Time Allotted :  $1\frac{1}{2}$  Hours

Full Marks : 35

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own  
words as far as practicable.*

makautonline.com

**PART - II ( Electronics )**

**GROUP - A**

**( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any *five* of the following :  $5 \times 1 = 5$

- i) A source follower using an FET has a voltage gain which is makautonline.com
- a) exactly unit but negative
  - ☒ b) slightly less than unity but positive
  - c) greater than + 100
  - d) none of these.

makautonline.com

- ii) The threshold voltage of an enhancement PMOS is
- a) Positive
  - ☒ b) Negative
  - c) Zero with respect to drain
  - d) Zero with respect to source.
- iii) The slew rate of an ideal OP-AMP is
- ☒ a) Zero
  - b) Infinite
  - c) Exactly unity
  - d) none of these.
- iv) Which of the following feedback topologies offers high input and output impedance ? makautonline.com
- a) Voltage series
  - b) Voltage shunt
  - ☒ c) Current series
  - d) Current shunt.
- v) Which of the following gate is called 'coincidence' gate ?
- a) AND
  - b) X-OR
  - ☒ c) NAND
  - d) X-NOR.
- vi) The decimal equivalent of  $10111.1011$  is
- a) 25.125
  - b) 32.4185
  - ☒ c) 23.6875
  - d) 32.6785.

**GROUP - B** makautonline.com

**( Short Answer Type Questions )**

Answer any *two* of the following.  $2 \times 5 = 10$

2. With proper sketch explain the drain characteristics of an  $n$ -channel JFET.
3. Derive suitable expressions to show the effects of negative feedback on input and output impedances of an amplifier.  $2\frac{1}{2} + 2\frac{1}{2}$   
makautonline.com
4. Mention the differences between ideal and practical Op-Amp. What do you mean by virtual ground in an Op-Amp?  $3 + 2$
5. a) What do you mean by Universal gates?  $2$   
b) Realise the following expression using NOR gates only –

$$Y = A' B' + AB. \quad 3$$

**GROUP - C** makautonline.com

**( Long Answer Type Questions )**

Answer any *two* of the following.  $2 \times 10 = 20$

6. a) Determine the value of  $g_{m0}$  for the graph shown in the Figure 1 :

makautonline.com

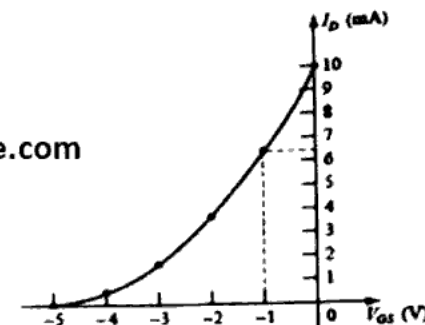


Figure 1

- b) Find out  $g_m$  for  $V_{gs} = -1.5$  V.
- c) Draw the Transfer Characteristics of an N-Ch FET. Explain the curve with the help of Shockley's Equation. makautonline.com
- d) Draw the small signal equivalent circuits for an FET.
- e) The Fixed Bias circuit has operating point defined by  $V_{gs} = -2$  V,  $I_{DQ} = 5.625$  mA as shown in Figure 2. If the output conductance is  $40 \mu S$  then find the following :
  - i)  $g_m$  makautonline.com

ii)  $r_d$

iii)  $R_i$

iv)  $R_o$

v)  $A_v$

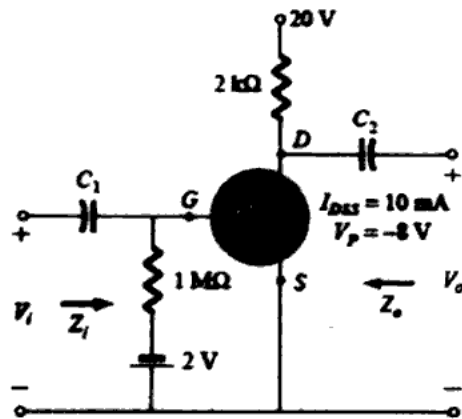


Figure 2

1 + 1 + 2 + 3 + 3

7. a) Design an adder circuit using an Op-Amp to get the output expression as –

$V_{out} = V_1 + 10V_2 + 100V_3$ , where  $V_1, V_2, V_3$  are inputs to the Op-Amp and  $R_F = 100 \text{ K}$ .

- b) How can an Op-Amp be used as an integrator ?
- c) What is an integrated circuit ? What are its advantages ?

3 + 4 + ( 1 + 2 )

8. a) State and explain the Barkhausen criteria.
- b) Derive an expression for the gain of an amplifier using positive feedback.
- c) A negative feedback of  $\beta = 0.002$  is applied to an amplifier of gain 1000. Calculate the change in the overall gain of the feedback amplifier if the internal gain of the amplifier is subjected to gain reduction of 15%.
- d) How does negative feedback affects the bandwidth of an amplifier ?

3 + 2 + 3 + 1

9. Write short notes on any two of the following :

2 × 1

- a) Enhancement type MOSFET
- b) Feedback amplifier topologies

CS/B.TECH/EVEN/SEM-2/ES-201 (PART-II)/2016-17

**makautonline.com**

- a) De Morgan's theorem
- d) CMRR and Slew rate
- e) Pinch-off condition to JFET
- f) Emitter-follower circuit.

**makautonline.com**