



ENGINEERING & MANAGEMENT EXAMINATIONS, JUNE - 2009
DIGITAL ELECTRONICS & INTEGRATED CIRCUITS
SEMESTER - 4

Time : 3 Hours]

[Full Marks : 70

GROUP - A**(Multiple Choice Type Questions)**

1. Choose the correct alternatives for any ten of the following :

10 × 1 = 10

i) The octal equivalent of the binary number 11010111 is

a) 656

b) 327

c) 653

d) D7.

 ii) The minimum number of NAND gates required to implement the Boolean function $A + AB' + AB'C$ is equal to


a) zero

b) 1

c) 4

d) 7.

 iii) Identify the operation of the following logic gate circuit.




a) OR gate


b) AND gate

c) NOT gate

d) none of these.

4526 (10/06)

 

 



3. Minimize the following expression in SOP form using Quine McClusky method :

$$F(A, B, C, D) = \sum m(1, 2, 3, 8, 9, 10, 11, 14) + \sum d(7, 15).$$

4. Explain the race around condition. Draw the Master/Slave JK flip-flop using all NAND gates. 2 + 3

5. Implement a full-adder circuit using 3 to 8 decoder with all active high outputs and other necessary logic gates.

6. Draw and explain the circuit of 8×1 MUX using two 4×1 MUX and one 2×1 MUX.


GROUP - C

(Long Answer Type Questions)

Answer any three of the following questions.

$3 \times 15 = 45$

 7. a) Design a clocked synchronous sequential network whose state diagram is given below : 8



- b) Design a combinational circuit, which converts excess - 3 number to its corresponding BCD number. 7

8. a) Implement the following Boolean expressions using Decoder.

$$F_1(A, B, C, D) = \sum (1, 2, 5, 7, 8, 10, 12, 13).$$

5

- b) Implement a full adder circuit using minimum number of NOR gates only. 5

4526 (10/06)

