

Name :

Roll No. :

Invigilator's Signature :

CS/B.Tech (EIE-NEW)/SEM-7/EE-701(EI)/2010-11

2010-11

POWER ELECTRONICS

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

GROUP - A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *ten* of the following : 10 × 1 = 10

i) PIV of full wave bridge rectifier is

- | | |
|---------------------|-------------------|
| a) $\sqrt{2} V_m$ | b) $2 V_m$ |
| c) $V_m / \sqrt{2}$ | d) none of these. |

ii) Reverse recovery current in a diode depends upon

- a) forward field current
- b) temperature
- c) storage current
- d) PIV.

CS/B.Tech (EIE-NEW)/SEM-7/EE-701(EI)/2010-11

- iii) For an SCR, $\frac{dv}{dt}$ protection is achieved through the use of
- a) RL in series with SCR
 - b) RC across SCR
 - c) L in series with SCR
 - d) L across SCR.
- iv) Forced commutation is generally employed in
- a) controlled rectifier b) cycloconverter
 - c) chopper d) none of these.
- v) In a single phase full converter, the number of SCR conducting during overlap is
- a) 1 b) 4
 - c) 3 d) 2.
- vi) When a power BJT is compared to power MOSFET
- a) BJT has lower switching losses but higher conduction losses
 - b) BJT has higher switching losses but lower conduction losses
 - c) BJT has lower switching losses and conduction losses
 - d) BJT has higher switching losses and conduction losses.

CS/B.Tech (EIE-NEW)/SEM-7/EE-701(EI)/2010-11

- vii) A forward voltage may be applied to the thyristor after its
- a) anode current reduces to zero
 - b) gate recovery time
 - c) reverse recovery time
 - d) anode voltage reduces to zero.
- viii) In a 1- ϕ full converter, for discontinuous load current and extinction angle $\beta > \pi$, each SCR conducts for
- a) α
 - b) $\beta - \alpha$
 - c) β
 - d) $\beta + \alpha$.
- ix) A single phase half-wave controlled rectifier has input voltage $V_s = 400 \sin 314t$. It is connected on load. For a triggering angle of 60° for SCR, the average output voltage is
- a) $400/\pi$
 - b) $300/\pi$
 - c) $240/\pi$
 - d) $200/\pi$.
- x) In a single-pulse modulation of PWM inverters, third harmonic can be eliminated if pulse width is equal to
- a) 30°
 - b) 60°
 - c) 120°
 - d) 150° .

CS/B.Tech (EIE-NEW)/SEM-7/EE-701(EI)/2010-11

- xi) In UJT, maximum value of charging resistance is associated with
- a) peak point
 - b) valley point
 - c) after valley point
 - d) any point between peak and valley points.
- xii) In a 3-phase semiconverter for firing angle equal to 120° and extinction angle equal to 110° , each SCR and diode conduct respectively for
- a) $30^\circ, 60^\circ$
 - b) $60^\circ, 60^\circ$
 - c) $90^\circ, 30^\circ$
 - d) $110^\circ, 30^\circ$

GROUP - B**(Short Answer Type Questions)**Answer any *three* of the following. $3 \times 5 = 15$

2. Draw and explain dynamic switching characteristics of power BJT.
3. Explain the two-transistor analogy of thyristor. Derive an equation for anode current. State the condition for turn-on.
 $2 + 2 + 1$
4. What is the difference between the natural & forced commutations ? Explain the method of auxiliary commutation circuit.

CS/B.Tech (EIE-NEW)/SEM-7/EE-701(EI)/2010-11

5. a) Design the triggering circuit of PUT. The parameters of the PUT are supply voltage = 30 V, gate current = 1 mA. The frequency of oscillation $f = 60$ Hz. The pulse width is 50 μ sec, peak point voltage = 10 V.
- b) Explain the effect of gate voltage over it. 3 + 2
6. Explain the operating principle of TRIAC with suitable diagram.

GROUP - C**(Long Answer Type Questions)**Answer any *three* of the following. 3 \times 15 = 45

7. a) Explain Boost and Cuk converters with neat circuit diagrams.
- b) What is advantageous between these two ? State briefly.
- c) A step-up chopper operating at 20 kHz has non-conductive time 20 micro-seconds. Calculate output voltage if input voltage is 100 V DC. 8 + 3 + 4
8. a) Thyristor is self latching device. Explain/with the help of two-transistor analogy.

CS/B.Tech (EIE-NEW)/SEM-7/EE-701(EI)/2010-11

b) What is UJT ? What is the peak voltage of a UJT ? What is the valley point voltage of a UJT ? What is the intrinsic stand-off ratio of UJT ? What are the advantages of a PUT over a UJT ?

c) The UJT relaxation oscillator uses UJT for triggering an SCR. The UJT has the following characteristics :

Intrinsic stand-off ratio = 0.7, peak point voltage = 50 μ A valley point voltage = 2 V, valley point current = 6 mA, supply voltage = 20 V, inter-base resistance = 7 K, emitter current = 2 mA. 5 + 5 + 5

9. a) Why is a three phase bridge control rectifier called a three pulse converter ?

b) In a single phase full-wave diode bridge rectifier, the diode has a reverse recovery time of 40 μ sec for an a.c. input voltage of 230 V. Determine the effect of reverse recovery time on the average output voltage for a supply frequency of

i) 50 Hz

ii) 2.5 kHz.

CS/B.Tech (EIE-NEW)/SEM-7/EE-701(EI)/2010-11

- c) With the suitable waveform explain the operation of a single phase uncontrolled rectifier with R-L load. Deduce the expression of RMS and average value of output voltage.
- d) 1-phase half controlled converter is with resistive load where the delay angle is $\frac{\pi}{4}$. Find the
- rectifier efficiency
 - form factor
 - ripple factor.
- 1 + 4 + 5 + 5

10. a) What is cyclo-converter ? Describe the operating principle of a 1- ϕ to 1- ϕ step-up cyclo-converter with the help of bridge type configuration. Illustrate your answer with appropriate circuit and waveforms. The conduction of various SCR's should also be indicated in the diagram.
- b) Draw the schematic circuit of a circulating current mode cyclo-converter and its operating waveforms.
- c) What are the merits and demerits of a cyclo-converter compared to a variable frequency a.c. motor drive ?

7 + 4 + 4

CS/B.Tech (EIE-NEW)/SEM-7/EE-701(EI)/2010-11

11. Write short notes on any *three* of the following :

3 × 5

- a) UPS
- b) IGBT
- c) Flyback converter
- d) Resonant series converter
- e) Induction heating.

501
EIE(7)