

CS/B.TECH/EEE/EE/ICE/ODD/SEM-3/EC(EE)-302/2017-18



**MAULANA ABUL KALAM AZAD UNIVERSITY OF  
TECHNOLOGY, WEST BENGAL**

**Paper Code : EC(EE)-302**

**DIGITAL ELECTRONIC CIRCUIT**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

**GROUP - A**

**( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any ten of the following : 10 × 1 = 10

- i) Gray code of 1011 (binary) = 1101
  - a) 0101
  - ☒ b) 1101
  - c) 1110
  - d) none of these.
- ii) An example of reflected code is
  - a) BCD
  - b) ASCII
  - c) GRAY
  - ☒ d) Hamming code.
- iii) The minimum number of NAND gates required to design one X-OR gate is
  - a) 3
  - b) 4
  - c) 5
  - d) 6.
- iv) If  $(212)_x = (23)_{10}$ , where  $x$  is base ( + ve integer ) then the value of  $x$  is
  - a) 2
  - ☒ b) 3
  - c) 4
  - d) 5.

CS/B.TECH/EEE/EE/ICE/ODD/SEM-3/EC(EE)-302/2017-18

- v) Full form of FPGA is
  - a) Full Programmable Gated Array
  - b) Field Programmable Gated Array
  - c) Full Peripheral Gated Array
  - d) Field Peripheral Gated Array.
- vi) The resolution of 8-bit A/d converter is
  - a) 0.62 %
  - b) 0.38 %
  - c) 0.39 %
  - d) 1.25 %.
- vii) One bit even parity detector code fails to detect
  - a) any even number of error
  - b) any odd number of error
  - c) both (a) and (b)
  - d) none of these.
- viii) What is the word size of  $16 \times 8$  ROM ?
  - a) 16
  - b) 8
  - c) 128
  - d) none of these.
- ix)  $(A + B' + A'B)C =$ 
  - a) 1
  - b) 0
  - ☒ c) C
  - d) C'
- x) F/F that makes output equals to input after clock is
  - ☒ a) J-K F/F
  - b) D F/F
  - c) T F/F
  - d) none of these.
- xi) 8421 is a
  - ☒ a) weighted code
  - b) non-weighted code
  - c) complementary code
  - d) none of these.
- xii) The characteristic equation of T flip-flop is given by
  - ☒ a)  $Q^+ = \bar{T}Q + T\bar{Q}$
  - b)  $Q^+ = \bar{T}\bar{Q} + TQ$
  - c)  $Q^+ = T\bar{Q}$
  - d) none of these.

CS/B.TECH/EEE/EE/ICE/ODD/SEM-3/EC(EE)-302/2017-18


**GROUP - B****( Short Answer Type Questions )**Answer any three of the following.  $3 \times 5 = 15$ 

2. Using the K-map method, simplify the following Boolean function and obtain minimal POS expression :  


$$Y = \sum_m (0, 2, 6, 7) + \sum_d (3, 8, 10, 11, 15)$$
3. Implement a full adder circuit by using two 2 : 1 multiplexers.
4. Design a full adder using minimum number of NAND gates.
5. Realize a D flip-flop by using a T flip-flop and other required logic gates.
6. Construct a full substructure by using two half substructures and an OR gate.

**GROUP - C****( Long Answer Type Questions )**Answer any three of the following.  $3 \times 15 = 45$ 

 7. a) Draw the timing diagram of a D flip-flop & D-latch for the given input signals.  $7 + 8$



 - b) Draw a neat diagram of an R-2R ladder type DAC.
8. a) Design a sequential circuit that implements the following state diagram. Using all D-type flip-flops for the design.



30103

3

{ Turn over

CS/B.TECH/EEE/EE/ICE/ODD/SEM-3/EC(EE)-302/2017-18

- b) Draw and explain the BCD adder using 7483.

10 + 5

9. a) Explain the operation of PROM, and EPROM.
- b) Design a 5 Mod synchronous binary counter using J-K flip-flop and necessary logic gates.  $6 + 9$
10. a) What are the differences between the Decoder and Demultiplexer ?
- b) Form a multiplexer tree to give 8 : 1 MUX from two 4 : 1 MUX and 2 : 1 MUX.
- c) Implement a full-adder circuit using 3 to 8 decoders with all active high outputs and other necessary logic gates.  $2 + 6 + 7$
11. Write short notes on any three of the following :  $3 \times 5$ 
  - a) Shift registers ✓
  - b) Johnson counter
  - c) Successive Approximation Type A/D Converter
  - d) Noise margin
  - e) Master-slave JK flip-flop. ✓

30103

4