

Name : .....

Roll No. : .....

Invigilator's Signature : .....

CS/B.Tech/(EE/ECE/PWE/EEE/CSE/IT/BME/ICE)/SEM-3/EE-301/2010-11

2010-11

**CIRCUIT THEORY & NETWORKS**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.***GROUP – A****( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any
- ten*
- of the following :

10 × 1 = 10

- i) The Laplace transform of a shifted unit step
- $f(t) = U(t - a)$
- is

- |               |                     |
|---------------|---------------------|
| a) $e^{-as}$  | b) $e^{-as/s}$      |
| c) $se^{-as}$ | d) $s(1 - e^{-as})$ |

- ii) A tie-set matrix has 3 rows and 7 branches. The number of twigs is

- |      |       |
|------|-------|
| a) 3 | b) 5  |
| c) 2 | d) 4. |

- iii) Unit step function is first derivative of

- |                  |                        |
|------------------|------------------------|
| a) Ramp function | b) Impulse function    |
| c) Gate function | d) Parabolic function. |

3051


[ Turn over

CS/B.Tech/(EE/ECE/PWE/EEE/CSE/IT/BME/ICE)/SEM-3/EE-301/2010-11

iv) A circuit having neither an e.m.f. source nor any energy source is


- a) active circuit                      b) passive circuit  
c) unilateral circuit                  d) bilateral circuit.

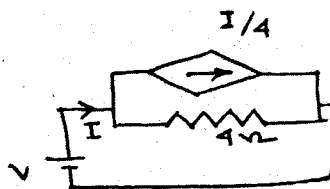v) In the network shown in the figure, the effective resistance faced by the voltage source is



- a)  $4\Omega$                                       b)  $3\Omega$   
c)  $2\Omega$                                       d)  $1\Omega$ .

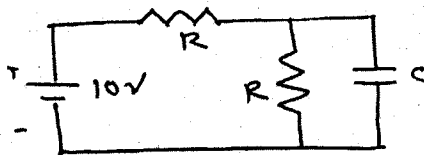
vi) The time constant of the network shown in the figure is



- a)  $2RC$                                       b)  $\frac{3}{2}RC$   
c)  $\frac{RC}{2}$                                       d)  $\frac{2RC}{3}$ .

CS/B.Tech/(EE/ECE/PWE/EEE/CSE/IT/BME/ICE)/SEM-3/EE-301/2010-11

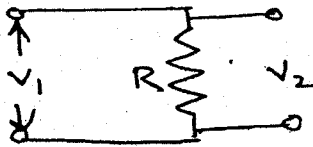vii) The Z parameter of the following network is



a)  $\begin{bmatrix} R & R \\ R & R \end{bmatrix}$

b)  $\begin{bmatrix} R & 0 \\ 0 & R \end{bmatrix}$

c)  $\begin{bmatrix} R & -R \\ -R & R \end{bmatrix}$

d) Cannot be determined.

viii) Two equal impedances  $10\angle 60^\circ$  are connected in parallel.

The equivalent impedance will be

a)  $20\angle 60^\circ$

b)  $10\angle 120^\circ$

c)  $15\angle 120^\circ$

d)  $5\angle 60^\circ$

ix) A series resonant circuit at resonance is called

a) an acceptor circuit

b) a rejector circuit

c) an oscillator circuit

d) a damped circuit.

x) The average power delivered to a reactive load is

a) zero

b)  $VI \sin \phi$

c)  $v(t) + i(t)$

d)  $\frac{1}{2} V_m I_m \sin \phi$

CS/B.Tech/(EE/ECE/PWE/EEE/CSE/IT/BME/ICE)/SEM-3/EE-301/2010-11

xi) The output  $Y$  and input  $X$  of a system are related by the equation  $Y = mX + c$ , where  $m, c$  are constants. The system is

- a) linear
- b) non-linear
- c) bilateral
- d) unilateral.

xii) The Fourier transform can be used to represent


- a) any signal
- b) all periodic signals
- c) all non-periodic signals
- d) all periodic signals that obey Dirichlet's condition.

#### GROUP - B

( Short Answer Type Questions )


Answer any *three* of the following.  $3 \times 5 = 15$

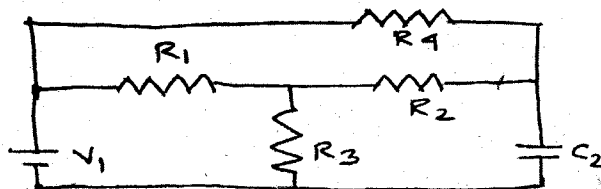2. Draw the oriented graph of the figure shown and find the incidence matrix.




CS/B.Tech/(EE/ECE/PWE/EEE/CSE/IT/BME/ICE)/SEM-3/EE-301/2010-11

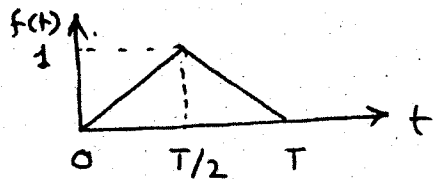
3. Find the Laplace transform of the triangular waveform shown.



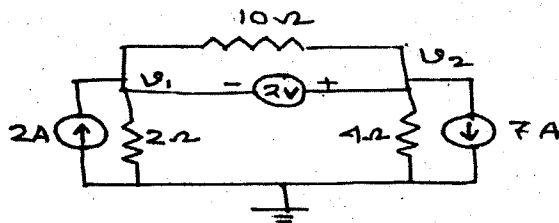4. For the circuit shown below, find the node voltages.



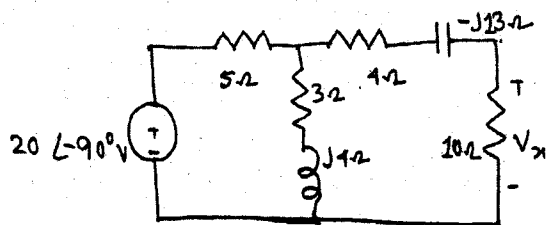5. Compute  $V_x$  in the circuit shown below using the method of source transformation.




6. Find the rms value of the periodic current ;

$$i(t) = 8 + 30 \cos 2t - 20 \sin 2t + 15 \cos 4t - 10 \sin 4t \text{ A.}$$


CS/B.Tech/(EE/ECE/PWE/EEE/CSE/IT/BME/ICE)/SEM-3/EE-301/2010-11

**GROUP - C****( Long Answer Type Questions )**Answer any three of the following.  $3 \times 15 = 45$ 

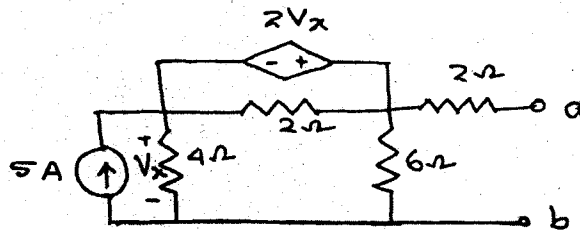
7. a) Find the Thevenin equivalent of circuit shown below :



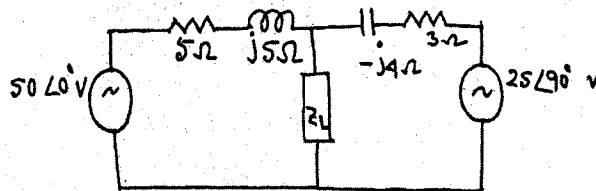- b) Find the load impedance  $Z_L$  to transfer maximum power in the circuit shown. Find also the value of power consumed by the load.  $7 + 8$




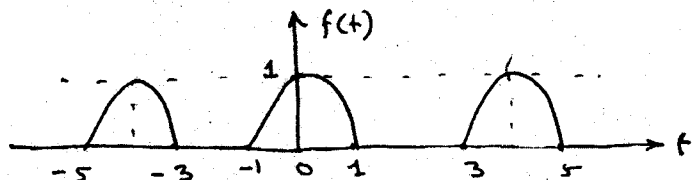8. a) Determine the Fourier series for the half wave rectified cosine function shown.




CS/B.Tech/(EE/ECE/PWE/EEE/CSE/IT/BME/ICE)/SEM-3/EE-301/2010-11

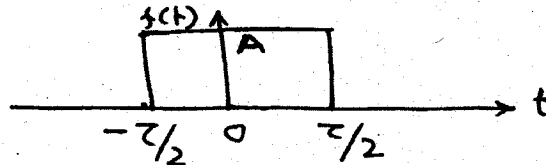
- b) Derive the Fourier transform of a single rectangular pulse of width  $\tau$  and height  $A$  shown below : 10 + 5



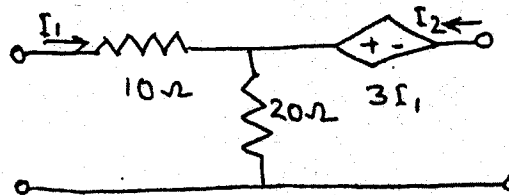
9. a) Find the transmission parameters for the two-part network shown below :



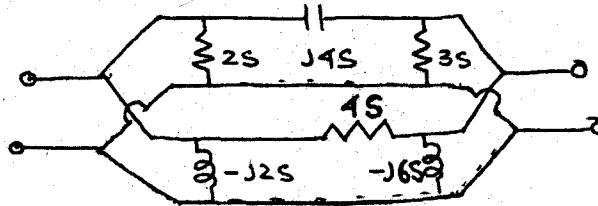- b) Find the Y parameters of the two-part network shown below : 8 + 7




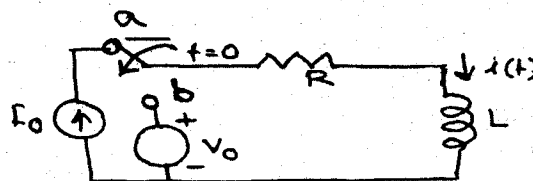10. a) In the circuit shown below, the switch moves from position  $a$  to position  $b$  at  $t = 0$ . Find  $i(t)$  for  $t > 0$ .



CS/B.Tech/(EE/ECE/PWE/EEE/CSE/IT/BME/ICE)/SEM-3/EE-301/2010-11

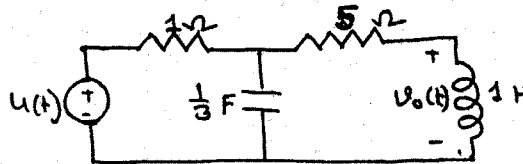- b) Find  $v_o(t)$  in the circuit shown below. Assume zero initial condition. 8 + 7



11. a) Draw the circuit diagram of a first order highpass filter & find out the expression of the cut-off frequency.
- b) What do you mean by wide bandpass and narrow band-pass filters ? Draw the circuit diagram for the two types of filters.
- c) Find the cut-off frequency of the following lowpass second order active filter shown below. 5 + 5 + 5

