

Name : .....

Roll No. : .....

Invigilator's Signature : .....

**CS/B.Tech(N)/SEM-1/ES-101/2012-13**

**2012**

**BASIC ELECTRICAL &  
ELECTRONICS ENGINEERING – I**

*Time Allotted : 3 Hours*

*Full Marks : 70*

**THIS QUESTION BOOKLET CONSISTS OF 2 PARTS —  
PART I & PART II.  
TO ANSWER THE QUESTIONS USE SEPARATE ANSWER  
BOOKS FOR SEPARATE PARTS.  
DO NOT ANSWER BOTH THE PARTS IN THE SAME  
ANSWER-BOOK.**

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words  
as far as practicable.*

**PART – I**

**( Marks : 35 )**

**GROUP – A**

**( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any *five* of the following :

$5 \times 1 = 5$

- i) Conductance is analogous to

- |               |                |
|---------------|----------------|
| a) permeance  | b) flux        |
| c) reluctance | d) inductance. |

1251 (N)

[ Turn over



- ii) Energy stored by a capacitor is given by
- a)  $\frac{1}{2} CV^2$
  - b)  $\frac{1}{2} QV$
  - c)  $\frac{Q^2}{2C}$
- iii) In an electrical circuit, if the current lags the voltage by  $60^\circ$ , the circuit nature is
- a)  $R-C$
  - b)  $R-L$
  - c)  $LC$
  - d) none of these.
- iv) Kirchhoff's voltage law is used for
- a) loop analysis
  - b) node analysis
  - c) finding out equivalent resistance
  - d) none of these.
- v) If  $E_1 = A \sin \omega t$  and  $E_2 = A \sin (\omega t - \theta)$ , then
- a)  $E_1$  lags  $E_2$
  - b)  $E_2$  lags  $E_1$
  - c)  $E_1$  and  $E_2$  are in phase
  - d) none of these.
- vi) The bandwidth of a series resonant a.c. circuit is equal to
- a)  $\frac{R}{(2\pi L)}$
  - b)  $\frac{1}{(RLC)}$
  - c)  $\frac{1}{(2\pi R)}$
  - d)  $\frac{1}{(\omega C)}$ .




**GROUP – B**

**( Short Answer Type Questions )**


Answer any *two* of the following.

$2 \times 5 = 10$

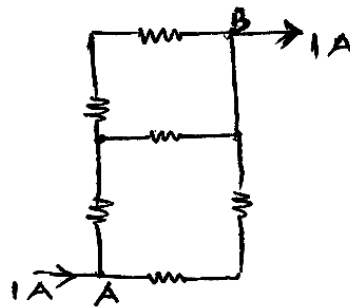2. Derive an expression for the resonant frequency of a parallel circuit, one branch consisting of a coil of inductance  $L$  and a resistance  $R$  and the other branch of capacitance  $C$ .
3. Establish the equivalence between Thevenin's and Norton's theorems.
4. Find  $V_{AB}$  from the circuit if all the resistances are of same value of 1 ohm.



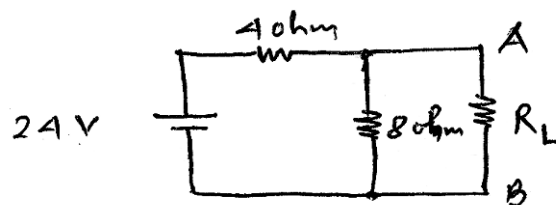5. Find the value of load resistance ( $R_L$ ) for which the power source will supply maximum power. Also find the value of the maximum power for the network as shown below :






**GROUP – C**

**( Long Answer Type Questions )**


Answer any *two* of the following.

$2 \times 10 = 20$

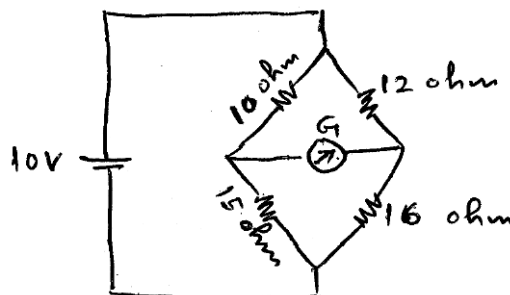6. a) Define power factor of an A.C. circuit. State the disadvantages associated with having a load power factor. 4
- b) The galvanometer shown in the circuit has a resistance of 5 ohms. Find the current through the galvanometer using Thevenin's theorem.



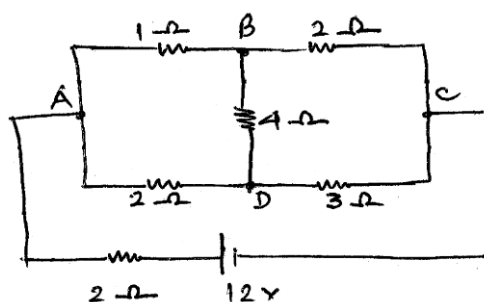7. a) Find the current in each branch of the network using Kirchhoff's law. 5



- b) Prove that the current in a purely resistive circuit is in phase with applied A.C. voltage and current in a purely capacitive circuit leads applied voltage by  $90^\circ$  and also draw their waveforms. 5



8. a) Define self and mutual inductance. Derive an expression for coefficient of coupling ( $k$ ) involving self inductances  $L_1$  &  $L_2$  and mutual inductance  $M$ . 4
- b) What is meant by hysteresis in a magnetic circuit ?  
What is the significance of B-H curve ? 3
- c) Find an expression for the energy stored in a magnetic field. 3
9. Explain (a) Star-delta conversion, (b) delta-star conversion with the help of a purely resistive circuit. 5 + 5

**USE SEPARATE ANSWER-BOOK TO ANSWER PART-II QUESTIONS.**

**PART – II**

**( Marks : 35 )**


**GROUP – A**

**( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any *five* of the following :

$$5 \times 1 = 5$$

- i) A transistor having a high input impedance and a low output impedance is operating in
- |            |                   |
|------------|-------------------|
| a) CB mode | b) CE mode        |
| c) CC mode | d) inverted mode. |

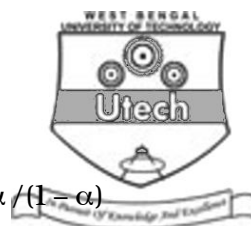

- ii)  $\alpha$  and  $\beta$  of a transistor are related by
- a)  $\alpha = (\beta + 1) / \beta$                       b)  $\beta = \alpha / (1 - \alpha)$   
c)  $\beta = \alpha / (1 + \alpha)$                       d)  $\alpha = \beta / (1 - \beta)$ .
- iii) The ripple factor of a half wave rectifier is
- a) 0.482                                      b) 0.41  
c) 1.21                                        d) 1.11
- iv) When both junctions are reverse biased, a transistor operates in
- a) active                                      b) saturation  
c) cut-off                                      d) inverted region.
- v) Band gap of Ge is
- a) 0.54 eV                                      b) 1.1 eV  
c) 0.72 eV                                      d) none of these.
- vi) An  $n$ -type semiconductor is
- a) negatively charged  
b) positively charged  
c) neutral.

### GROUP – B

#### ( Short Answer Type Questions )

Answer any *two* of the following.                       $2 \times 5 = 10$

2. Explain the operation of a full wave rectifier with centre tapped transformer and draw the D.C. output waveform.
3. What is the role of doping of impurities in pure silicon or germanium ? Draw roughly the position of Fermi level for extrinsic semiconductor and explain.




4. Write a sort note on varactor diode.
5. At 300 K, the intrinsic carrier concentration of silicon is  $1.5 \times 10^{16} \text{ m}^{-3}$ . If the electron and hole mobilities are 0.13 and 0.05  $\text{m}^2\text{V}^{-1}\text{s}^{-1}$ , calculate the intrinsic resistivity of Si at 300 K.

### GROUP – C


#### ( Long Answer Type Questions )

Answer any *two* of the following.  $2 \times 10 = 20$

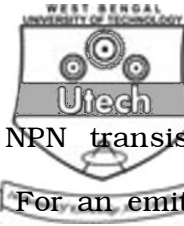6. a) Write the differences between Zener breakdown and avalanche breakdown. 3
- b) Explain how a Zener diode can act as a voltage regulator. 4
- c) Write a short note on clipper circuit. 3
7. a) Discuss the static characteristics of transistor in CB configuration. 5
- b) What do you mean by intrinsic semiconductor ? Explain drift and diffusion current for a semiconductor . 2 + 3



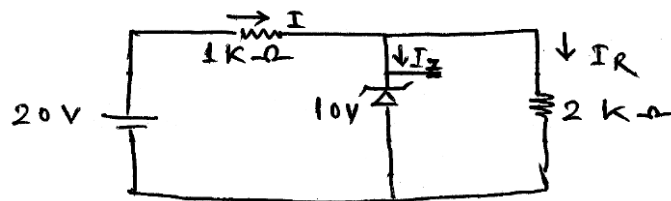8. a) The reverse saturation current of a NPN transistor operating in CB configuration is  $10 \mu\text{A}$ . For an emitter current of  $2.4 \text{ mA}$ , the collector current is  $2.26 \text{ mA}$ . Calculate the current gain and base current. 5
- b) Calculate the current  $I$ ,  $I_R$  and  $I_Z$  for the following circuit. 5



9. Write short notes on any *two* of the following : 2 × 5
- a) Clamper circuit
  - b) Fermi level
  - c) Junction capacitance.

=====