



Name :

Roll No. :

Invigilator's Signature :

CS/B.Tech (ECE)/SEM-4/EC-401/2010

2010

ANALOG ELECTRONIC CIRCUITS

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

GROUP – A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *ten* of the following : 10 × 1 = 10

i) To start the oscillation, the gain of a Wien-bridge oscillator is to be

- | | |
|----------|------------|
| a) > 1 | b) > 2 |
| c) < 1 | d) < 2 . |

ii) The o/p imp. of a series voltage amplifier is

- | | |
|----------------------|---------------------|
| a) $R_o/(1+\beta A)$ | b) $R_o(1+\beta A)$ |
| c) $\beta R_o/(1+A)$ | d) none of these. |

iii) Max. phase shift in a two-pole network is

- | | |
|----------------|------------------|
| a) 90° | b) 150° |
| c) 180° | d) 270° . |

- 4003



- ix) The Q point in a voltage amplifier is selected in the middle of the active region because
- a) it gives better stability
 - b) the circuit needs a small *d.c.* voltage
 - c) the biasing circuit then needs less number of resistors
 - d) it gives a distortionless output.
- x) An ideal regulated power supply should have regulation which is
- a) maximum
 - b) 50%
 - c) zero
 - d) 75%.
- xi) To avoid false triggering of the NE 555 timer, the RESET pin (Pin 4) is generally connected to
- a) Pin 8
 - b) Pin 1
 - c) Pin 3
 - d) No connection (NC).
- xii) In a logarithmic amplifier, the logarithmic effect of the input is obtained from
- a) non-linear device, like diode or transistor
 - b) negative feed-back
 - c) the Op-Amp itself
 - d) the inverting input terminal.



xiii) The value of V_0 for the following circuit is given by

- a) $-3V_1 + 2V_2$ b) $-3V_2$
- c) $1.5V_2 - 2.55V_1$ d) $2V_2 - 3V_1$

xiv) Differential amplifier can be used to amplify

- a) only A.C. signal (input)
- b) only D.C. signal (input)
- c) both A.C and D.C. signals
- d) none of these.

xv) Heat sinks are used in power amplifier circuits primarily to increase

- a) the output power
- b) the voltage gain
- c) collector dissipation rating of the transistor
- d) dissipation of energy of free electrons.



GROUP – B
(Short Answer Type Questions)

Answer any *three* of the following. $3 \times 5 = 15$

2. What do you mean by clamping circuit ? Draw its circuit diagram and discuss its operation.
3. What is Common Mode Rejection Ratio (CMRR) and Slew rate of Operational Amplifier ?
4. What is the difference between series and shunt regulators ? Draw the circuit diagram of a series regulator.
5. List the three sources of instability of collector current in a transistor. Define three stability factors.

GROUP – C
(Long Answer Type Questions)

Answer any *three* of the following. $3 \times 15 = 45$

6. a) Draw the circuit diagram of an emitter follower and explain the nature of feedback in this circuit. What is the feedback topology of the emitter follower ? Derive an expression for the voltage gain of the circuit from the concept of feedback. $2 + 1 + 3$
- b) Show that negative feedback improves the stability of the gain of an amplifier. 4



- c) The open-loop gain of an amplifier is -200 . A voltage series negative feedback is used with a feedback ratio of -0.02 . The input and the output impedances of the amplifier are $2\text{ k}\Omega$ and $40\text{ k}\Omega$, respectively in the absence of feedback. Determine the closed loop gain, and the input and the output impedances when the feedback circuit is completed. 5
7. a) Draw & explain a circuit which uses a diode to compensate for changes
- i) in V_{BE}
- ii) in I_{CO} . 6
- b) Quiescent levels of the network in figure are given as : $I_{CQ} = 1.1\text{ mA}$ & $V_{CEQ} = 3.7\text{ V}$. When $V_{CC} = 10\text{ V}$, $R_B = 250\text{ k}$ & transistor parameters are $\beta = 90$ & $V_{BE} = 0.7\text{ V}$ and at room temperature, find R_C & R_E . 5
- c) Explain the consequences of Early effect (base-width modulation). 4



8. a) Draw the circuit diagram of a voltage to current converter (grounded load) and explain its operation. 5
- b) What is Schmitt trigger ? Explain with circuit diagram. 5
- c) Explain Logarithmic amplifier with circuit diagram. 5
9. a) Draw the *a.c.* equivalent circuit of dual input balanced output differential amplifier and find out the expression of differential gain (A_{id}), input impedance, output impedance. 10
- b) Mention the advantages of active filters over passive filters. 5
10. Write short notes on any *three* of the following : $3 \times 5 = 15$
- a) Comparator
- b) Astable multivibrator
- c) Schottky diode
- d) Switch Mode Power Supply (SMPS)
- e) DC load line.
-