

CS/B.Tech/(EE/EEE/ICE)-(NEW)/SEM-3/EC(EE)-301/2013-14

2013

**ANALOG ELECTRONIC CIRCUITS**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

**GROUP - A**

**( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any ten of the following :  
 $10 \times 1 = 10$

i) Gain of the emitter follower is approximately equal to

- |             |                             |
|-------------|-----------------------------|
| a) $\alpha$ | b) $\beta + 1$              |
| c) $\beta$  | d) $\frac{1}{(1 - \alpha)}$ |

ii) To improve the efficiency of amplifier we have to reduce

- a) the power dissipation rating
- b) supply voltage
- c) the load power
- d) unwanted power loss.

iii) An instrumentation amplifier

- a) is a differential amplifier
- b) has a gain less than one
- c) has very high output impedance
- d) has low CMRR.

iv) Saturation region of a BJT implies

- a) base-emitter junction forward biased, base-collector junction reverse biased
- b) base-emitter junction forward biased, base-collector junction forward biased
- c) base-emitter junction reverse biased, base-collector junction reverse biased
- d) none of these.

v) A differential amplifier has the differential amplifier gain of 100. If its CMRR = 240, then the common mode gain is

- |          |          |
|----------|----------|
| a) 0.24  | b) 0.417 |
| c) 24000 | d) 1.    |

vi) A full-wave rectifier supplies 0.2A current at 30V DC. The ripple factor to be expected when two 100 mF capacitor and one 5H inductor are used in a  $\pi$ -filter with a 50Hz supply is

- a) 0.0076%                      b) 0.076%
- c) 0.76%                        d) 76%.

vii) The  $Q$  point in a voltage amplifier is selected in the middle of the active region because

- a) it gives better stability
- b) the circuit needs a better small signal DC voltage
- c) the biasing circuit needs a small DC voltage
- d) it gives distortion-less output.

viii) The current gain of a bipolar transistor drops at high frequencies because of

- a) transistor capacitances
- b) high current effects in the base
- c) parasitic inductive elements
- d) the early effect.

ix) The gain required for sustained oscillation in Wien-bridge oscillator is

- a) 29                                      b) 3
- c) 1                                        d) 1.5.

x) A dc power supply has no-load voltage of 30V and a full-load voltage of 25V at full-load current of 1A. Its output resistance & load regulation, respectively are

- a) 5  $\Omega$  & 20%
- b) 25  $\Omega$  & 20%
- c) 5  $\Omega$  & 16.7%
- d) 25  $\Omega$  & 16.7%.

xi) The output voltage of an IC7915 is

- a) 15V                                      b) - 15V
- c) 79V                                        d) - 79V.

xii) An instrumentation amplifier has a high

- a) Supply voltage
- b) Power gain
- c) CMRR
- d) Output impedance.

**GROUP - B**

**( Short Answer Type Questions )**

Answer any *three* of the following.  $3 \times 5 = 15$

- 2. Write down the effect of base width modulation. Explain the compensation technique using Thermistor.
- 3. What are the criteria of a good instrumentation amplifier ? Why is it needed ? Draw the circuit diagram of an instrumentation amplifier.
- 4. What is a multivibrator ? Explain the operation of a monostable multivibrator using 555 timer and draw the output voltage waveform.
- 5. What are the differences between series and shunt regulators ? Draw a circuit of a shunt regulator and explain its operation.
- 6. Draw and explain the Schmitt Trigger circuit using OP-AMP.

**GROUP - C**

**( Long Answer Type Questions )**

Answer any *three* of the following.  $3 \times 15 = 45$

- 7. Explain Barkhausen criteria for oscillation and find out frequency of oscillation in phase shift oscillator and also prove that the amplifier gain in a phase shift oscillator is 29 for sustained oscillation. Discuss the advantages of Switched Mode Power Supply ( SMPS ) over regulated power supply. Using a circuit diagram explain in short the operation of SMPS.  $2 + 6 + 7$
- 8. What do you mean by regulation ? Draw and explain a CLC or  $\pi$  filter. Draw and explain the operation of shunt regulated power supply.  $2 + 4 + 4 + 5$
- 9. Explain the operation of a Class B push-pull amplifier and prove that the efficiency is 78.5%. What is cross-over distortion in Class B amplifier and how can we remove the problem ? Compare different types of power amplifier in respect of efficiency and phase response.  $7 + 4 + 1 + 3$
- 10. In what respects Class B push-pull amplifier configuration is better than Class A push-pull amplifier ? What are the major drawbacks of Class B operation and how is it remedied ? Prove that the maximum efficiency of a Class B amplifier is 78.5%. What is the function of tuned amplifier ?  $3 + 3 + 5 + 4$

CS/B.Tech/(EE/EEE/ICE)-(NEW)/SEM-3/EC(EE)-301/2013-14

11. Write short notes on any *three* of the following :  $3 \times 5$

- a) Clamping and clipping circuit
  - b) Tuned amplifier
  - c) Antilog amplifier
  - d) Precision rectifier
  - e) Triangular wave generator.
- 

<http://www.makaut.com>

<http://www.makaut.com>