

Name : .....

Roll No. : .....

Invigilator's Signature : .....

**CS/B.Tech(EE-N)/SEM-4/EC(EE)-401/2010  
2010**

**ANALOG ELECTRONIC CIRCUITS**

**Time Allotted : 3 Hours**

**Full Marks : 70**

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words  
as far as practicable.*

**GROUP - A**

**( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any ten of the following :

$10 \times 1 = 10$

- i) The gain required for sustained oscillation in  
Wien-bridge oscillator is

- |       |        |
|-------|--------|
| a) 29 | b) 1.5 |
| c) 3  | d) 1.  |

- ii) The function of a linear voltage regulator is to

- |   |
|---|
| a) minimize the change in voltage at any load<br>condition        |
| b) reduce the ripple at the output voltage                        |
| c) reduce the voltage fluctuation due to sudden<br>change in load |
| d) supply constant current at all load condition.                 |

**4005**

**[ Turn over**



## CS/B.Tech(EE-N)/SEM-4/EC(EE)-401/2010

- viii) An instrumentation amplifier
- a) is a differential amplifier
  - b) has a gain less than 1
  - c) has very high output impedance
  - d) has low CMRR.
- ix) In an amplifier, a coupling capacitor is used to
- a) match the impedance
  - b) control frequency
  - c) limit bandwidth
  - d) prevent dc mixing with the output.
- x) To avoid false triggering of the NE 555 timer, the RESET pin ( Pin 4 ) is generally connected to
- a) Pin 8
  - b) Pin 3
  - c) Pin 1
  - d) no connection ( NC ).
- xi) The output pulse width for a monostable multivibrator using IC 555 where external resistance and capacitance are  $20\text{ k}\Omega$  and  $0.1\text{ }\mu\text{F}$  is
- a)  $2.1\text{ s}$
  - b)  $2\text{ ms}$
  - c)  $2.5\text{ ms}$
  - d)  $2.2\text{ }\mu\text{s}$ .
- xii) A push-pull amplifier balances out
- a) odd harmonics
  - b) even harmonics
  - c) odd as well as even harmonics
  - d) neither odd nor even harmonics.




CS/B.Tech(EE-N)/SEM-4/EC(EE)-401/2010

5. a) Draw the output waveforms if input of a differentiator is
- Triangular wave
  - Square wave.
- b) Obtain the expression for output voltage of an integrator using Op-Amp.
6. Write a note with related mathematical derivation of Op-Amp as an inverting and non-inverting amplifier. What is buffer ?

**GROUP - C****( Long Answer Type Questions )**Answer any *three* of the following.  $3 \times 15 = 45$ 

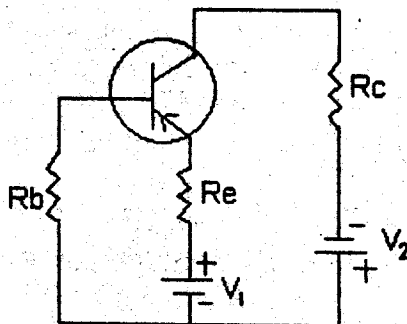7. a) Draw and explain the self bias circuit for a BJT. 6
- b) For the two-battery transistor circuit shown, prove that the stabilization factor  $S$  is given by

$$S = \frac{1 + \beta}{1 + \beta R_e / (R_e + R_b)} \quad 6$$



- c) Define load line and  $Q$ -point. Why is the line called 'load line' ?  $2 + 1$

**CS/B.Tech(EE-N)/SEM-4/EC(EE)-401/2010**

8. a) What do you mean by the conversion efficiency of a power amplifier ? 2
- b) Draw the circuit of a Class B push-pull power amplifier and show that its maximum power efficiency is 78.5%. 8
- c) Explain with a neat diagram the working of a Class C tuned power amplifier. 5
9. a) Draw and explain the operation of a monostable multivibrator using 555 timer. 5
- b) With a neat diagram explain the operation of a square wave generator and hence prove that the frequency of oscillation depends only on external components used. 5
- c) Draw and explain the operation of a clipper circuit using Op-Amp. 5
10. a) What is a voltage regulator ? Write down the advantages of adjustable voltage regulator over fixed voltage regulators. 2 + 3
- b) With a proper circuit diagram explain the operation of a series voltage regulator. 5
- c) Explain the operation of a current mirror circuit. 5

---

CS/B.Tech(EE-N)/SEM-4/EC(EE)-401/2010

11. Write short notes on any *three* of the following : 3 × 5

- a) Current mirror
  - b) SMPS
  - c) PLL
  - d) Wave shaper
  - e) Enhancement MOSFET.
-