

CS/B.Tech/Odd/Sem-1st/ES-101/2015-16



MAULANA ABUL KALAM AZAD UNIVERSITY OF TECHNOLOGY,
WEST BENGAL

ES-101

BASIC ELECTRICAL AND ELECTRONIC ENGINEERING - I

Time Allotted: 3 Hours

Full Marks: 70

*The questions are of equal value
The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.
All symbols are of usual significance*

PART - I (Electrical)

GROUP A

(Multiple Choice Type Questions)


1. Answer any five questions.

5 × 1 = 5

- (i) Inductive reactance of a coil of inductance 0.2H at 50Hz is
(A) 62.8 Ω (B) 628 Ω (C) 6.28 Ω (D) 4 Ω
- (ii) If a voltage source is to be neglected then the terminals across the source will be
(A) open circuited (B) short circuited
(C) both (A) and (B) (D) none of these

CS/B.Tech/Odd/Sem-1st/ES-101/2015-16

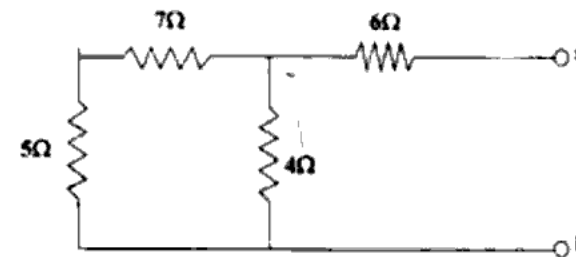- (iii) The form factor of a waveform is 1, its shape is
(A) sinusoidal (B) triangular
(C) square (D) sawtooth
- (iv) The equivalent resistance across the terminal a-b will be
(A) 9 Ω (B) 3 Ω
(C) 6 Ω (D) 2 Ω



- (v) An inductive coil with impedance $Z = (5 + j10)$, its conductance will be
(A) 0.2 Ω (B) 2 Ω
(C) 4 Ω (D) 0.4 Ω
- (vi) The bandwidth of a series resonant a. c. circuit is equal to
(A) $\frac{1}{2\pi R}$ (B) $\frac{L}{2\pi R}$
(C) $\frac{R}{2\pi L}$ (D) $\frac{1}{RLC}$
- (vii) Kirchhoff's current law is used for
(A) loop analysis (B) node analysis
(C) finding out equivalent resistance (D) none of these

CS/B.Tech/Odd/Sem-1st/ES-101/2015-16


GROUP B

(Short Answer Type Questions)

Answer any two questions.

2 × 5 = 10

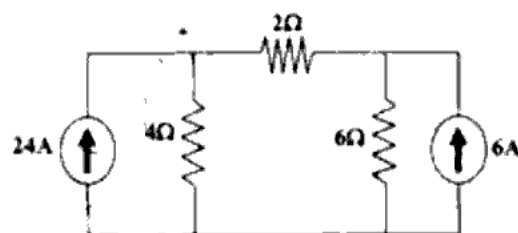2. Derive an expression for the resonant frequency of a parallel circuit, one branch consisting of a coil of inductance L in series with resistance R and the other branch of capacitance C .
3. Two coils having self inductances L_1 and L_2 and mutual inductance between them is M . Derive a mathematical expression for co-efficient of coupling k for these coils.
4. State and prove Maximum Power Transfer Theorem.
5. Applying Superposition theorem compute the current through $2\ \Omega$ resistor.



GROUP C

(Long Answer Type Questions)

Answer any two questions.

2 × 10 = 20

6. (a) A capacitor of $100\ \mu\text{F}$ is connected across a $200\ \text{V}$, $50\ \text{Hz}$ single phase supply. Calculate (i) the reactance of the capacitor, (ii) r.m.s. value of current, (iii) the maximum current.
- (b) What is meant by bandwidth? With a neat sketch of waveform find out the expression for the bandwidth of a resonant circuit.


Turn Over

1251


3

CS/B.Tech/Odd/Sem-1st/ES-101/2015-16

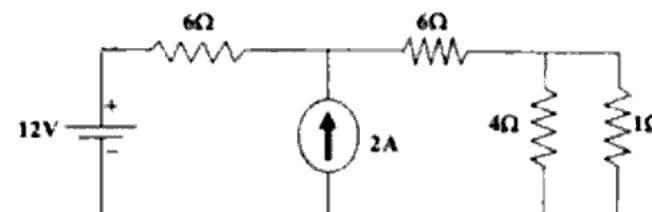7. (a) Give an example of passive element.
- (b) State and explain Thevenin's Theorem.
- (c) Find the current through $1\ \Omega$ resistor using Thevenin's Theorem.



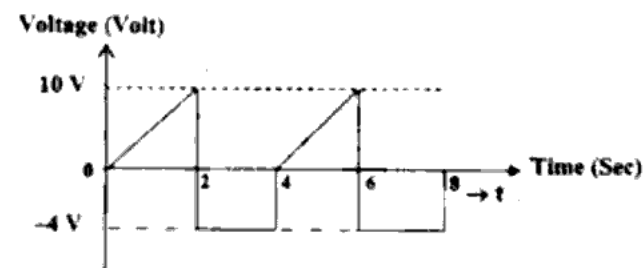8. (a) State and explain Bio-Savart's law.
- (b) What is meant by hysteresis in a magnetic circuit? Draw the B-H curve.
- (c) The coil of a moving coil instrument is wound with 50 turns of wire. The flux density in the gap is $0.06\ \text{wb/m}^2$ and the effective length of the coil side in the gap is $4\ \text{cm}$. Find the force acting on each side of the coil when the current is $40\ \text{mA}$.
9. (a) Prove that the current in purely capacitive circuit leads the applied voltage by an angle 90° and draw their waveforms. Also calculate the average power of capacitive circuit.
- (b) Find the Form Factor of the given waveform.



1251

4

CS/B.Tech/Odd/Sem-1st/ES-101/2015-16

PART – II (Electronic)

GROUP A (Multiple Choice Type Questions)

1. Answer any five questions.

5 × 1 = 5

- (i) The temperature coefficient of resistance of a pure semiconductor is-
(A) negative (B) positive
(C) constant (D) none of these
- (ii) Unit of diffusion constant for silicon in SI unit is
(A) $m^2 / V.s$ (B) m^2 / s
(C) m / s (D) V / s
- (iii) If line frequency is 60 Hz, the output frequency of a bridge rectifier is
(A) 30 Hz (B) 60 Hz
(C) 120 Hz (D) 240 Hz
- (iv) Without a DC source, a clipper acts like a
(A) rectifier (B) clamper
(C) chopper (D) demodulator
- (v) Zener diodes are used as
(A) reference voltage elements (B) reference current elements
(C) reference resistance (D) both (A) and (B)
- (vi) A transistor acts like a diode and a
(A) voltage source (B) current source
(C) power supply (D) resistance
- (vii) A BJT is a
(A) voltage controlled device (B) current controlled device
(C) power controlled device (D) none of these

CS/B.Tech/Odd/Sem-1st/ES-101/2015-16

- (viii) For an npn transistor, I_{CBO} approximately doubles for temperature rise of every

- (A) 5°C (B) 7°C
(C) 10°C (D) none of these

GROUP B

(Short Answer Type Questions)

Answer any two questions.

2 × 5 = 10

2. Define the mobility of charge carriers in a semiconductor. Obtain expressions for the electrical conductivity of (i) an intrinsic, (ii) an n-type.
3. Draw the energy band diagram of a (a) forward biased pn junction diode, (b) reverse biased pn junction diode, (c) unbiased pn junction diode.
4. A full wave bridge rectifier is fed from a 15 V r.m.s. source and is connected across a 100 ohm load. Calculate PIV, RMS current draw from the supply and average D.C. current across the load.
5. What is meant by d.c. operating point or Q point in the context of transistor characteristics? What is load line? Why is transistor biasing necessary?

GROUP C

(Long Answer Type Questions)

Answer any two questions.

2 × 10 = 20

6. (a) Write the difference between metal, insulator and semiconductor. 4
(b) Why does extrinsic semiconductor behave as good conductor? 3
(c) What do you mean by depletion region of p-n junction diode? 3

CS/B.Tech/Odd/Sem-1st/ES-101/2015-16

7. (a) What is ripple factor? Evaluate the ripple factor and efficiency of full-wave rectifier. 5
- (b) A silicon diode having internal resistance $R_F = 30 \Omega$ is used for half-wave rectification. The input ac voltage is $V_i = 6 \sin \omega t$ and load resistance is 500Ω . Find 5
- (i) dc output voltage,
 (ii) ac input power,
 (iii) the efficiency of the rectifier.
8. (a) Explain why the collector region is larger than that of the emitter and base in a transistor? 3
- (b) Why n-p-n and p-n-p transistors are called bipolar transistors? 2
- (c) Show that the collector current is given by : $I_C = \beta I_B + (1 + \beta) I_{CO}$ 5
9. Draw the common-base input characteristics of a transistor. What is early effect? Refer to the following circuit $V_{BE,sat} = 0.85 \text{ V}$ and $V_{CE,sat} = 0.22 \text{ V}$. If $h_{FE} = 110$, is the transistor operating in the saturation region? 3+2+5

