



ENGINEERING & MANAGEMENT EXAMINATIONS, DECEMBER - 2006

ELECTRONIC SYSTEM DESIGN**SEMESTER - 3**

Time : 3 Hours]

[Full Marks : 70

*The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.*

Answer Question No. 1 and any 4 questions from the rest.

1. Choose the correct answer from the given alternatives in each of the following questions : 10 × 1 = 10

a) A differentiator converts a triangular wave to

- | | |
|------------------|---------------------------|
| i) linear ramp | ii) constant D.C. voltage |
| iii) square wave | iv) sawtooth wave. |

b) A differential amplifier is used at input stage of any operational amplifier, to ensure

- | | |
|---------------------|--------------------------|
| i) high CMRR | ii) wide bandwidth |
| iii) high slew rate | iv) high open loop gain. |

c) The peak inverse voltage for full-wave rectifier is

- | | |
|------------------|--------------------|
| i) V_m | ii) $2V_m$ |
| iii) V_m / π | iv) $2V_m / \pi$. |

d) An ideal operational amplifier is

- | |
|--|
| i) voltage controlled current source |
| ii) current controlled voltage source |
| iii) current controlled current source |
| iv) voltage controlled voltage source. |



- e) A filter used after rectification in power supply is
- i) high-pass filter ii) low-pass filter
 - iii) all pass filter iv) bandpass filter.
- f) The gain required for sustained oscillation in Wien-bridge oscillator is
- i) 29 ii) 1.5
 - iii) 3 iv) none of these.
- g) A bistable multivibrator has
- i) no stable state ii) only one stable state
 - iii) two stable states iv) none of these.
- h) A linear integrator with an input of square wave provides at the output
- i) Triangular wave ii) Ramp
 - iii) Sharp pulses iv) none of these.
- i) The function of a linear voltage regulator is to
- i) minimise the change in voltage at any load condition
 - ii) reduce the ripple at the output voltage
 - iii) reduce the voltage fluctuation due to sudden change in load
 - iv) supply constant current at all load condition.
- j) A transconductance amplifier has a gain of 20 m A/V. For an input signal of 50 mV peak to peak, the peak to peak output current is
- i) 1 mA ii) 0.4 A
 - iii) 1 Amp iv) none of these.

2. a) Draw the circuit and explain the operation of a square wave generator.
- b) Draw the circuit diagram for a differential amplifier using op-amps for a voltage gain of 10. Choose the resistances accordingly.
- c) Explain the role of an instrumentation amplifier in industry with the help of suitable block diagrams.

5 + 5 + 5



CS/B.Tech(IT)/SEM-3/EC-311/06

5

3. a) Draw the simulation diagram using analog computers for the differential equation

$$\frac{d^2y}{dt^2} + 4 \frac{dy}{dt} + 8y = 3e^{-2t} \text{ for } y(0) = -1, \frac{dy}{dt}(0) = 1.$$

- b) Draw and explain the function of an Antilog converter. 10 + 5

4. a) Draw the circuit diagram of a Schmitt trigger using op-amp. Explain the role of hysteresis and indicate the parameters to adjust this property in comparator.

- b) Draw the circuit diagram for an astable multivibrator using 555 I.C. (Timer). Derive the expression for frequency of the output waveform. (4 + 3) + (3 + 5)

5. a) Draw the circuit diagram for a bandpass filter. Derive its resonant frequency and bandwidth in terms of circuit parameters.

- b) Design a circuit using single operational amplifier to provide an output

$$V_0 = -0.3 V_1 + 0.2 V_2 + 0.5 V_3$$

Where V_1, V_2, V_3 are all less than the power supply voltage. 15

6. Write short notes on any *three* of the following : 3 × 5

- a) V to F converter.
- b) Analog signal multiplier.
- c) Input and output offset voltage of op-amp.
- d) Passive filters
- e) Current mirror.

7. a) Draw the circuit diagram of a monostable multivibrator and sketch the relevant waveforms. Derive expression for the ON time.

- b) Draw the circuit diagram for a linear voltage regulator using amplifier and Zener diode. Determine the regulation in terms of the gain of the amplifier.

(5 + 3) + (5 + 2)