



Name :
Roll No. :
Invigilator's Signature :

CS/B.TECH (ECE-N)/SEM-3/EC-301/2011-12

2011

CIRCUIT THEORY & NETWORKS

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

GROUP – A


(Multiple Choice Type Questions)

1. Choose the correct alternatives for the following :

$$10 \times 1 = 10$$

- i) For N no. of nodes and B no. of branches of a graph, the rank is
- a) $N - B + 1$ b) $N + B + 1$
c) $N + 1$ d) $N - 1$.
- ii) Laplace transform analysis gives
- a) time domain response
b) frequency domain response
c) both (a) and (b)
d) none of these.

- 3104-(N)

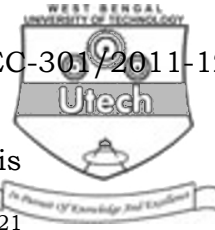

viii) Condition for reciprocity of y -parameter is

- a) $y_{11} = y_{12}$ b) $y_{12} = y_{21}$
 c) $y_{11} = y_{22}$ d) $y_{22} = y_{21}$.

ix) Initial value theorem states that

- a) $\lim_{s \rightarrow 0} F(s) = f(0)$ b) $\lim_{s \rightarrow 0} SF(s) = f(0)$
 c) $\lim_{s \rightarrow \infty} F(s) = f(0)$ d) $\lim_{s \rightarrow \infty} SF(s) = f(0)$.

x) A dc voltage V is applied to a series R-L circuit. The steady state current is

- a) $\frac{V}{R^2 + L^2}$ b) $\frac{V}{L}$
 c) 0 d) $\frac{V}{R}$.

GROUP – B

(Short Answer Type Questions)

Answer any *three* of the following.

$$3 \times 5 = 15$$

2. Explain under what condition, an RC circuit behaves as
 a) integrator b) differentiator.
3. State and prove maximum power transfer theorem.
4. A shifted unit step function is expressed as $f(t) = u(t - a)$.
 Obtain its Laplace Transform.



5. For a two port network, show that $AD - BC = 1$.
6. Draw the oriented graph of the network in the following figure (Fig. 1) and find the complete incidence matrix.

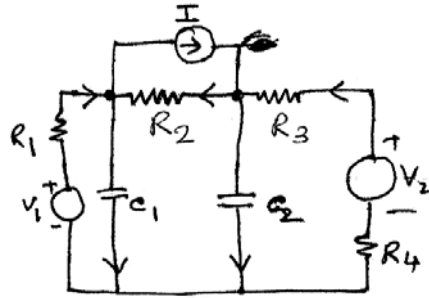


Fig. 1

GROUP - C

(Long Answer Type Questions)

Answer any *three* of the following. $3 \times 15 = 45$

7. a) Explain series and parallel resonance with necessary circuits.
- b) Show that for an RLC series circuit the resonance frequency $\omega_r = \sqrt{\omega_1 \omega_2}$, where ω_1 and ω_2 are the half power frequencies.
- c) A coil is at resonance at 10 kHz with a capacitor. If the resistance and inductance of the coil are 200Ω and 5 H, find Q-factor of the coil. $5 + 5 + 5$
8. a) Find the total inductance of the three series connected coupled circuits. (Fig. 2)


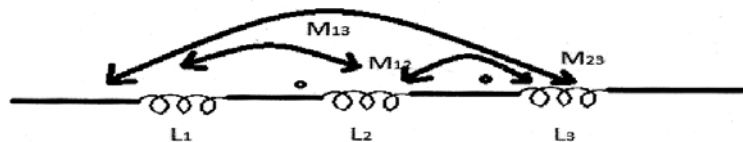


Fig 2

Given, $L_1 = 1 \text{ H}$; $L_2 = 2 \text{ H}$; $L_3 = 5 \text{ H}$

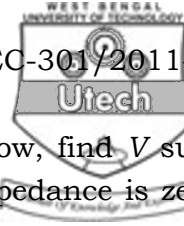$M_{12} = 0.5 \text{ H}$; $M_{23} = 1 \text{ H}$, $M_{13} = 1 \text{ H}$



- b) In the network shown in the Fig. 3 below, find V such that the current through $(3 + j 4) \Omega$ impedance is zero. Use node voltage analysis.

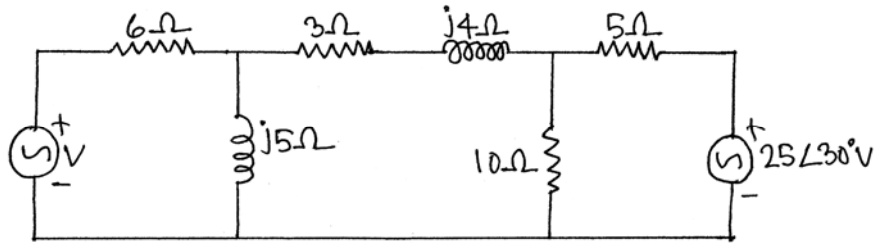


Fig. 3

- c) Find the current through R_L in the circuit shown in Fig. 4 below using Norton's theorem.

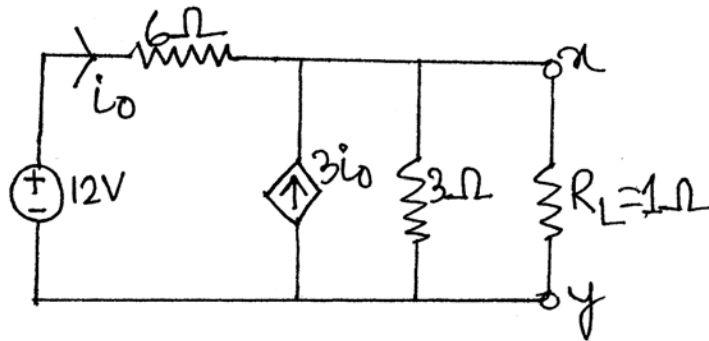


Fig. 4

5 + 5 + 5

9. a) Why are h -parameters called hybrid parameters ? Find the h -parameters from the two port network given in Fig. 5. Is the network reciprocal or symmetric ? Justify.


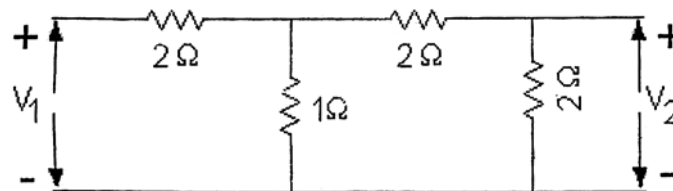


Fig. 5

5

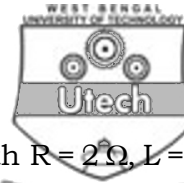

- b) For an RL series circuit shown below with $R = 2\Omega$, $L = 1H$ and no initial current in the inductor, a voltage $V = 4e^{-t}V$ is applied at $t = 0$. Find expression for the resulting current in the circuit for $t \geq 0$ using Laplace transform method. (Fig. 6)

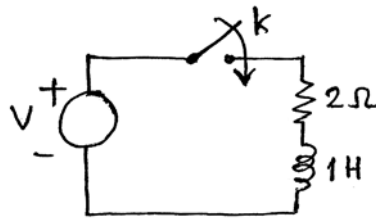


Fig. 6

- c) Find the inverse Laplace transform of the function

$$V(S) = \frac{10(S+4)}{S(S+3)(S+1)^2} \quad 5 + 5 + 5$$

10. a) State and explain superposition theorem.
b) Find the net current flowing through 10 ohm resistor applying superposition theorem. (Fig. 7)

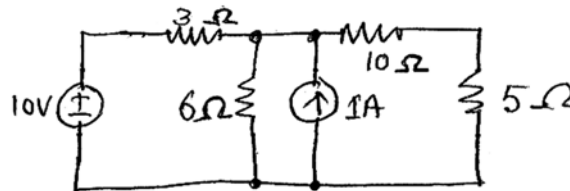


Fig. 7

- c) Find the equivalent delta connection of the given network (Fig. 8)

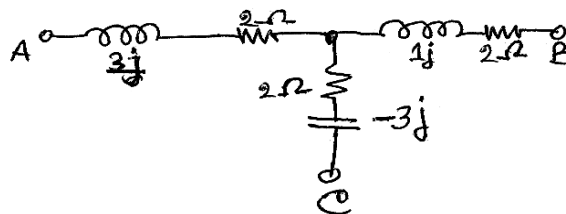


Fig. 8

5 + 5 + 5



11. Write short notes on any *three* of the following : 3×5

- a) Driving point impedance
 - b) Compensation theorem
 - c) Concept of complex frequency
 - d) Initial value theorem and final value theorem
 - e) Phasor diagrams.
-