

Name :

Roll No. :

Invigilator's Signature :

CS/B.Tech/(EE/ECE/PWE/EEE/CSE/IT/BME/ICE)/SEM-3/EE-301/2010-11

2010-11

CIRCUIT THEORY & NETWORKS

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.***GROUP - A****(Multiple Choice Type Questions)**

1. Choose the correct alternatives for any
- ten*
- of the following :

10 × 1 = 10

- i) The Laplace transform of a shifted unit step
- $f(t) = U(t - a)$
- is

- | | |
|---------------|---------------------|
| a) e^{-as} | b) $e^{-as/s}$ |
| c) se^{-as} | d) $s(1 - e^{-as})$ |

- ii) A tie-set matrix has 3 rows and 7 branches. The number of twigs is

- | | |
|------|-------|
| a) 3 | b) 5 |
| c) 2 | d) 4. |

- iii) Unit step function is first derivative of


- | | |
|------------------|------------------------|
| a) Ramp function | b) Impulse function |
| c) Gate function | d) Parabolic function. |

CS/B.Tech/(EE/ECE/PWE/EEE/CSE/IT/BME/ICE)/SEM-3/EE-301/2010-11

iv) A circuit having neither an e.m.f. source nor any energy source is


- a) active circuit b) passive circuit
c) unilateral circuit d) bilateral circuit.

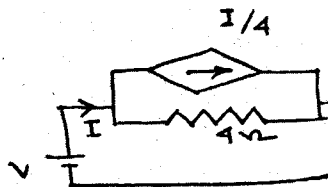v) In the network shown in the figure, the effective resistance faced by the voltage source is



- a) 4Ω b) 3Ω
c) 2Ω d) 1Ω .

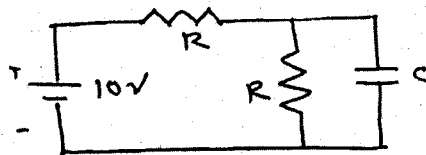
vi) The time constant of the network shown in the figure is



- a) $2RC$ b) $3RC$
c) $\frac{RC}{2}$ d) $\frac{2RC}{3}$.

CS/B.Tech/(EE/ECE/PWE/EEE/CSE/IT/BME/ICE)/SEM-3/EE-301/2010-11

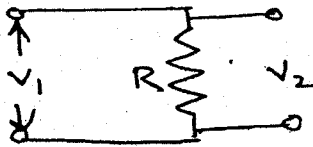vii) The Z parameter of the following network is



a) $\begin{bmatrix} R & R \\ R & R \end{bmatrix}$

b) $\begin{bmatrix} R & 0 \\ 0 & R \end{bmatrix}$

c) $\begin{bmatrix} R & -R \\ -R & R \end{bmatrix}$

d) Cannot be determined.

viii) Two equal impedances $10\angle 60^\circ$ are connected in parallel.

The equivalent impedance will be

a) $20\angle 60^\circ$

b) $10\angle 120^\circ$

c) $15\angle 120^\circ$

d) $5\angle 60^\circ$

ix) A series resonant circuit at resonance is called

a) an acceptor circuit

b) a rejector circuit

c) an oscillator circuit

d) a damped circuit.

x) The average power delivered to a reactive load is

a) zero

b) $VI \sin \phi$

c) $v(t) + i(t)$

d) $\frac{1}{2} V_m I_m \sin \phi$

CS/B.Tech/(EE/ECE/PWE/EEE/CSE/IT/BME/ICE)/SEM-3/EE-301/2010-11

xi) The output Y and input X of a system are related by the equation $Y = mX + c$, where m, c are constants. The system is

- a) linear
- b) non-linear
- c) bilateral
- d) unilateral.

xii) The Fourier transform can be used to represent

- a) any signal
- b) all periodic signals
- c) all non-periodic signals
- d) all periodic signals that obey Dirichlet's condition.


GROUP - B

(Short Answer Type Questions)

Answer any *three* of the following.


$3 \times 5 = 15$

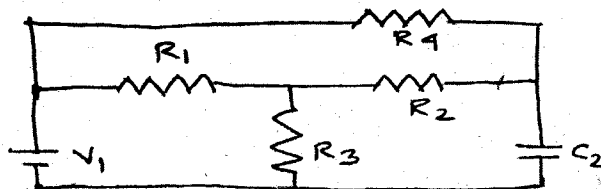2. Draw the oriented graph of the figure shown and find the incidence matrix.




CS/B.Tech/(EE/ECE/PWE/EEE/CSE/IT/BME/ICE)/SEM-3/EE-301/2010-11

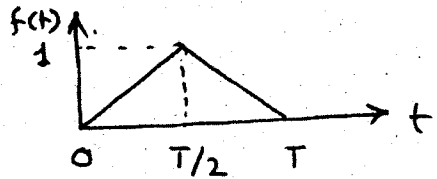
3. Find the Laplace transform of the triangular waveform shown.



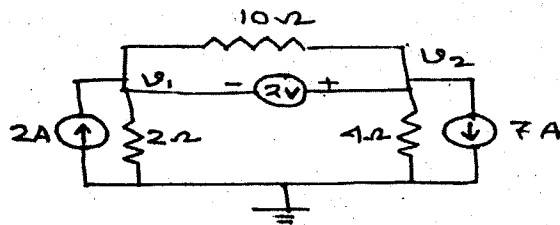4. For the circuit shown below, find the node voltages.



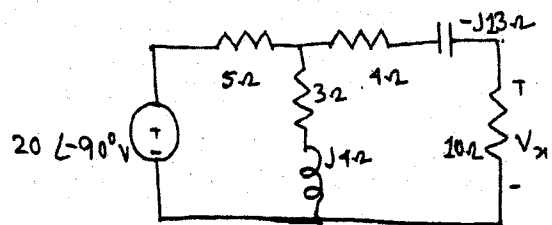5. Compute V_x in the circuit shown below using the method of source transformation.




6. Find the rms value of the periodic current ;

$$i(t) = 8 + 30 \cos 2t - 20 \sin 2t + 15 \cos 4t - 10 \sin 4t \text{ A.}$$


CS/B.Tech/(EE/ECE/PWE/EEE/CSE/IT/BME/ICE)/SEM-3/EE-301/2010-11

GROUP - C**(Long Answer Type Questions)**Answer any three of the following. $3 \times 15 = 45$

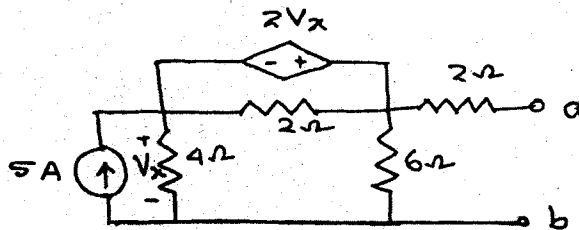
7. a) Find the Thevenin equivalent of circuit shown below :



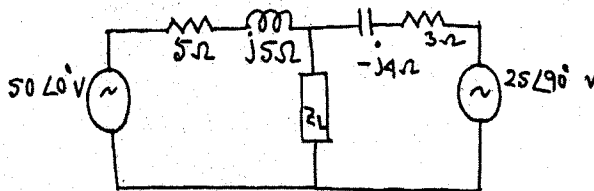- b) Find the load impedance Z_L to transfer maximum power in the circuit shown. Find also the value of power consumed by the load. $7 + 8$




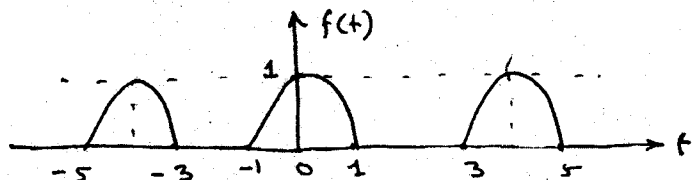8. a) Determine the Fourier series for the half wave rectified cosine function shown.




CS/B.Tech/(EE/ECE/PWE/EEE/CSE/IT/BME/ICE)/SEM-3/EE-301/2010-11

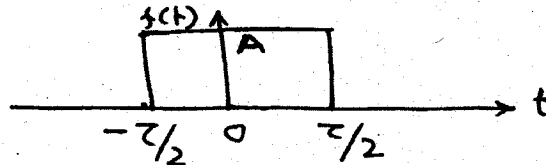
- b) Derive the Fourier transform of a single rectangular pulse of width τ and height A shown below : 10 + 5



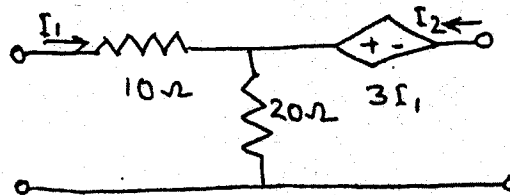
9. a) Find the transmission parameters for the two-part network shown below :



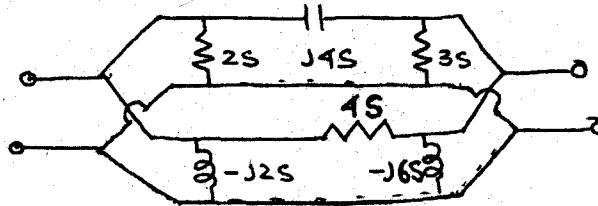- b) Find the Y parameters of the two-part network shown below : 8 + 7




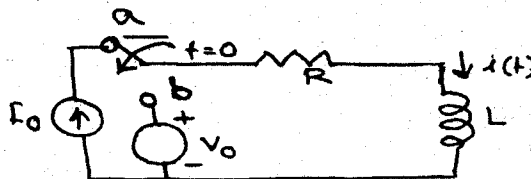10. a) In the circuit shown below, the switch moves from position a to position b at $t = 0$. Find $i(t)$ for $t > 0$.



CS/B.Tech/(EE/ECE/PWE/EEE/CSE/IT/BME/ICE)/SEM-3/EE-301/2010-11

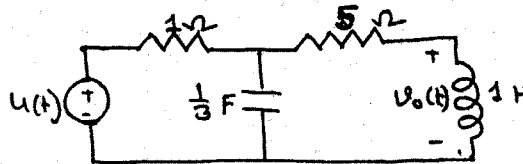- b) Find $v_o(t)$ in the circuit shown below. Assume zero initial condition. 8 + 7



11. a) Draw the circuit diagram of a first order highpass filter & find out the expression of the cut-off frequency.
- b) What do you mean by wide bandpass and narrow band-pass filters ? Draw the circuit diagram for the two types of filters.
- c) Find the cut-off frequency of the following lowpass second order active filter shown below. 5 + 5 + 5

