



**MAULANA ABUL KALAM AZAD UNIVERSITY OF  
TECHNOLOGY, WEST BENGAL**

**Paper Code : EE-301**

**ELECTRIC CIRCUIT THEORY**

Time Allotted: 3 Hours

Full Marks: 70

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words  
as far as practicable.*

<http://www.makaut.com>

**Group – A**

**(Multiple Choice Type Questions)**

1. Choose the correct alternatives for any ten of the following:

1×10=10

(i) When compared to a first-order low pass filter, a second-order low pass filter has

(a) low voltage gain

(b) higher voltage gain

(c) faster drop in filter response

(d) higher cut-off frequency

(ii)  $F(s) = (1 - e^{-Ts})/s$  is the Laplace transform of <http://www.makaut.com>


(a) a pulse of width T

(b) a square wave of period T

(c) a unit step delayed by T

(d) a ramp delayed by T

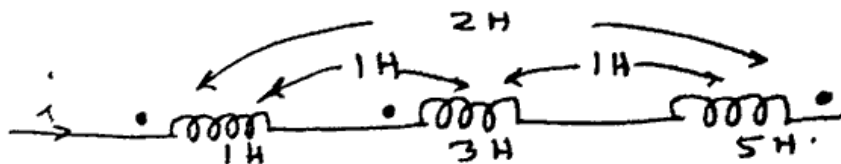(iii) The total inductance of the three series connected coupled coils is



<http://www.makaut.com>

(a) 6 H

(b) 5 H


(c) 7 H

(d) 8 H

(iv) The output  $Y$  and input  $X$  of a system are related by the equation  $Y = mX + c$ , where  $c$  is a constant. The system is

- (a) linear (b) non-linear  
(c) bilateral (d) unilateral

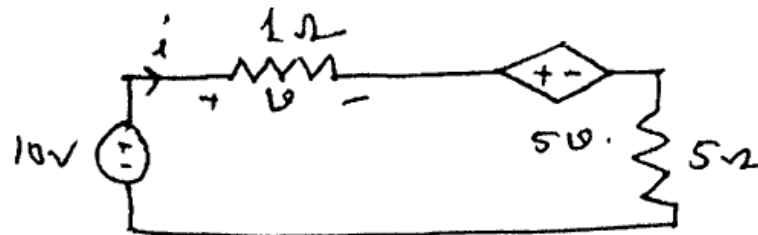(v) The current ' $i$ ' in the circuit shown is given by



- (a) 10 A (b) 5 A  
(c) 2 A (d) 20 A



(vi) When a unit impulse voltage is applied to an inductor of  $1H$ , the energy supplied by the source is

- (a)  $\propto J$  (b)  $1 J$   
(c)  $\frac{1}{2} J$  (d)  $0 J$

(vii) An initially relaxed  $RC$  series circuit with  $R = 2M\Omega$  and  $C = 1\mu F$  is switched to a  $10V$  step input. The voltage across the capacitor after 2 seconds will be <http://www.makaut.com>

- (a)  $0V$  (b)  $3.68V$   
(c)  $6.32V$  (d)  $10V$

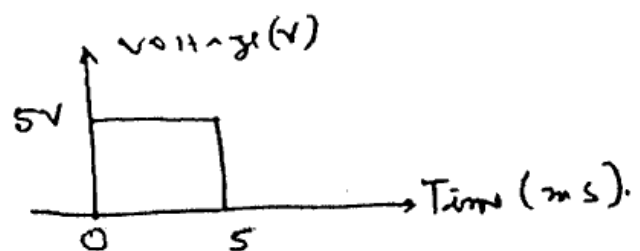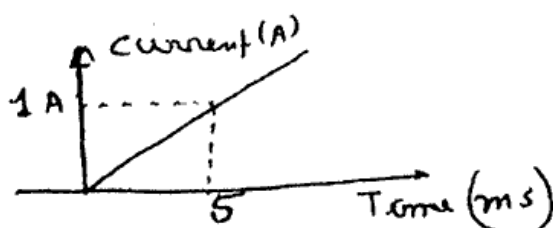(viii) The current and voltage profile of a circuit element vs time is shown in the figure. The element is



- (a) inductor (b) capacitor  
(c) resistor (d) transistor





(ix) The  $V$ - $S$  characteristic of a resistor is  $i = 2v^2$ . The resistor is <http://www.makaut.com>

- (a) linear, passive, bilateral (b) nonlinear, active, bilateral  
(c) nonlinear, passive, bilateral (d) nonlinear, active, unilateral

(x) For a connected planar graph of  $v$  vertices and  $e$  edges, the number of meshes is

- (a)  $e - v + 1$  (b)  $e + v + 1$   
(c)  $e + v - 1$  (d)  $e - v - 1$

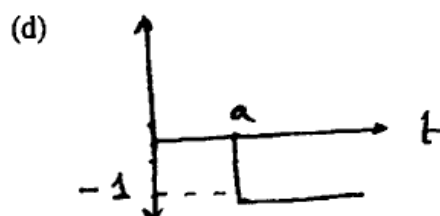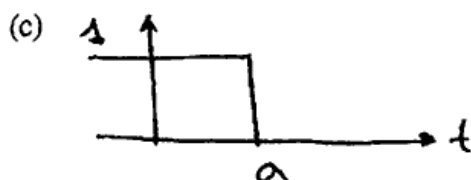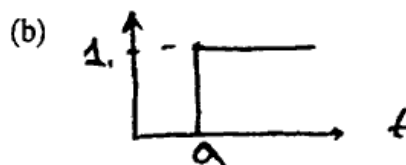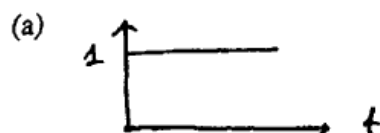(xi) The graphical representation of  $u(a - t)$  is given by <http://www.makaut.com>



(xii) At steady state condition, the inductor and capacitor will behave as respectively

- (a) short circuit, open circuit (b) open circuit, short circuit  
(c) both open circuit <http://www.makaut.com> (d) both short circuit


### Group - B

#### (Short Answer Type Questions)


Answer any three of the following.

5×3=15

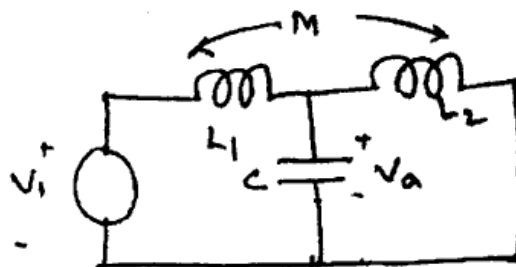
2. In the circuit shown below,  $V_1(t) = 2 \cos t$ ,  $C = 1F$ ,  $L_1 = L_2 = 1H$  and  $M = \frac{1}{4}H$ . Find the voltage  $V_a(t)$ .



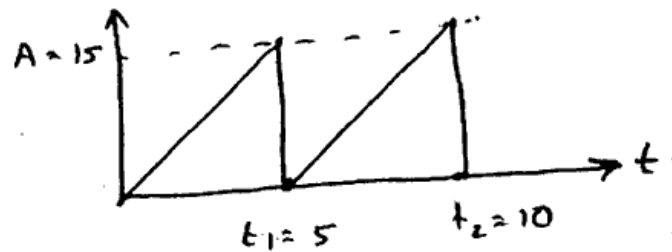3. Find the Laplace transform of the following waveform. <http://www.makaut.com>




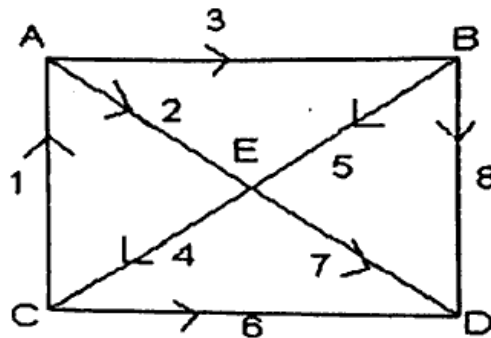4. Consider the circuit shown in the figure. Draw the corresponding graph. Find the complete incidence matrix and the reduced incidence matrix. Find the possible no. of trees. <http://www.makaut.com>



5. Draw the circuit of a second order low pass filter and calculate its cut off frequency for  $R = 34 \text{ k}\Omega$  and  $C = 0.0047 \mu\text{F}$ . <http://www.makaut.com>

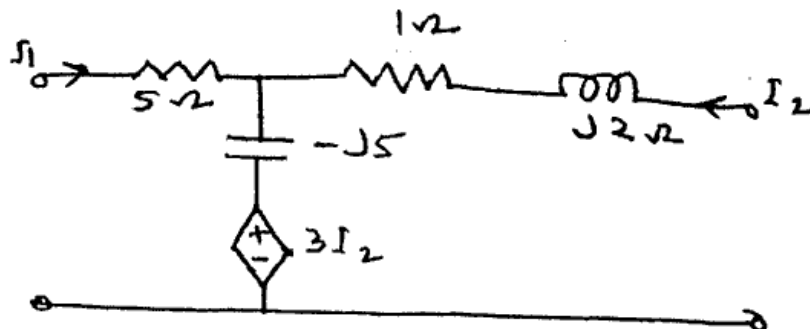6. Find the Z-parameters of the circuit given below.




Group - C

(Long Answer Type Questions)


Answer any three of the following.

15/3=45

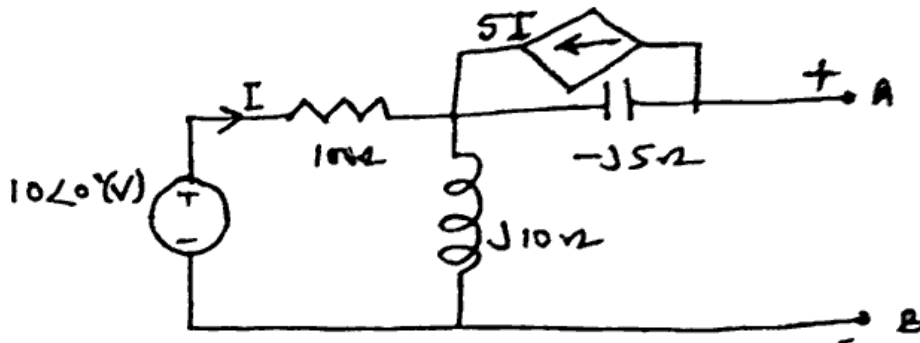
7. (a) Compute Thevenin equivalent of the network shown: <http://www.makaut.com>



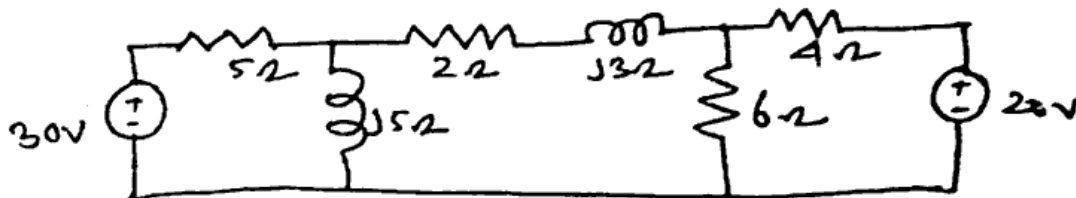- (b) Using superposition theorem, calculate the current through the  $(2 + j3)$  ohm impedance of the circuit shown: <http://www.makaut.com>



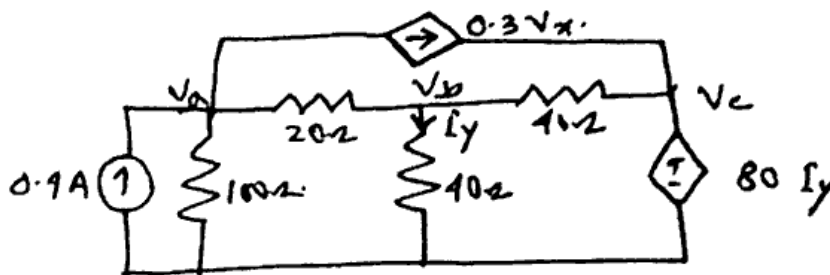
- (c) Use Nodal analysis method to find the voltages  $V_a$ ,  $V_b$ , and  $V_x$  in the circuit shown.




<http://www.makaut.com>

5+5+5=15

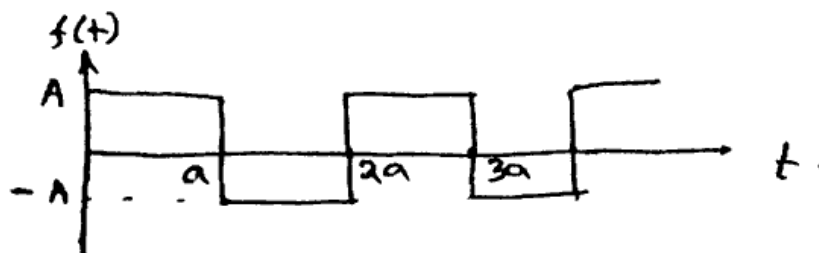8. (a) Find the Laplace transform of the square wave shown below:




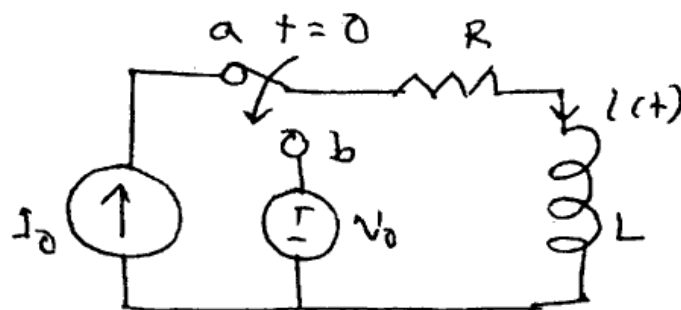- (b) In the circuit shown below, the switch moves from position 'a' to position 'b' at  $t = 0$ . Find  $i(t)$  for time  $t > 0$ . <http://www.makaut.com>




- (c) Mention differences between the Laplace transform and the Fourier transform. What are the application of these transforms. <http://www.makaut.com> 5+5+5=15

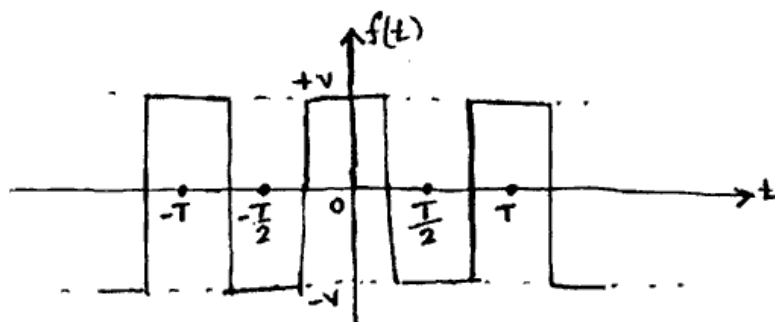9. (a) Write down the conditions which a periodic function must satisfy to have its Fourier series expansion.
- (b) Write down the trigonometric form of the Fourier series for a function  $f(t)$  and evaluate various Fourier Coefficients.
- (c) Determine the Fourier series for the square waveform shown in the figure and plot the magnitude and phase spectra. <http://www.makaut.com> 2+5+8=15



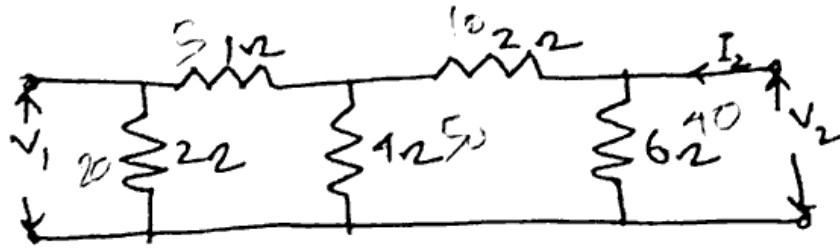10. (a) Find the Y parameter of the network shown:




- (b) Deduce the conditions for symmetry for the hybrid parameters of 2 port network.

- (c) What are AB < D parameters? Prove that  $AD - BC = 1$ . <http://www.makaut.com>

5+5+5=15

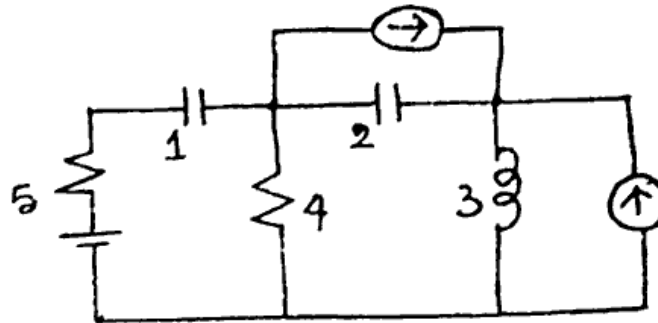11. (a) Define incidence matrix. For the network shown in figure, construct the complete incidence matrix.



- (b) For the same network shown in figure, determine all the tree and co-tree. Then considering the tree formed by branches 1, 2, 5 construct cut-set matrix and tie-set matrix.

(1+4)+10=15

<http://www.makaut.com>