

CS/B.Tech/Even/4th Sem/ECE/EC-402/2014

2014**Digital Electronic & Integrated Circuits****Time Alloted : 3 Hours****Full Marks : 70***The figure in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable***GROUP - A****(Multiple Choice Type Questions)**

1. Choose the correct alternatives for any ten of the following
10x1=10
- i) Gray code of $(110101)_2$ is
a) 101111 b) 100110 c) 111010 d) 101011
 - ii) If $(211)_x = (152)_8$, then the value of base x is
a) 6 b) 5 c) 7 d) 9
 - iii) Minimum number of 2-input NOR gates are required to design a 2-input NAND gate is
a) 1 b) 2 c) 3 d) 4
 - iv) Which of the following expressions is in the sum-of-products (SOP) form?
a) $(A+B)(C+D)$ b) $(A)B(CD)$
c) $AB(CD)$ d) $AB + CD$
 - v) In fig.- 1 the input condition, needed to produce $X = 1$, is

 


Fig.-1

- a) $A = 1, B = 1, C = 0$ b) $A = 1, B = 1, C = 1$
 c) $A = 0, B = 1, C = 1$ d) $A = 1, B = 0, C = 0$
- vi) The minimization of logic expression is done in order to
 a) reduces pace b) reduce cost
 c) reduce number of gates d) all
- vii) The number of 2 line to 4 line decoders are used to design a 4 line to 16 line decoder is
 a) 2 b) 4 c) 5 d) 6
- viii) The final carry output equation of carry-look-ahead addition is
 a) $C_{n+1} = P_n C_n + G_n$ b) $C_{n+1} = P_n + C_n G_n$
 c) $C_n = P_n + C_n G_n$ d) $C_n = P_n C_n + G_n$
- ix) Multichannel signals can be transmitted through a single channel by using
 a) demultiplexer b) encoder
 c) decoder d) multiplexer
- x) The initial output of S-R Flipflop Q is 0. It changes to 1, when a clock pulse is applied. The input S and R will be-
 a) $S=1, R=1$ b) $S=0, R=0$ c) $S=0, R=1$ d) $S=1, R=0$
- xi) A Mod -2 counter, followed by a Mod -5 counter is
 a) Decade counter b) Mod-9 counter
 c) Mod-11 counter d) Mod-7 counter
- xii) The Moore machine is defined by the following equations:
 a) Next state = F (Present state, Inputs) and Outputs = G (Present State)
 b) Next state=F(Inputs) and Outputs=G(Present State)

CS/B.Tech/Even/4th Sem/ECE/EC-402/2014

- c) Next state=F(Present state) and Outputs=G(Present State)
 d) Next state=F(Present state) and Outputs=G(Inputs)

GROUP - B**(Short Answer Type Questions)**Answer any *three* of the following

3x5=15

2. Convert J-K f/f to S-R f/f. (5)
3. Design a 16:1 multiplexer using 4:1 multiplexers only. (5)
4. Write down the excitation table of SR and T flip-flop and derive the characteristic equation for these two flip-flops. (2 + 3)
5. Design a bi-directional shift registers and explains its operation. (5)
6. Implement the BCD to Excess-3 code conversion using ROM. (5)
7. Design a full subtractor using two half-subtractors and OR gate. (5)

GROUP - C**(Long Answer Type Questions)**Answer any *three* of the following.

3x5=15

8. a) What is the main difference between a latch and a flip-flop?
 b) What is the race around condition? How can we overcome the race around condition?
 c) Design Mod-6 Synchronous counter using JK flip-flops and other gates. (3 + (2 + 3) + 7)
9. a) Consider a chemical mixing tank for which there are 3 variables of interest: liquid level, pressure and temperature. The alarm will be triggered under the following conditions:
 i) Low level with high pressure
 ii) High level with low pressure

CS/B.Tech/Even/4th Sem/ECE/EC-402/2014

- iii) High level with low temperature and high pressure.
Design the system, implement using only NOR gates.

b) Simplify using k-map in SOP form:

$$F = \sum m(1, 3, 4, 5, 9, 11, 14, 15) + \sum d(2, 6, 7, 8)$$

(10+5)

10. For Synchronous counter with sequence $2 \rightarrow 6 \rightarrow 5 \rightarrow 3 \rightarrow 1 \rightarrow 0 \rightarrow 2$

- Give present state/next state table.
- Write state transition table using D flip-flops.
- Simplify and realize the circuit. Draw the state diagram.
- Justify whether the design counter will go in lockout condition or not.
- What should be the corrective design process to avoid the lockout condition?

(2+3+6+2+2)

11. What is the difference between synchronous counter and asynchronous counter? Realize a 4-bit Ring counter using JK flip flops. Develop the state table. Can this circuit be used to realize a frequency divider?

(5+8+2)

12. a) Define the resolution of a DAC. A 6-bit DAC has a step size of 50 mV. Determine the full scale output voltage and resolution.

b) Describe the working principle of 4-bit R-2R ladder circuit.

c) For a R-2R ladder 4-bit DAC converter with $R=10K\Omega$ and $V_R=10V$, find out the feedback resistance R_f of the OP-AMP for

- First LSB input at the output will be 0.1 V.
- Analog output of 6 V for a binary input of 1000.
- Full scale output voltage of 12 V.
- The actual maximum output Voltage of 10 V.

(2+3)+5+5

13. Write short notes on any three of the following:

(3x5=15)

- Venn diagram
- A 3-bit magnitude comparator
- Glitch and Spike
- Successive approximation ADC
- Draw the NAND, NOR, NOT gates using CMOS

———— • ————