



Name :

Roll No. :

Invigilator's Signature :

CS/B.TECH/EE(N) /EEE(N)/PWE(N)/ICE(N)/SEM-3/EE-301/2012-13

2012

ELECTRIC CIRCUIT THEORY

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.


GROUP – A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *ten* of the following :

$$10 \times 1 = 10$$

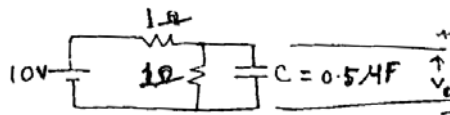- i) The internal impedance of an ideal voltage source should be
 - a) zero
 - b) infinite
 - c) greater than zero but less than infinity
 - d) none of these.
- ii) The steady state voltage V_c in this given figure is



- a) 10 V
- b) 15 V
- c) 5 V
- d) none of these.

3106(N)

[Turn over

CS/B.TECH/EE(N) /EEE(N)/PWE(N)/ICE(N)/SEM-3/EE-301/2012-13



iii) What is the condition for reciprocity in term of h parameters ?

- a) $h_{11} = h_{22}$ b) $h_{21}h_{12} = h_{11}h_{22}$
 c) $h_{12} \text{ \& } h_{21} = 0$ d) $h_{12} = h_{21}$.


iv) An ideal filter should have

- a) zero attenuation in the pass band
 b) zero attenuation in the attention band
 c) infinite attenuation in the pass band
 d) none of these.

v) The number of links of a graph having n nodes and b branches are

- a) $b - n + 1$ b) $n - b + 1$
 c) $b + n - 1$ d) $b + n$.

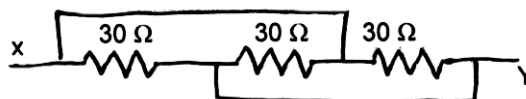vi) The equivalent resistance between x & y of the figure shown below is



- a) 30Ω b) 50Ω
 c) 60Ω d) 10Ω .





vii) A Periodic Waveform having halfwave symmetry has no

- a) odd harmonics b) even harmonics
 c) cosine terms d) sine terms.

CS/B.TECH/EE(N) /EEE(N)/PWE(N)/ICE(N)/SEM-3/EE-301/2012-13



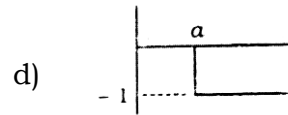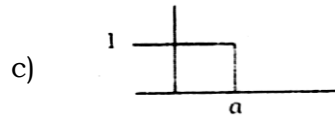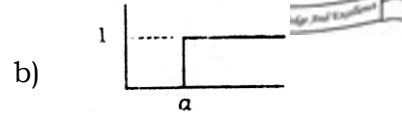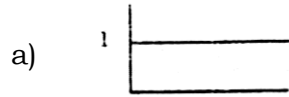viii) Graphical representation of $u(a - t)$ is



ix) A tie-set matrix has 3 rows and 7 branches. The number of twigs is

- a) 3 b) 5
c) 2 d) 4.

x) Inverse Laplace of $F(s) = \frac{2}{s(s+1)}$ is

- a) $2 + e^{-2t}$ b) $1 + 2e^{-t}$
c) $2 + 2e^{-t}$ d) $2 - 2e^{-t}$.

xi) Two networks can be dual when


- their nodal equations are same
- the loop equations of one network are the nodal equations of the other
- their loop equations are same
- none of these.

xii) The *dc* gain of a system having the transfer function


$$H(s) = \frac{12}{(s+2)(s+3)}$$

- a) 2 b) 1
c) 12 d) 3
e) 0.


CS/B.TECH/EE(N) /EEE(N)/PWE(N)/ICE(N)/SEM-3/EE-301/2012-13

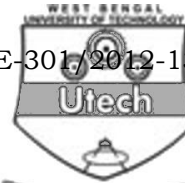**GROUP – B****(Short Answer Type Questions)**Answer any *three* of the following $3 \times 5 = 15$

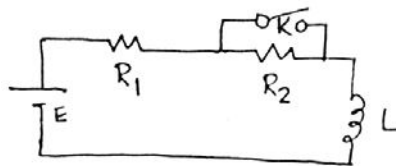
2. In the figure given below the battery voltage is applied for a steady state period. Obtain the q complete expression for the current for the current after closing the switch K . Assume $R_1 = 1\Omega$, $R_2 = 2\Omega$, $L = 1H$, $E = 10V$.



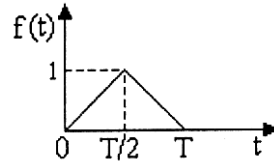3. Find the Laplace transform of the triangular waveform shown in the figure :



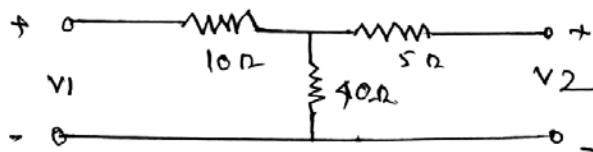4. Find the y -parameters for the following networks shown in the figure :



5. Define incident matrix of a graph and draw the orientation graph from the reduced incident matrix.

$$[A] = \begin{bmatrix} 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$


3106(N)

4

CS/B.TECH/EE(N) /EEE(N)/PWE(N)/ICE(N)/SEM-3/EE-301/2012-13



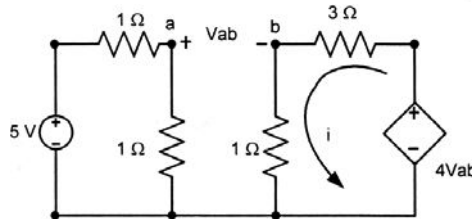6. For the circuit shown in the figure, find the value of the current i .




7. Explain under what condition, a RC series circuit behaves as
- Low-pass filter
 - Integrator.

GROUP – C

(Long Answer Type Questions)


Answer any *three* of the following. $3 \times 15 = 45$

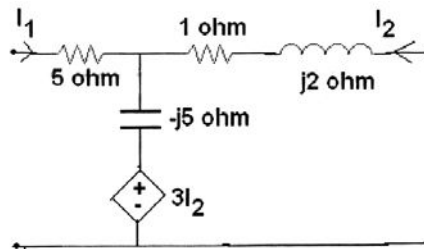8. a) Find the Z-parameter and ABCD parameter of the circuit given below in the figure.




- Express h -parameter in terms of Y-parameter of a two port network.
 - What is the cascade connection between two 2-port networks ? Explain with diagram. $7 + 4 + 4$
9. a) Draw the circuit diagram of a first order high pass filter and find out the expression for the cut-off frequency.
- Draw and explain the characteristics of an ideal band-pass and an ideal band-stop filter.

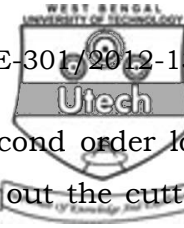CS/B.TECH/EE(N) /EEE(N)/PWE(N)/ICE(N)/SEM-3/EE-301/2012-13



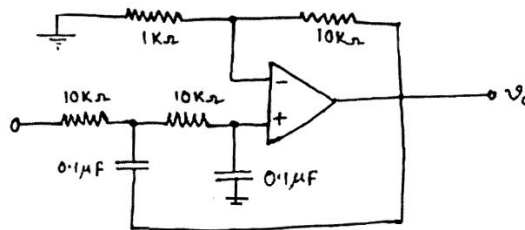- c) The circuit shown in the figure is a second order low-pass filter. Analyze the circuit and find out the cut-off frequency.




5 + 5 + 5


10. a) Find the inverse Laplace of $F(s)$.

$$F(s) = \frac{s+1}{s(s^2+4s+4)}$$

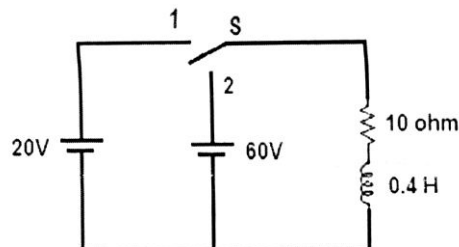- b) The circuit in the figure was in steady state with switch in position 1. Find current $i(t)$ for $t > 0$ if the switch is moved from position 1 to 2 at $t = 0$.



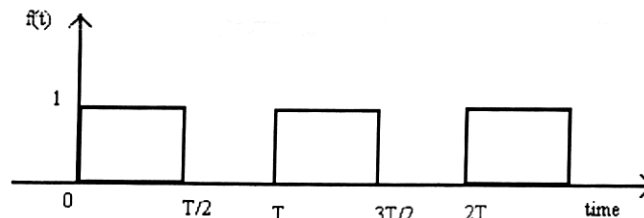- c) Determine the Laplace transform of the periodic square pulse train of amplitude as shown in the figure.




3106(N)

6

CS/B.TECH/EE(N) /EEE(N)/PWE(N)/ICE(N)/SEM-3/EE-301/2012-13



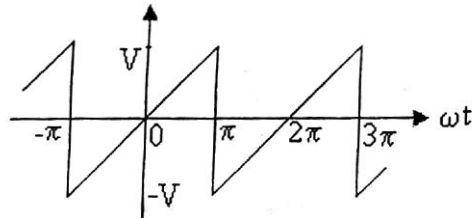11. a) Find the Fourier expansion of the following waveform shown in figure.




- b) Determine the Fourier transform and sketch the amplitude and phase spectrums of the function

$$f(t) = Ve^{-t/a} \text{ for } t \geq 0$$

$$= 0 \text{ for } t \leq 0$$

$$8 + 7$$

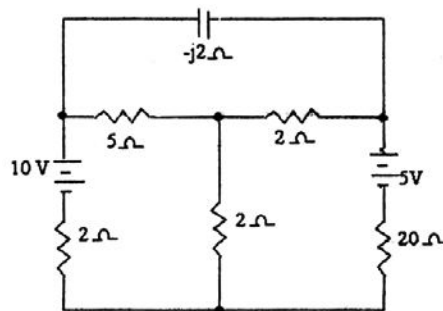12. a) What is oriented graph of a network ? Explain with a suitable example.
- b) Develop at least three trees for your considered network. Mark the twigs and links.
- c) For the network in figure, draw the oriented graph, develop the incidence matrix, choose a tree and considering the tree develop the tie-set matrix.



=====