



**MAULANA ABUL KALAM AZAD UNIVERSITY OF
TECHNOLOGY, WEST BENGAL**

**Paper Code : EE-301
ELECTRIC CIRCUIT THEORY**

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.


GROUP - A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any ten of the following : 10 × 1 = 10
 - i) A tie-set matrix has 3 rows and 7 branches. The number of twigs is
 - a) 3
 - b) 5
 - c) 2
 - ☒ d) 4.
 - ii) If a function is shifted by T , then it is correctly represented as
 - a) $f(t - T) u(t)$
 - ☒ b) $f(t - T) u(t - T)$
 - c) $f(t) u(t - T)$
 - d) $(t - T) f(t - T)$
 - iii) If all the elements in a particular network are linear, then the superposition theorem would hold, when the excitation is
 - ☒ a) DC only
 - b) AC only
 - c) either AC or DC
 - d) an Impulse.

CS/B.TECH/EE/EEE/PWE/ICE/ODD/SEM-3/EE-301/-

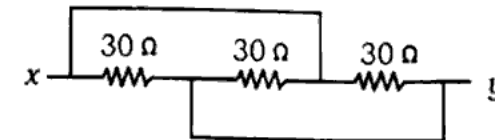- iv) In balanced bridge, if the positions of detector and source are interchanged, the bridge will still remain balanced. This can be explained from which theorem ?
 - ☒ a) Reciprocity theorem
 - b) Thevenin's theorem
 - c) Norton's theorem
 - d) Compensation theorem.
- v) When we use super node technique
 - a) Current source branch is common for two meshes
 - b) Ideal voltage source is connected between two non-reference nodes
 - c) Ideal voltage source is connected between non-reference node and reference
 - d) All of these.
- vi) The number of links of a graph having n nodes and b branches are
 - ☒ a) $b - n + 1$
 - b) $b + n - 1$
 - c) $n - b + 1$
 - d) $b + n$.
- vii) The equivalent resistance between x & y of the figure shown below is




- a) 30 ohm
 - b) 50 ohm
 - c) 60 ohm
 - ☒ d) 10 ohm.
- viii) A network with 5 independent loops and 7 nodes will have number of branches in the network
- a) 10
 - b) 7
 - c) 4
 - ☒ d) none of these.

- ix) A current in a circuit is given by,
 $I(s) = \frac{2s+8}{s^2+4s+12}$. If the current flows through a 5Ω resistor, power dissipated at $t = 0$ is
- a) 20 watt b) 15 watt
 c) 40 watt d) 10 watt.

- x) A network is linear if
- a) Response proportional to excitation function
 b) Principle of superposition applies
 c) Principle of homogeneity applies
 d) Both (b) and (c).

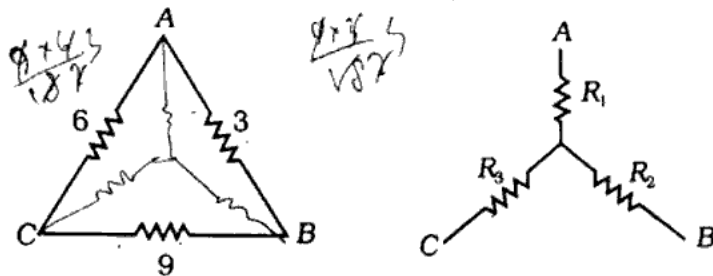- xi) The resistances R_1 , R_2 and R_3 are respectively



- a) 1, 3/2 & 3 b) 3, 3/2 & 3
 c) 9, 3 & 1 d) 2, 1 & 9.

- xii) If poles and zeros are arranged alternatively on imaginary axis, then type of network is

- a) LC network b) RC network
 c) RL network d) Any of these.

GROUP - B

(Short Answer Type Questions)

Answer any three of the following. $3 \times 5 = 15$

2. Find v_x using source transformation technique in the given Fig. 1.

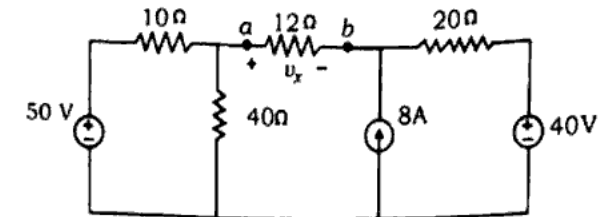


Fig.-1.

3. Apply superposition principle to find v_o and in the Fig. 2.

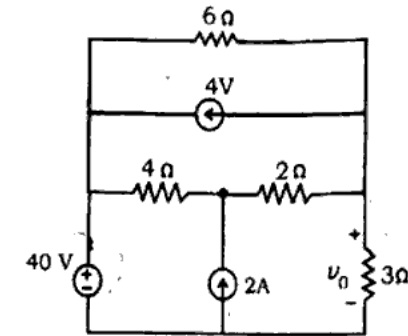


Fig.-2.

4. Find the incidence matrix of the given network in Fig. 3.

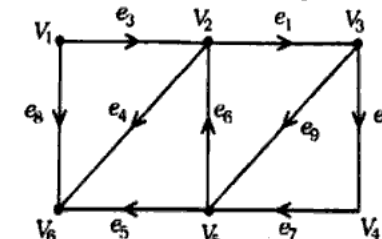


Fig.-3.

5. Find Norton equivalent circuit across a & b terminals from the Fig. 4.

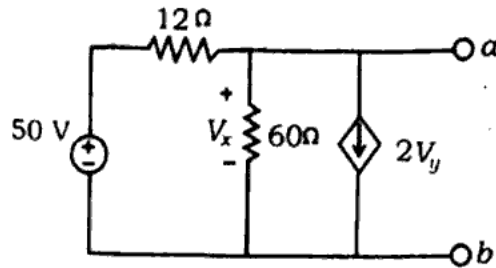


Fig.-4.

6. Find the Laplace transform of the periodic function in Fig. 5.

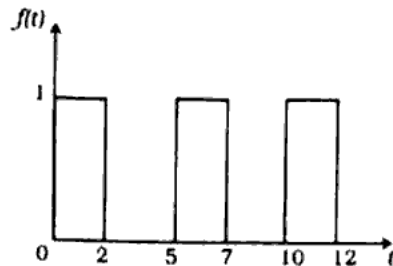


Fig.-5

GROUP - C

(Long Answer Type Questions)

Answer any three of the following. $3 \times 15 = 45$

7. a) Find Thevenin equivalent at terminals $a - b$ of the network in Fig. 6.

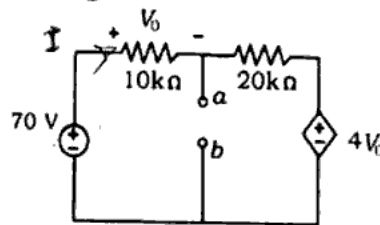


Fig.-6.

- b) Determine the Laplace transform of $f(t) = t^2 * \sin(2t) * u(t)$.

6

8. a) Solve for V_0 using mesh analysis in Fig. 7.

8


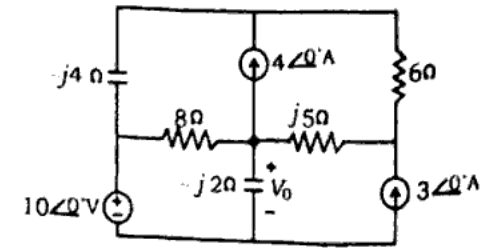



Fig.-7.

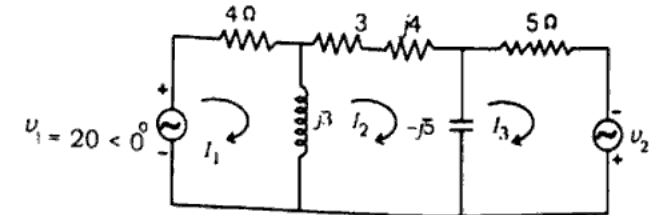- b) Determine the value of v_2 such that the current through impedance $(3 + j4)\Omega$ is zero.



7

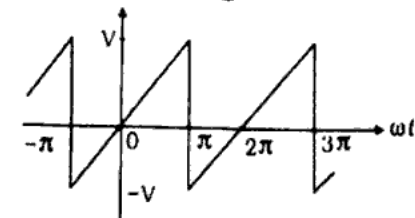9. a) Find the Fourier expansion of the following waveform shown in figure.



- b) Determine the Fourier transform and sketch the amplitude and phase and phase spectrums of the functions

$$f(t) = Ve^{-t/a} \text{ for } t \geq 0$$

$$= 0 \text{ for } t \leq 0$$

8 + 7

10. Find out the fundamental cut-set matrix and fundamental tie-set matrix of Fig. 8.

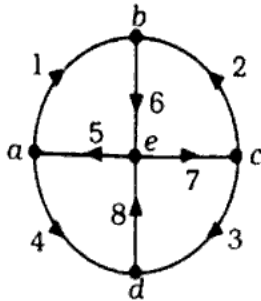


Fig. 8

11. a) A 2nd order active filter is shown in the Fig. 9 find out the transfer function of the filter and show that it is a low-pass filter. 9

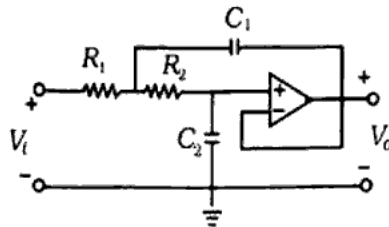


Fig. 9

- b) Design a high-pass filter with a high frequency gain of 5 and a corner frequency of 2 kHz. Use a $0.1 \mu\text{F}$ capacitor in your design. 6