



WEST BENGAL UNIVERSITY OF TECHNOLOGY

ES-201

BASIC ELECTRICAL & ELECTRONIC ENGINEERING - II

Time Allotted: 3 Hours

Full Marks: 70

The questions are of equal value.

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

PART-I(Electrical)

(Used blue color answer book for this part)

GROUP A

(Multiple Choice Type Questions)

1. Answer any *five* questions. 5×1 = 5
- (i) The output voltage of a dc generator is
- (A) ac square wave (B) ac sinusoidal wave
(C) pulsating dc (D) pure dc
- (ii) In a transformer, the flux phasor
- (A) leads the induced emf by 90°
(B) lags the induced emf by 90°
(C) leads the induced emf by slightly less than 90°
(D) lags the induced emf by slightly less than 90°

CS/B.Tech/Even/Sem-2nd/ES-201/2015

- (iii) When a 50 Hz transformer is operated at 400 Hz, its KVA rating is
- (A) increased by 8 times
 - (B) reduced by 8 times
 - (C) unaffected
 - (D) determined by load on secondary
- (iv) Two wattmeters are connected to measure the input to a balanced three phase circuit. The readings of the instruments are W_1 & W_2 respectively. The currents lag by an angle θ behind the corresponding phase voltages
- (A) if $\theta = 0^\circ$, $W_1 > W_2$
 - (B) if $\theta < 60^\circ$ both W_1 & W_2 are positive
 - (C) if $\theta = 30^\circ$, $W_2 > 0$
 - (D) for $\theta > 60^\circ$, W_1 is positive
- (v) Power developed by dc motor is maximum when the ratio of back emf & applied voltage is
- (A) double
 - (B) zero
 - (C) unity
 - (D) half
- (vi) The critical resistance of a dc generator refers to the resistance of
- (A) load
 - (B) brushes
 - (C) field
 - (D) armature

GROUP B
(Short Answer Type Questions)

Answer any *two* questions.

2×5 = 10

2. Draw the exact equivalent circuit of a transformer & describe briefly the various parameters involved in it.

CS/B.Tech/Even/Sem-2nd/ES-201/2015

3. Find an expression of electric field intensity and electric potential of an isolated point charge.
4. Show that the power in a three phase circuit can be measured using 2 wattmeters.
5. What is slip? Deduce a relationship between rotor current frequency & supply frequency in terms of slip of an induction motor.

GROUP C
(Long Answer Type Questions)

Answer any two questions.

 $2 \times 10 = 20$

6. (a) Why is the open circuit test on a transformer conducted at a rated voltage? Explain. 3+7
 (b) A 20 KVA, 2000/200V single phase transformer has a primary resistance of 2.1Ω and a secondary resistance of 0.02Ω . If the total iron loss equals 200W, find the efficiency on (i) full load & a p.f of 0.5 lagging (ii) half load & a p.f of 0.8 leading.
7. (a) What is meant by back emf? Explain the principle of torque production in a dc motor. 5
 (b) A dc motor takes an armature current of 100A at 230V. The armature resistance is 0.05Ω . The total number of lap connected armature conductors are 500 & the number of poles is 4. The flux per pole is 0.03wb. Find the speed & torque. 5
8. (a) "A rotating field is created in a three phase induction motor when a balanced three phase ac supply is applied at the stator". Explain. 5

CS/B.Tech/Even/Sem-2nd/ES-201/2015

- (b) A three phase 4 kw, 400V, 50Hz, induction motor is working at full load with an efficiency of 90% at a power factor of 0.8 lagging. Calculate (i) the input power (ii) the line current. 5
- 9.(a) In a three phase four wire power distribution system, phase B is open while current through R & Y are $100 \angle -30^\circ$ & $60 \angle 60^\circ$. Find the current through the neutral connection. 4
- (b) Three equal charges each of magnitude 3.5×10^{-6} C are placed at three corners of a right angled triangle of sides 3cm, 4cm, 5cm. Find the force on the charge at the right angle corner. 6

PART-II(Electronics)*(Used green color answer book for this part)***GROUP A****(Multiple Choice Type Questions)**1. Answer any *five* questions.

5×1 = 5

(i) FET is less noisy than BJT because of

- (A) high input resistance (B) low output resistance
(C) voltage controlled current (D) unipolar current

(ii) MOSFET is a

- (A) current controlled device
(B) voltage controlled device
(C) temperature controlled device
(D) none of these

(iii) Current shunt feedback is used in

- (A) voltage amplifier
(B) current amplifier
(C) transconductance amplifier
(D) transresistance amplifier

(iv) An OP-AMP has

- (A) negligible input resistance
(B) infinitely large voltage gain
(C) very large output impedance
(D) all of these

(v) The simplest form of Boolean expression $A \oplus \bar{A}B$ is

- (A) A (B) B
(C) AB (D) A+B

- (vi) What range of decimal values can be represented by an eight bit positive unsigned binary number
- (A) 0 to 63 (B) 0 to 127
(C) 0 to 255 (D) 0 to 511

GROUP B
(Short Answer Type Questions)

Answer any *two* questions.

$$2 \times 5 = 10$$

2. (a) What is the relation among JFET parameters? 2.5+2.5
(b) What are the advantages of FET over BJT?
3. Deriving proper expression explain the effect of positive feedback on gain, input impedance, output impedance, stability and bandwidth. 5
4. Draw the block diagram of an OP-AMP and write down the characteristics of an ideal OP-AMP. 5
5. (a) Perform the following number conversion: 2.5+2.5
(i) $(11011.1010)_2 = (?)_{10}$
(ii) $(756.603)_8 = (?)_{16}$
(b) Realize the Boolean expression using minimum number of NOR gates
 $Y = AB' + A'B$


GROUP C
(Long Answer Type Questions)

Answer any *two* questions.

$2 \times 10 = 20$


6. (a) An N-channel JFET amplifier with a voltage divider biasing circuit as shown in the figure has the following parameters: $V_p = -4V$, $I_{DSS} = 4mA$. Calculate the value of drain current at the operating point. Verify whether the FET will operate in the pinch-off region.

7+3

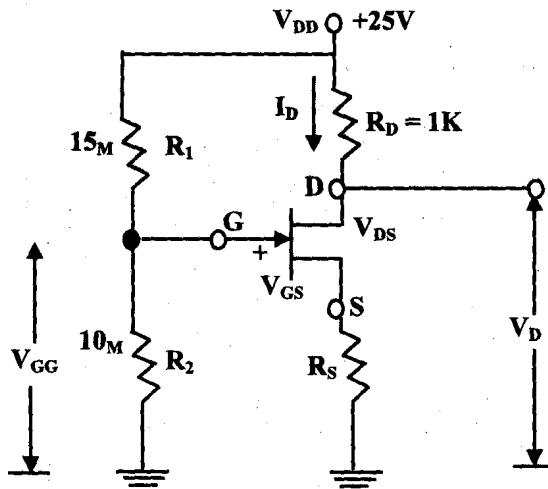

- (b) Explain the basic operation of depletion type n channel MOSFET with a suitable diagram.

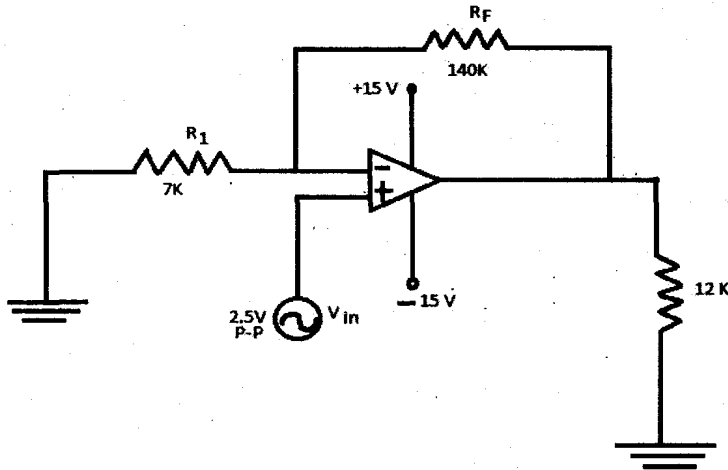7. (a) Obtain the closed loop gain, CMRR in dB and maximum operating frequency for the non-inverting amplifier shown in the figure whose common-mode gain is 0.003 and slew rate is $0.2 \text{ V}/\mu\text{s}$. 5+2+3



- (b) What do you mean by negative feedback?
 (c) Why is it used in designing an amplifier?
8. (a) Why NAND gate is called a 'universal' gate? Explain with examples. 5+5
 (b) A current series feedback amplifier has the following circuit parameters: $R_L = 1K\Omega$, $R_E = 100\Omega$, $R_2 = 20k\Omega$, $R_1 = 30k\Omega$ and $h_{fe} = 100$. Calculate A , β , R_{if} , A_f and loop gain in dB.
9. Write short notes on any two of the following: 2×5
 (a) Slew rate
 (b) Barkhausen criterion
 (c) Pinch-off condition of JFET
 (d) Op-amp as an integrator.