



**WEST BENGAL UNIVERSITY OF TECHNOLOGY**

**ES-201**

**BASIC ELECTRICAL & ELECTRONIC ENGINEERING - II**

Time Allotted: 3 Hours

Full Marks: 70

*The questions are of equal value.*

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

**PART-I(Electrical)**

*(Used blue color answer book for this part)*

**GROUP A**

**(Multiple Choice Type Questions)**

1. Answer any five questions.

5 × 1 = 5

(i) The output voltage of a dc generator is

- (A) ac square wave                      (B) ac sinusoidal wave  
(C) pulsating dc                        (D) pure dc

(ii) In a transformer, the flux phasor

- (A) leads the induced emf by  $90^\circ$   
(B) lags the induced emf by  $90^\circ$   
(C) leads the induced emf by slightly less than  $90^\circ$   
(D) lags the induced emf by slightly less than  $90^\circ$

(iii) When a 50 Hz transformer is operated at 400 Hz, its KVA rating is

- (A) increased by 8 times  
(B) reduced by 8 times  
(C) unaffected  
(D) determined by load on secondary

(iv) Two wattmeters are connected to measure the input to a balanced three phase circuit. The readings of the instruments are  $W_1$  &  $W_2$  respectively. The currents lag by an angle  $\theta$  behind the corresponding phase voltages

- (A) if  $\theta = 0^\circ$ ,  $W_1 > W_2$   
(B) if  $\theta < 60^\circ$  both  $W_1$  &  $W_2$  are positive  
(C) if  $\theta = 30^\circ$ ,  $W_2 > 0$   
(D) for  $\theta > 60^\circ$ ,  $W_1$  is positive

(v) Power developed by dc motor is maximum when the ratio of back emf & applied voltage is

- (A) double                                      (B) zero  
(C) unity                                        (D) half

(vi) The critical resistance of a dc generator refers to the resistance of

- (A) load                                        (B) brushes  
(C) field                                        (D) armature

**GROUP B**

**(Short Answer Type Questions)**

Answer any two questions.

2 × 5 = 10

2. Draw the exact equivalent circuit of a transformer & describe briefly the various parameters involved in it.

3. Find an expression of electric field intensity and electric potential of an isolated point charge.
4. Show that the power in a three phase circuit can be measured using 2 wattmeters.
5. What is slip? Deduce a relationship between rotor current frequency & supply frequency in terms of slip of an induction motor.

**GROUP C**  
**(Long Answer Type Questions)**

Answer any two questions.

2×10 = 20

6. (a) Why is the open circuit test on a transformer conducted at a rated voltage? Explain.
- (b) A 20 KVA, 2000/200V single phase transformer has a primary resistance of  $2.1\Omega$  and a secondary resistance of  $0.02\Omega$ . If the total iron loss equals 200W, find the efficiency on (i) full load & a p.f of 0.5 lagging (ii) half load & a p.f of 0.8 leading.
7. (a) What is meant by back emf? Explain the principle of torque production in a dc motor.
- (b) A dc motor takes an armature current of 100A at 230V. The armature resistance is  $0.05\Omega$ . The total number of lap connected armature conductors are 500 & the number of poles is 4. The flux per pole is 0.03wb. Find the speed & torque.
8. (a) "A rotating field is created in a three phase induction motor when a balanced three phase ac supply is applied at the stator". Explain.

3+7

5

5

5

- (b) A three phase 4 kw, 400V, 50Hz, induction motor is working at full load with an efficiency of 90% at a power factor of 0.8 lagging. Calculate (i) the input power (ii) the line current.
- 9.(a) In a three phase four wire power distribution system, phase B is open while current through R & Y are  $100 \angle -30^\circ$  &  $60 \angle 60^\circ$ . Find the current through the neutral connection.
- (b) Three equal charges each of magnitude  $3.5 \times 10^{-6}$  C are placed at three corners of a right angled triangle of sides 3cm, 4cm, 5cm. Find the force on the charge at the right angle corner.

5

4

6