

**ENGINEERING & MANAGEMENT EXAMINATIONS, DECEMBER - 2008****ELECTRONIC SYSTEM DESIGN****SEMESTER - 3**

Time : 3 Hours]

[Full Marks : 70

GROUP - A**(Multiple Choice Type Questions)**

1. Choose the correct answer from the given alternatives for any *ten* of the following :

 $10 \times 1 = 10$

i) The gain of a OP-AMP is

- | | |
|---------|---------------|
| a) low | b) very low |
| c) high | d) very high. |

ii) The input impedance of OP-AMP is

- | | |
|--------------------------------|----------------|
| a) infinite | b) zero |
| c) very high, but not infinite | d) very small. |

iii) We are giving sine wave to the input of a differentiator, the output we get is

- | | |
|----------------|--------------------|
| a) square wave | b) triangular wave |
| c) cosine wave | d) sawtooth wave. |

iv) Schmitt Trigger is used to

- | |
|--|
| a) form sine wave |
| b) form square wave |
| c) convert irregular shaped waveform in square pulse |
| d) none of these. |

v) A filter that cannot pass only 3 kHz frequency signal is a

- | | |
|-------------|----------------------|
| a) low-pass | b) highpass |
| c) notch | d) band-pass filter. |




vi) An OP-AMP has a slew rate of $5\text{V}/\mu\text{s}$. The largest sine wave output voltage possible at a frequency of 1 MHz is

- a) $5/2$ volt b) $3/2$ volt
c) 2 volt d) $3/8$ volt.



vii) The voltage follower has a

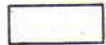- a) small open loop voltage gain
b) closed loop voltage gain of unity
c) closed loop bandwidth of zero
d) large closed loop output impedance.



viii) The OP-AMP circuit shown in the fig. (1) is a filter, the type of filter and its cut-off frequency are respectively

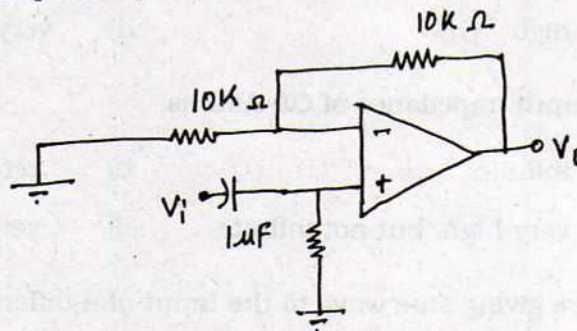


Fig. 1

- a) high-pass, 1000 rad/s b) low-pass, 1000 rad/s
c) high-pass, 10000 rad/s d) low-pass, 10000 rad/s .



ix) For the circuit shown in fig. (2) $V_i = -0.3\text{ V}$. The value of V_o is


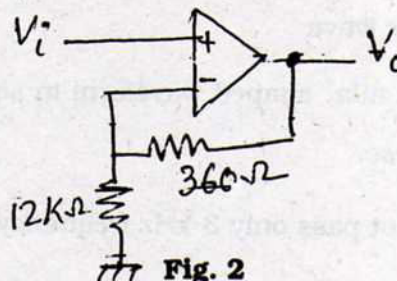


Fig. 2

- a) -9.6 V b) -9.3 V
c) -2 V d) -10 V .

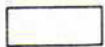



- x) A band-pass filter is built by cascading a low-pass filter with a high-pass filter. Which filter has the lower cut-off frequency ?
- a) The high-pass filter b) The low-pass filter
- c) Neither of them d) Both of them combinedly.
- xi) For a non-inverting OP-AMP, which of the following statements is true ?
- a) The closed loop gain is reduced by a factor β
- b) CMRR is increased by a factor β
- c) The bandwidth increased by a factor β
- d) All of these.
- xii) A differential amplifier is used at the input stage of any operational amplifier to ensure
- a) high CMRR b) Wide bandwidth
- c) high slew rate d) high open loop gain.
- xiii) We can reject only one frequency by
- a) LPF b) HPF
- c) BPF d) Notch Filter.
- xiv) Astable multivibrator has
- a) one quasi-stable state b) one stable state
- c) no stable state d) none of these.

GROUP - B

(Short Answer Type Questions)

Answer any *three* of the following.

3 × 5 = 15

2. Draw a circuit diagram of a basic log amplifier using a transistor as the feedback element.

Derive the expression for the output voltage. What are the applications of log amplifier ?

2 + 2 + 1

3. Draw the circuit diagram and explain the principle of operation of a non-inverting comparator circuit.

5



4. Draw and explain the operation of window detector circuit. 5
5. Draw the circuit for an astable multivibrator using 555 timer to get 50% duty cycle. 5
6. Explain the operating principle of both voltage-to-current as well as current-to-voltage converters. 5

GROUP - C

(Long Answer Type Questions)

Answer any three questions.

3 × 15 = 45

7. a) Draw and explain Wien-bridge oscillator. 8
- b) Explain with diagram, the operation of a triangular wave generator. 7
8. Explain how to use the 555 timer as a voltage controlled oscillator.

What do you mean by pH of a solution ? Describe the principle of the technique of pH measurement. 8 + 7

9. Explain what you mean by an active low-pass filter. Design a non-inverting low-pass filter circuit that has a gain of 10 at low frequencies, a high frequency cut-off point of 159 Hz and an input impedance of 10 kΩ. 5 + 10

10. Draw the 3-OP-AMP instrumentation amplifier circuit and derive its output voltage expression. What is the need of a variable resistance in the transducer bridge to make an instrumentation amplifier ? The following circuit (Fig. 3) shows a controlled gain amplifier. What is the gain of the amplifier circuit when

- i) switch S is off
- ii) switch S is on ?

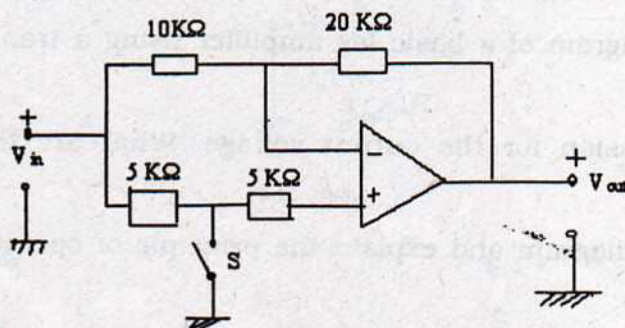


Fig. 3

3 + 5 + 2 + 5



3 × 5 = 15

11. Write short notes on any *three* of the following :

- a) Slew rate
- b) CMRR
- c) Precision rectifier
- d) Strain gauge
- e) Input offset voltage.

END