

**CS/B.TECH/EE/EVEN/SEM-8/EE-801A/2015-16**



**MAULANA ABUL KALAM AZAD UNIVERSITY OF  
TECHNOLOGY, WEST BENGAL**

**Paper Code : EE-801A**

**HVDC TRANSMISSION**

*Time Allotted : 3 Hours*

*Full Marks : 70*

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own  
words as far as practicable.*

**GROUP – A**

**( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any *ten* of the  
following :  $10 \times 1 = 10$

i) The lowest current harmonic produced in 12-pulse  
converters is

- |       |                   |
|-------|-------------------|
| a) 11 | b) 13             |
| c) 23 | d) none of these. |

8/80115

[ Turn over

**CS/B.TECH/EE/EVEN/SEM-8/EE-801A/2015-16**

ii) During commutation in a converter with very high  
inductive load

- a) voltage is exchanged
- b) current is transferred from one valve to the  
other
- c) dc voltage is blocked
- d) dc current is blocked.

iii) Peak to peak ripple in a 12-pulse converter is

- |                 |                 |
|-----------------|-----------------|
| a) $0.5236 V_d$ | b) $0.114 V_d$  |
| c) $0.3206 V_d$ | d) $0.0345 V_d$ |

iv) For an existing ac transmission line, the string  
efficiency is 80%. If dc voltage is supplied for the  
same set up, the string efficiency will be

- |         |         |
|---------|---------|
| a) 100% | b) 90%  |
| c) 80%  | d) 50%. |

8/80115

2

CS/B.TECH/EE/EVEN/SEM-8/EE-801A/2015-16

v) For a six-pulse converter with source reactance  $X \Omega$  per phase, the equivalent resistance of the converter is given by

- a)  $3X$
- b)  $\frac{3X}{\pi}$
- c)  $\frac{X}{\pi}$
- d)  $3\pi X$

vi) Fault current level is highest for

- a) converter internal fault
- b) *dc* line fault
- c) commutation failure
- d) lightning stroke on lines.

vii) Voltage dependent current order limit controlling is done and it is necessary

- a) when low voltage due to faults
- b) to regulate *dc* current depending on *dc* voltage due to fault on *ac* side
- c) to regulate *dc* current when *dc* voltage dips
- d) to regulate *ac* current under faults.

CS/B.TECH/EE/EVEN/SEM-8/EE-801A/2015-16

viii) Valve group protection is done using

- a) overcurrent protection
- b) differential protection
- c) current control limiter
- d) HRC fuses in each group.

ix) Converter faults are cleared by

- a) tripping of *ac* side CBs
- b) blocking the rectifier and inverter
- c) opening the ground or neutral CB
- d) using backup protection schemes.

x) Basic control philosophy in MTDC systems is

- a) total rectifier current is constant
- b) total inverter current is constant
- c) total current, both rectifier and inverter is zero
- d) none of these.

CS/B.TECH/EE/EVEN/SEM-8/EE-801A/2015-16

xi) Which of the following faults is self-clearing ?

- a) DC line fault
- b) single commutation failure
- c) multiple commutation failure
- d) arc back and arc through.

xii) In a bipolar system

- a) both conductor and positive
- b) both conductor are negative
- c) one conductor is positive and the other is negative
- d) one conductor is positive or negative and the other is at ground potential.

#### GROUP – B

##### ( Short Answer Type Questions )

Answer any *three* of the following.  $3 \times 5 = 15$

2. What are the various sources for generation of harmonics in HDVC systems ? Mention the adverse effects caused due to the presence of harmonics.
3. Explain the equidistant pulse control scheme used in HVDC systems.

CS/B.TECH/EE/EVEN/SEM-8/EE-801A/2015-16

4. What are the different losses in HVDC system ?

Compare it with *ac* systems.

5. With a neat schematic diagram, state the various apparatus required for HVDC station and explain the purpose of each.

6. Why are multi-terminal *dc* systems needed ? What are the different types of MTDC systems used ?

#### GROUP – C

##### ( Long Answer Type Questions )

Answer any *three* of the following.  $3 \times 15 = 45$

7. a) With the help of a schematic diagram, explain the principle of operation of 12-pulse converter.  
b) Obtain the expression for PIV, peak to peak ripple and valve volt ampere rating of a 6-pulse Graetz converter circuit. 9 + 6
8. a) What are the different types of faults that can occur in HVDC systems ?  
b) Discuss protection scheme in HVDC system for  
(i) protection against overcurrent & overvoltage,  
(ii) protection of filter unit. 5 + 10

CS/B.TECH/EE/EVEN/SEM-8/EE-801A/2015-16

9. a) Explain characteristic variation of harmonic currents with variation of firing angle and overlap angle.
- b) What are non-characteristic harmonic in HVDC systems ?
- c) The ac system voltage at the rectifier end is 220 kV. Estimate the six harmonic voltage of a 6-pulse converter when  $\alpha = \frac{\pi}{2}$  &  $\mu = 0$ . 7 + 3 + 5
10. a) What are the various control schemes employed for HDVC converters ?
- b) Explain the vector control scheme of HVDC-VSC schemes. 7 + 8
11. a) Explain with schematic diagram, the principle of operation of FACTS converters.
- b) What is meant by 'multi-level dc system' ? Explain.
- c) Discuss parallel operation of MTDC. 7 + 4 + 4
-