

CS/B.Tech/ECE/odd/Sem-7th/EC-705D/2014-15

CS/B.Tech/ECE/odd/Sem-7th/EC-705D/2014-15

**EC-705D****POWER ELECTRONICS**

Time Allotted: 3 Hours

Full Marks: 70

*The questions are of equal value.**The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable***GROUP A  
(Multiple Choice Type Questions)**1. Answer any *ten* questions. 10×1 = 10

(i) The chopper is used

- (A) to obtain variable dc voltage from a source of constant dc voltage
- (B) to obtain variable dc voltage from a source of constant ac voltage
- (C) to obtain variable ac voltage from a source of constant dc voltage
- (D) to obtain variable ac voltage from a source of constant ac voltage

(ii) Meaning of RCT is

- (A) reverse conducting thyristor
- (B) random collection of thyristor
- (C) repeated conduction thyristor
- (D) reverse conducting transistor

(iii) The function of inverter is

- (A) to get variable ac voltage from dc voltage
- (B) to get ac voltage from dc voltage
- (C) to get variable dc voltage from ac voltage
- (D) to get variable ac voltage from ac voltage

(iv) In a thyristor the ratio of latching current to holding is

- (A) 0.4
- (B) 1.0
- (C) 2.5
- (D) 6.0

(v) Static V-I characteristics of an SCR with different gate drives applied to the gate are indicated by

- (A)  $I_{g2} > I_{g1} > I_{go}$
- (B)  $V_{g2} > V_{g1} > V_{go}$
- (C)  $P_{g2} > P_{g1} > P_{go}$
- (D) either (A) or (B)

(vi) For an SCR dv/dt protection is achieved through the use of

- (A) RL in series with SCR
- (B) RC across SCR
- (C) L in series with SCR
- (D) L across SCR

(vii) The average of 180° conduction mode of three phase inverter circuit over 120° conduction mode is

- (A) it needs less number of switches
- (B) there is no paralleling of switches
- (C) devices in series are not simultaneously switched
- (D) load terminal are not left open during switching

(viii) Chopper control of DC motors provides variations in

- (A) input voltage
- (B) current
- (C) frequency
- (D) all of these

(ix) Resonant converters are basically used to

- (A) generate large peak voltages
- (B) eliminate harmonics
- (C) reduce switching losses
- (D) convert a square wave into a sine wave

(x) A single phase half wave controlled rectifier has  $400 \sin 314t$  as the input voltage and R as the load. For a firing angle of 30° for the thyristor, the average output voltage is

- (A) 118.85
- (B) 127.38
- (C) 95.54
- (D) 76.43

(xi) Switching mode power supplies are superior to linear power supplies in respect of

- (A) size and efficiency
- (B) efficiency and regulation
- (C) regulation and noise
- (D) noise and cost

CS/B.Tech/ECE/odd/Sem-7th/EC-705D/2014-15

CS/B.Tech/ECE/odd/Sem-7th/EC-705D/2014-15

**GROUP B**  
(Short Answer Type Questions)

Answer any three questions.

3×5 = 15

2. A thyristor is used to feed a load resistance  $8\Omega$  from a 230V single phase supply. The ratings of thyristors are: Repetitive peak current = 300A,  $(di/dt)_{\max} = 40A/\mu\text{sec}$  and  $(dv/dt)_{\max} = 150V/\mu\text{sec}$ . Design a snubber circuit for protection of thyristor. 5
3. What is cyclo-converter? Explain the operation of a single phase step down cyclo-converter. 1+4
4. Explain with two transistor analogy of SCR, how positive feedback action takes place during turn-on an SCR. 5
5. What are the advantages of resonant converters over conventional DC to DC converters? State the concept of quasi resonant converter. 3+2
6. Draw a comparison between power transistors, power MOSFET and IGBT in relation to their application in power electronics.

**GROUP C**  
(Long Answer Type Questions)

Answer any three questions.

3×15 = 45

7. (a) Why is three phase bridge full wave controlled rectifier called a six-pulse converter? Explain with circuit diagram and output waveforms. 8+7
- (b) A 3-phase full converter feeds power to a resistive load of  $10\Omega$ . For a firing angle delay of  $30^\circ$ , the load takes 5 kW. Find the magnitude of per phase input supply voltage.

8. (a) Why is a three phase bridge full wave controlled rectifier called a six-pulse converter?
- (b) Explain the operation of a single phase fully controlled bridge converter connected with R-L load. Show the possible waveforms of the output voltage, SCR current and source current for a firing angle and considering ripple free output current.
- (c) Derive expressions for average and RMS value of output voltage for converter mentioned in (b).
- (d) A battery is charged by a fully controlled single phase converter. The input supply is 50V at 50Hz. The load consists of a 30V battery and a resistance of  $5\Omega$  connected in series to limit the current. What is the minimum possible firing angle? Compute the value of average output voltage. 2+5+4+4
9. (a) Describe with the help of necessary voltage waveforms and circuit diagram, the operation of a three phase and circuit diagram, the operation of a three phase voltage source inverter with  $180^\circ$  conduction mode delivering power to star connected pure resistive load. 10+5
- (b) A single phase half-wave inverter feeds a resistive load  $R_L = 10\Omega$ . Source voltage is 240V DC. Determine the r.m.s. value of current.
10. (a) With the help of relevant waveforms discuss the static and dynamic characteristics of SCR.
- (b) Draw a comparison between power transistor, power MOSFET and IGBT in relation to their application in power electronics.
- (c) Explain the effect of source inductor in the operation of a 3-phase full converter.
11. Write short notes on any three of the following: 3×5
  - (a) RC triggering
  - (b) UPS
  - (c) Induction heating
  - (d) MOSFET
  - (e) Electronic ballast.