

Name : .....

Roll No. : .....

Invigilator's Signature : .....

**CS/B.TECH (EIE)(N)/SEM-3/EC(EI)-301/2012-13**

**2012**

**DIGITAL ELECTRONIC CIRCUITS**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words  
as far as practicable.*

**GROUP - A**

**( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any ten of the following :

10 × 1 = 10


- i) The octal equivalent of the binary number 11010111 is
- |        |        |
|--------|--------|
| a) 656 | b) 327 |
| c) 653 | d) D7. |
- ii) The minimum number of NAND gates required to implement the Boolean function  $A + AB' + AB'C$  is equal to
- |         |       |
|---------|-------|
| a) zero | b) 1  |
| c) 4    | d) 7. |
- iii) The fastest logic gate family is
- |         |         |
|---------|---------|
| a) CMOS | b) ECL  |
| c) TTL  | d) RTL. |

3156(N)

[ Turn over

CS/B.TECH (EIE)(N)/SEM-3/EC(EI)-301/2012-13

 iv) Identify the operation of the following logic gate circuit :



- a) OR gate                      b) AND gate  
 c) NOT gate                      d) none of these.
- v) Which one is used in EPROM eraser ?  
 a) Laser light                      b) UV ray  
 c) LED light                      d) Sunrays.
- vi) Gray code of 1011 (binary) =  
 a) 0101                      b) 1101  
 c) 1110                      d) none of these.
- vii) A ring counter consists of 5 flip-flops will have  
 a) 5 states                      b) 10 states  
 c) 32 states                      d) none of these.
- viii) The flip-flop, which is free from race amount problem is  
 a) R-S flip-flop  
 b) Master-slave JK flip-flop  
 c) J-K flip-flop  
 d) none of these.
- ix) The minterms for  $A + BC$  are  
 a)  $\sum m(2,3,4,5,7)$                       b)  $\sum m(3,4,5,6,7)$   
 c)  $\sum m(1,3,4,5,6,7)$                       d) none of these.
- x) A 10 Mhz signal is applied to a MOD-5 counter followed by a MOD-8 counter then the O/P frequency will be  
 a) 10 kHz                      b) 2.5 kHz  
 c) 5 kHz                      d) 250 kHz.

CS/B.TECH (EIE)(N)/SEM-3/EC(EI)-301/2012-13


- xi) Calculator keyboard is an example of  
 a) decoder                      b) encoder  
 c) multiplexer                d) demultiplexer.
- xii) A single bit memory device is  
 a) ROM                          b) RAM  
 c) F-F                           d) PROM.

**GROUP - B****( Short Answer Type Questions )**Answer any *three* of the following       $3 \times 5 = 15$ 

2. Perform the arithmetic operation :  
 $(-22)_{\text{decimal}} + (13)_{\text{decimal}} + (-15)_{\text{decimal}}$  using 2's complement binary form.
3. Minimize the following expression in SOP form using Quine McClusky method :  
 $F(A, B, C, D) = \sum m(1, 2, 3, 8, 9, 10, 11, 14) + \sum d(7, 15)$
4. Explain the race around condition. Draw the Master/Slave JK flip-flop using all NAND gates.       $2 + 3$
5. Realize the 3-input majority function using NAND gates only.
6. Realize JK flip-flop using T flip-flop and other SSI gates.

**GROUP - C****( Long Answer Type Questions )**Answer any *three* of the following.       $3 \times 15 = 45$ 

 7. a) Design a clocked synchronous sequential network whose state diagram is given below :



- b) Design a mod-6 ripple counter using PRESET lines of JK flip-flops.       $8 + 7$

CS/B.TECH (EIE)(N)/SEM-3/EC(EI)-301/2012-13

8. a) Implement the following Boolean expression using Decoder and extra gate :  

$$F(A, B, C, D) = \sum(1, 2, 5, 7, 8, 10, 12, 13).$$
- b) Implement a full adder circuit using minimum number of NOR gates only.
- c) An 8 : 1 MUX has inputs  $A, B, C$  connected to select line  $S_2, S_1, S_0$  respectively. The data inputs  $I_0$  to  $I_7$  are connected as  $I_1 = I_2 = I_7 = 0$ ,  $I_3 = I_5 = 1$ ,  $I_0 = I_4 = D$ ,  $I_6 = D'$ . Determine the Boolean expression of the MUX output. 5 + 5 + 5
9. a) Construct a 4-bit register with parallel load and shift right controls.
- b) Describe the basic principles of Successive Approximation Method for A/D converter. 10 + 5
10. a) Design MOD-8 synchronous DOWN-counter using the D-flip-flops and other required logic gates.
- b) Calculate the propagation delay for a 4-bit synchronous UP-counter when JK flip-flops are connected in series connection and parallel connection. Given propagation delay  $t_p(FF)$  equals to 30 nsec and the propagation delay of the gates used in the circuit are 20 nsec (assumed to be equal for all gates). 10 + 5
11. Write short notes on any *three* of the following : 3 × 5
- Tri-state gates in TTL family
  - Data Lock-out in a counter
  - Magnitude comparator
  - Mealy machine and Moore machine
  - Parity generator.

=====