

Name :

Roll No. :

Invigilator's Signature :

**CS/B.Tech(CSE/IT)/SEM-3/EC-312/2009-10****2009****DIGITAL ELECTRONICS & LOGIC DESIGN**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words
as far as practicable.***GROUP - A****(Multiple Choice Type Questions)**1. Choose the correct alternatives for any *ten* of the following : $10 \times 1 = 10$

- i) An example of weighted code is
 - a) Excess-3
 - b) ASCII
 - c) Hamming code
 - d) 8421.
- ii) The minimum number of NAND gates required to design one Full Adder circuit is
 - a) 5
 - b) 9
 - c) 6
 - d) 10.
- iii) A decoder with enable input can be used as
 - a) Encoder
 - b) Parity Generator
 - c) NAND
 - d) Demultiplexer.

44001

[Turn over

- iv) The value of 2^6 in octal system is
 a) 20 b) 420
 c) 32 d) none of these.
- v) The maxterm corresponding to decimal 15 is
 a) ABCD b) $A' + B' + C' + D'$
 c) $A + B + C + D$ d) $A' B' C' D'$.
- vi) The decimal equivalent of $(332)_4$ is
 a) 63 b) 94
 c) 62 d) none of these.
- vii) How many 1's are present in the binary representation of decimal number $(3 \times 512 + 7 \times 64 + 5 \times 8 + 3)$?
 a) 8 b) 9
 c) 10 d) 11.
- viii) The greatest negative number of 1-byte in 2's complement scheme is
 a) -256 b) -255
 c) -128 d) -127.
- ix) The output of a logic gate is '1' when all its i/p are at logic '0'. The gate is either
 a) NAND or XOR gate b) NOR or XOR gate
 c) AND or XNOR gate d) NOR or XNOR gate.
- x) J-K flip-flop has
 a) one stable state b) two stable states
 c) no stable state d) none of these.
- xi) Which of the following is reflected code?
 a) 8421 b) Excess-3
 c) Gray d) ASCII.

- xii) Gray code of a binary number 1011 is
- a) 1110 b) 1100
c) 1101 d) 1111.
- xiii) The fast logic family is
- a) TTL b) ECL
c) TRL d) DRL.
- xiv) The operation which is commutative but not associative is
- a) AND b) XOR
c) NAND d) NOT.
- xv) The number of XOR gates required for conversion of 11011 to its equivalent grey code is
- a) 2 b) 4
c) 3 d) 5.

GROUP - B

(Short Answer Type Questions)

Answer any *three* of the following. $3 \times 5 = 15$

2. Realize the following expression using K-map and implement the simplified expression using NOR gates only :
$$F(A, B, C, D) = \Sigma(0, 1, 4, 6, 7, 10, 11, 12, 13, 15) + d(2, 5, 9, 14).$$
3. a) Design 4×16 decoder using 3×8 decoders. 3
b) Implement 2-input XOR function using minimum number of 2-input NAND gates. 2
4. Design full subtractor using 4 : 1 multiplexers.
5. Perform the conversion from S-R to J-K flip-flop.
6. Realise a full-subtractor using all NAND gates.

CS/B.Tech(CSE/IT)/SEM-3/EC-312/2009-10

GROUP - C**(Long Answer Type Questions)**Answer any *three* of the following. $3 \times 15 = 45$

7. a) Describe the operation of successive approximation type ADC. How many clock pulses are required in worst case for each conversion cycle of an 8-bit SAR type ADC ? Define quantizing error for an ADC.
b) Draw a neat diagram for an R-2R ladder type DAC & explain its operation. $7 + 8$
8. a) Design a MOD-10 synchronous binary UP-counter using JK flip-flop & other necessary logic gates.
b) Calculate the propagation delay for a 4-bit synchronous binary UP-counter when JK flip-flops are connected in series connection & parallel connection.
Given Propagation delay T_p (F/F) in 30 nsec & propagation delay of the gates used in the circuit is 20 nsec (assumed to be equal for all gates). $8 + 7$
9. a) Draw the circuit for a 4-bit Johnson counter using D flip-flop & explain its operation. Draw its timing diagram. How does its timing diagram differ from that of Ring counter ?
b) Perform the conversion from D f/f to JK f/f. $8 + 7$
10. a) Distinguish between ROM, PLA & PLD's as elements realizing Boolean function.
b) Design a combinational circuit using an 8×4 ROM that accepts a 3-bit number & generates an output binary number equal to the square of input no.
c) Draw a logic diagram of master-slave JK f/f. Why is it called so ? $7 + 5 + 3$
11. Write short notes on any *three* of the following : 3×5
 - a) EEPROM
 - b) D/A converter
 - c) Triggering of flip-flops
 - d) Comparator
 - e) Data lock-out in a counter.