

CS/B.TECH/EE(N)/EEE(N)/ICE(N)/SEM-3/EC(EE)-302/2013-14

2013

DIGITAL ELECTRONIC CIRCUITS

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks. .**Candidates are required to give their answers in their own words as far as practicable.***GROUP - A****(Multiple Choice Type Questions)**

1. Choose the correct alternatives for any ten of the following :

$$10 \times 1 = 10$$

i) Which code is used in K-map ?

- a) Gray b) BCD
c) Binary d) Hamming.

ii) Gray code of a number is 10110. What is its decimal number ?

- a) 10 b) 15
c) 27 d) None of these.

iii) What is Excess-3 Code of 27 ?

- a) 0101 1001 b) 0010 0100
c) 0101 1010 d) None of these.

3105 (N)

[Turn over

iv) How many flip-flops are required to design Mod-10 Counter ?

- a) 3 b) 4
c) 5 d) 6.

v) $(15)_{10} - (10)_{10}$ is equal to { using 1's complement }

- a) 0101 b) 1010
c) 1110 d) 0010.

vi) If you want to convert a J-K FF to a D-FF then which gate is to be connected between J & K terminals of the J-K FF ?

- a) AND b) OR
c) NOT d) EX-OR.

vii) If an asynchronous counter have three flip-flops with identical, $t_{pd} = 50$ ns, then what is the total propagation delay and the maximum frequency ?

- a) 150 ns & 6.67 MHz b) 160 ns & 5.67 MHz
c) 140 ns & 2.23 MHz d) None of these.

viii) BCD coding of 12 is

- a) 00001010 b) 00001100
c) 00010010 d) none of these.

ix) The result of the BCD addition of 00000111 & 00000011 is

- a) 00001010 b) 00010000
c) 01000001 d) none of these.

3105 (N)

2

- x) A ring counter consists of 5 flip-flops will have
- 5 states
 - 10 states
 - 32 states
 - none of these.
- xi) The equation $\sqrt{213} = 13$ is valid for which one of the number systems with base ?
- Base 8
 - Base 6
 - Base 5
 - Base 4.
- xii) The octal equivalent of $(5EA)_{16}$ is
- 6543
 - 2752
 - 5722
 - 3453.

GROUP - B**(Short Answer Type Questions)**

Answer any *three* of the following. $3 \times 5 = 15$

- Given the logical expression $U = (A + BC)(B + \overline{C}A)$. Design the circuit using NAND gates.
- What is race around condition ? How can we overcome the race around condition ?
- Find the characteristic equation of a JK flip-flop.
- Draw and explain the circuit of 8×1 MUX using two 4×1 MUX and one 2×1 MUX.
- Implement the following Boolean expression using decoder :
 $F(A, B, C, D) = \sum m(1, 2, 5, 7, 8, 10, 12, 13)$

GROUP - C**(Long Answer Type Questions)**

Answer any *three* of the following. $3 \times 5 = 15$

- What is lock out state ?
 - Write a short note on Ring Counter ?
 - Design Mod-6 synchronous counter using JK flip-flops and other gates.
- Write short notes on any *three* of the following :
 - Johnson Counter
 - Propagation Delay
 - Parallel In Serial Out (PISO)
 - Even Parity Generator & Checker
 - Two-bit Comparator.
- Design a Full Adder circuit using $3 : 8$ Decoder.
 - What is priority encoder ? Write the truth table of 4 input priority encoder.
 - Implement the following function using $8 : 1$ MUX
 $F(A, B, C, D) = \sum m(0, 1, 3, 4, 8, 9, 15) + \sum d(5, 10, 13)$
- Find the minimal sum of product for the Boolean expression :
 $f = \sum m(1, 3, 4, 5, 9, 10, 11) + \sum d(6, 8)$ using K-map.
 - Write a short note on Dual slope A/D converter.
- What are the types of PLD ?
 - Design a code converter circuit for BCD to Excess-3 using ROM ?
 - Design a circuit which find the square of a three-bit number using ROM.