



**MAULANA ABUL KALAM AZAD UNIVERSITY OF
TECHNOLOGY, WEST BENGAL**
Paper Code : EE-402
**ELECTRICAL AND ELECTRONICS
MEASUREMENT**

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

GROUP – A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *ten* of the following : $10 \times 1 = 10$

- i) Which bridge is used to measure inductance of high Q inductor ?
- a) Maxwell bridge
 - b) Hay bridge
 - c) Anderson bridge
 - d) Wien bridge.

- ii) In measurement systems, which of the following static characteristics are desirable ?
- a) Sensitivity
 - b) Accuracy
 - c) Reproducibility
 - d) All of these.
- iii) For the measurement of frequency the suitable bridge is
- a) Wien bridge
 - b) Schering bridge
 - c) Hay's bridge
 - d) None of these.
- iv) The deflecting torque of a moving iron instrument is proportional to
- a) I
 - b) I^2
 - c) $I^{1/2}$
 - d) $I^{3/2}$.
- v) In PMMC the scale is
- a) Logarithm
 - b) Exponential
 - c) Uniformly divided
 - d) Non-linear.
- vi) Burden of a CT is expressed in terms of
- a) secondary winding current
 - b) VA rating of the transformer
 - c) Power and power factor of the secondary winding circuit
 - d) Impedance of secondary winding circuit.

- vii) Kelvin's double bridge is called 'double' because
- It has double the accuracy of a Wheatstone bridge
 - Its maximum scale range is double that of a Wheatstone bridge
 - It can measure two unknown resistances simultaneously, i.e., double the capacity of a Wheatstone bridge
 - It has two additional ratio arms, i.e., double the number of ratio arms as compared to a Wheatstone bridge.
- viii) LVDT is a
- Capacitive transducer
 - Resistive transducer
 - Inductive transducer
 - None of these.
- ix) A 1 mA ammeter has a resistance of 100 ohm. It is to be converted to a 1 A ammeter. The value of shunt resistance is
- 0.001 Ω
 - 0.1001 Ω
 - 100000 Ω
 - 100 Ω .
- x) Piezoelectric transducers are
- Passive transducer
 - Active transducer
 - Inverse transducer
 - Both of (b) and (c).

- xi) Horizontally mounted moving iron instrument use
- eddy current damping
 - electromagnetic damping
 - fluid friction damping
 - air friction damping.
- xii) Which of these bridges have high Q -factor and is preferred for measurement of inductance ?
- Maxwell bridge
 - Hay's bridge
 - Owen's bridge
 - De sauty bridge.
- xiii) Which of the following instruments can be used to measure 100 kV ac voltage ?
- PMMC voltmeter
 - moving iron voltmeter
 - electrostatic voltmeter
 - hot wire instrument.

GROUP – B

(Short Answer Type Questions)

Answer any *three* of the following. $3 \times 5 = 15$

- Describe with suitable schematic diagram, the Varley Loop test for localizing earth fault in low voltage cables. 2 + 3
- Explain why Maxwell's Inductance-Capacitance Bridge is not suitable for measurement of inductor values with Q -factor.

4. Explain the construction of CRT with proper diagram.
5. What are the different methods of damping in indicating instruments ?
6. Why the secondary winding of a CT should never be open circuited with its primary still energized ?
7. Why is it necessary to have lag adjustment devices in induction type energy meters ? Draw and explain in brief, operation of such arrangements in a single phase energy meter. 1 + 4

GROUP – C

(Long Answer Type Questions)

Answer any *three* of the following. $3 \times 15 = 45$

8. a) Derive the equations of balance for an Anderson's bridge. Draw the phasor diagram for condition under balance.
- b) The four arms of a bridge are the following :
 Arm ab : an imperfect capacitor C1 with an equivalent series resistance of r_1 .
 Arm bc : a non inductive resistance R3.
 Arm cd : a non inductive resistance R4.

Arm da : an imperfect capacitor C2 with an equivalent series resistance of r_2 , in series with a resistance R2.

A supply of 450 Hz is given between terminals a and c and the detector is connected between b and d. At balance : $R_2 = 4.8 \Omega$, $R_3 = 2 \text{ K } \Omega$, $R_4 = 2.85 \text{ K } \Omega$, $C_2 = 0.5 \mu\text{F}$ and $r_2 = 0.4 \Omega$.

Calculate the value of C1, r_1 and also calculate dissipation factor of this capacitor. Deduce the expression used. (5 + 2) + 8

9. a) Draw and explain different blocks of a CRO. Write the operating principle of a CRT.
- b) What are Lissajous patterns ? How do we measure phase and frequency of ac quantity with the help of a CRO ? (7 + 3) + (1 + 4)
10. Draw and explain the nature of equivalent circuit and corresponding phasor diagram of a potential transformer. Derive expressions for the corresponding ratio error and phase-angle error. 5 + 10
11. a) Write briefly about the construction of an electrodynamic type instrument.
- b) Derive the torque equation of the instrument when an alternative current is passed through the coil.
- c) List the principle errors of this type of instrument.

5 + 7 + 3

CS/B.TECH/EE/EEE/ICE/PWE/EVEN/SEM-4 /EE-402/2015-16

12. Write short notes on any *three* of the following :

$3 \times 5 = 15$

- a) LVDT
 - b) Megger
 - c) Digital Voltmeter
 - d) *Q*-meter
 - e) Creeping and Phantom loading
 - f) Difference between CT and PT.
-