

CS/B.Tech/CSE/IT/Odd/Sem-3rd/CS-301/2015-16

CS/B.Tech/CSE/IT/Odd/Sem-3rd/CS-301/2015-16



**MAULANA ABUL KALAM AZAD
UNIVERSITY OF TECHNOLOGY, WEST BENGAL**

CS-301**ANALOG AND DIGITAL ELECTRONICS****Time Allotted: 3 Hours****Full Marks: 70***The questions are of equal value.**The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable. All symbols are of usual significance.*

**GROUP A
(Multiple Choice Type Questions)**

1. Answer any ten questions.**10×1 = 10****(i) A 2-transistor class B power amplifier is commonly called**

- (A) push-pull (B) dual
(C) differential (D) none of these

(ii) A stable multivibrator has

- (A) no stable state (B) one stable state
(C) two stable states (D) none of these

(iii) Schmitt trigger circuit generates

- (A) triangular wave (B) square wave
(C) saw tooth wave (D) none of these

(iv) A Wien-bridge oscillator has a frequency

- (A) $\frac{1}{2\pi\sqrt{RC}}$ (B) $\frac{1}{RC}$
(C) $\frac{1}{2\pi RC}$ (D) none of these

(v) Which of the following oscillators is used at audio frequency?

- (A) Crystal oscillator (B) Hartley oscillator
(C) RC phase-shift oscillator (D) Colpitts oscillator

(vi) $A + A'B + B'$ is equal to

- (A) A (B) B'
(C) 1 (D) 0

(vii) Negative feedback in an amplifier is

- (A) reduced gain
(B) increased noise
(C) increased frequency and phase
(D) reduced bandwidth

(viii) How many minimum number of NOR gates is required to implement NAND gate?

- (A) 3 (B) 4
(C) 5 (D) 2

(ix) The digital logic family which has minimum power dissipation is

- (A) TTL (B) RTL
(C) DTL (D) CMOS

(x) If the input to T-flip-flop is 100 Hz signal, the final output of the three T-flip-flops in cascade is

- (A) 1000 Hz (B) 500 Hz
(C) 300 Hz (D) 12.5 Hz

CS/B.Tech/CSE/IT/Odd/Sem-3rd/CS-301/2015-16

CS/B.Tech/CSE/IT/Odd/Sem-3rd/CS-301/2015-16

(xi) Which one is the sequential circuit?

- (A) Multiplexer (B) Decoder
(C) Encoder (D) Counter

(xii) 8421 is a

- (A) weighted code (B) non-weighted code
(C) complementary (D) none of these

GROUP B
(Short Answer Type Questions)

Answer any *three* questions.

3×5 = 15

2. Implement Full-adder circuit using two Half-adders. Write the truth table of Half-subtractor. 3+2
3. What is Multiplexer? Why it called data selector? Write the important characteristics of digital IC. 2+1+2
4. Implement the function $F(A,B,C) = \sum m(1,3,5,6)$ using decoder. What is the difference between combinational circuit and sequential circuit? 3+2
5. Draw and explain the operation of Monostable multivibrator using 555 Timer. 5
6. Draw and explain the Schmitt trigger circuit. 5

GROUP C
(Long Answer Type Questions)

Answer any *three* questions.

3×15 = 45

7. (a) Write truth table, circuit diagram and timing diagram of SR flip-flop using NOR gate. 8
(b) Convert D flip-flop into JK flip-flop. 7
8. Explain the operation of a class-B push-pull power amplifier with a neat circuit diagram. Determine its collector circuit efficiency. Explain why even harmonics are not present in push-pull amplifier. 8+4+3
9. (a) Design and implement a comparator circuit, which can compare two 3 bit binary numbers. 5
(b) Simplify the Boolean function using Quine McClusky method. 7
- $$F = \sum_m (1, 3, 4, 5, 9, 10, 11) + \sum_d (6, 8)$$
- (c) Design a 3 bit binary parallel combined ADDER / SUBTRACTOR circuit. 3
10. What is the Barkhausen criterion for a feedback amplifier to function as an oscillator? Give a neat circuit diagram of Wien bridge oscillator and explain how it works. Find an expression for the frequency of oscillation of the astable multivibrator. 2+2+3+3+5
11. Write short notes on any *three* of the following: 3×5
(a) Cross over distortion
(b) Ring counter
(c) Even parity generator and checker
(d) 555 timer
(e) CMOS Logic.