

**MAULANA ABUL KALAM AZAD UNIVERSITY OF TECHNOLOGY, WEST BENGAL**

Paper Code : EC302 Digital System Design

UPID : 003461

Time Allotted : 3 Hours

Full Marks : 70

*The Figures In the margin Indicate full marks.**Candidate are required to give their answers In their own words as far as practicable***Group-A (Very Short Answer Type Question)**

1. Answer any ten of the following :

[1 x 10 = 10]

- (i) The excess-3 code of 584 is given by
- (ii) If the values of R and S are 0, 1 respectively, then the present state and next states are
- (iii) What is the minimum input voltage corresponding to the logic 1 state?
- (iv) In which logic devices both AND-plane and OR-plane are programmable?
- (v) A Carry Look Ahead adder is frequently used for the addition because it _____
- (vi) The Moore circuit output depends on _____
- (vii) A BCD subtractor requires how many parallel adders? _____
- (viii) Shifting binary data to right by one-bit position using shift right register, results
- (ix) If the fan-out parameter of an IC is indicated as 12, it means that
- (x) Which model of VHDL used port mapping?
- (xi) Which number system has radix 4?
- (xii) Mention one of the major drawbacks of using asynchronous counters.

Group-B (Short Answer Type Question)

Answer any three of the following

[5 x 3 = 15]

- 2. What is a logic gate? Mention its types. [5]
- 3. What do you mean by signed and unsigned number representation? How many ways a signed integer can be represented? [5]
- 4. Draw the logic circuit of the S-R flip-flop using the D flip-flop. [5]
- 5. Classification of Digital IC Logic families [5]
- 6. Design the circuit of the Universal shift register. Mention the applications of the Shift register. [5]

Group-C (Long Answer Type Question)

Answer any three of the following

[15 x 3 = 45]

- 7. (a) What is meant by K-Map or Karnaugh Map? Define Quad and Octet. [5]
(b) What are the advantages and disadvantages of the K-Map Method? [5]
(c) How we can implement a 6-variable K-map using a 5-variable? [5]
- 8. (a) What is a flip-flop? Mention the applications of Flip-Flops. [5]
(b) What is a Sequential circuit? Mention the applications of sequential circuits. [5]
(c) Compare Asynchronous counter and Synchronous counter [5]
- 9. (a) Give differences between Latches and Flip-flops. [5]
(b) Explain the operation of the SR latch using NAND gates. [5]
(c) Explain the operation of the SR latch using NOR gates. [5]
- 10. (a) Classification of Semiconductor memories [5]
(b) What are the different memory access methods? [5]
(c) Give five differences between SRAM and DRAM [5]
- 11. (a) What do you mean by FPGA? Name some manufacturers of FPGA. [5]
(b) Explain the architectural design in FPGA. [5]
(c) Mention the applications of FPGA. [5]