

CS/B.TECH/ODD SEM/SEM-1/ES-101/2016-17



**MAULANA ABUL KALAM AZAD UNIVERSITY OF  
TECHNOLOGY, WEST BENGAL**

Paper Code : ES-101

**BASIC ELECTRICAL AND ELECTRONIC  
ENGINEERING - I**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own  
words as far as practicable.*

**PART - I (ELECTRICAL)**

**GROUP - A**

**( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any *five* of the  
following : 5 × 1 = 5

- i) An open circuit may be considered as a resistor of  
value

- ☒ a) zero b) 100 Ω  
c) infinity d) 10 MΩ.

1/10201

[ Turn over

- ii) The admittance of a parallel circuit is  $0.5 \angle -30^\circ$ .  
The circuit is  
a) inductive b) capacitive  
c) resistive d) in resonance.
- iii) Which statement is true for resonance condition of  
RLC series circuit ?  
☒ a) Both impedance and current are maximum  
b) Impedance is maximum & current is minimum  
c) Impedance is minimum & current is maximum  
d) Both impedance & current are minimum.
- iv) An ideal voltage source should have  
a) large value of e.m.f.  
☒ b) small value of e.m.f.  
c) infinite source resistance  
☒ d) zero source resistance.
- v) When a source is supplying maximum power to a  
resistive load, the efficiency of the circuit is  
a) 80 % ☒ b) 50 %  
c) less than 50 % d) 100 %.
- vi) The form factor of a current waveform is 1. Its  
shape is  
a) Sinusoidal b) Triangular  
c) Square d) Sawtooth.

1/10201

2


- vii) In a series R - L circuit, the phase difference between the applied ac voltage & current increases when
- R is increased
  - $X_L$  is increased
  - $X_L$  is decreased
  - input voltage is increased.

### GROUP - B

#### ( Short Answer Type Questions )

Answer any two of the following  $2 \times 5 = 10$

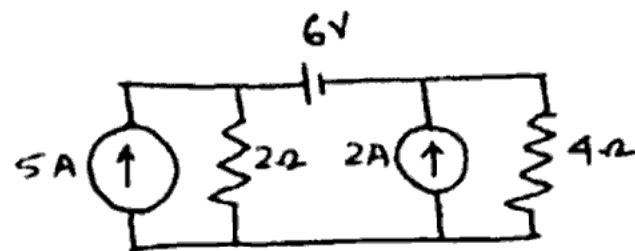2. Deduce an expression of average and RMS value of a half wave rectified voltage wave.
3.
  - a) State and explain Biot-Savart law.
  - b) Deduce an expression of magnetic field due to an infinite length of wire carrying current  $I$  ampere, using Ampere's circuital law.  $2 + 3$
4. Determine the current through  $4 \Omega$  resistor for the circuit shown below :



5. Two coils A of 1000 turns and B of 500 turns are mutually coupled with 80% coupling. If a current of 5A in coil A produces a flux of 0.25 mWb, find the mutual inductance and co-efficient of coupling between the coils.

### GROUP - C

#### ( Long Answer Type Questions )

Answer any two of the following.  $2 \times 10 = 20$


6.
  - a) Define power factor. Show that the active power of a purely capacitive circuit over a complete cycle is zero.
  - b) A coil of resistance  $10 \Omega$  and inductance  $0.02 \text{ H}$  is connected in series with another coil of resistance  $6 \Omega$  & inductance  $15 \text{ mH}$  across a  $230 \text{ V}$ ,  $50 \text{ Hz}$  supply.

Calculate i) impedance of the circuit


ii) the voltage drop across each coil

iii) the total power consumed by the circuit.  $4 + 6$

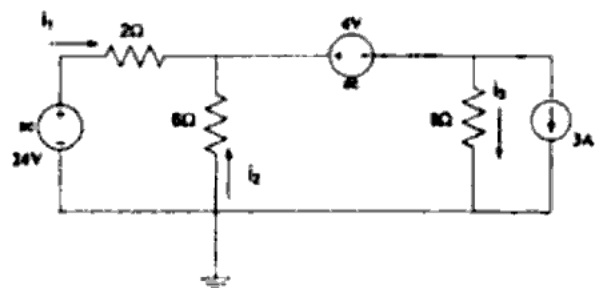7. a) For the circuit shown below, determine the currents  $i_1$ ,  $i_2$ ,  $i_3$  using nodal analysis : 5 + 5




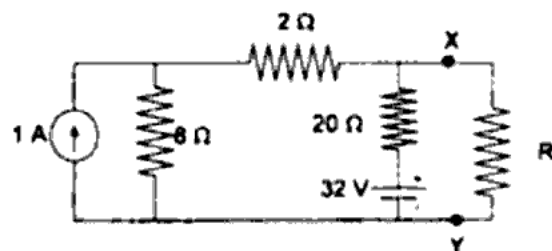- b) Find the Thevenin's equivalent circuit of the following figure between the terminals X-Y.




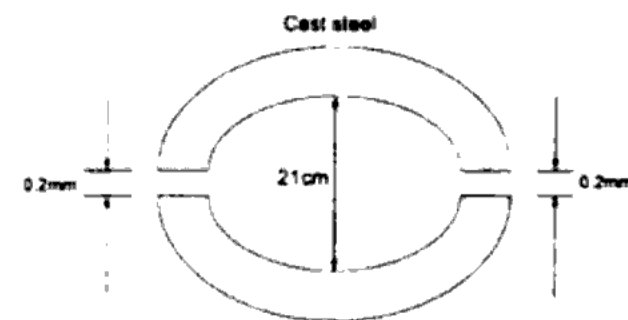8. a) What do you mean by the terms 'Hysteresis' and 'Eddy current losses'.
- b) A ring having a mean diameter of 21cm and a cross-section of  $10\text{cm}^2$  is made of two semi-circular sections of cast-iron and cast-steel respectively with each joint having reluctance equal to air-gap of 0.2 mm as shown in figure. Determine the ampere-turns required to produce a flux of 0.8 mWb. The relative permeabilities of cast-iron

and cast-steel are 166 and 800 respectively. Neglect fringing and leakage effects.



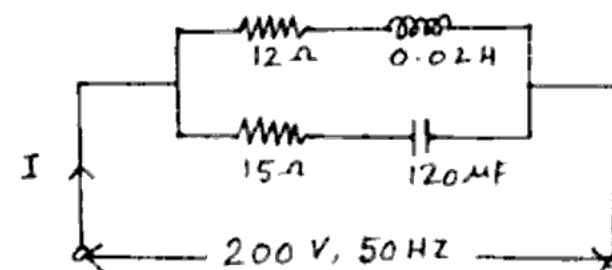9. a) What is resonance ? Deduce the expression of frequency in a series RLC circuit at resonance & its 'Q' factor.
- b) Find the net current  $I$  of the ac parallel circuit shown in figure below.



5 + 5

## PART - II (ELECTRONIC)

### GROUP - A

#### ( Multiple Choice Type Questions )

1. Choose the correct alternatives for any *five* of the following :  $5 \times 1 = 5$ 
  - i) If the cut-in voltage of Ge  $p$ - $n$  diode is  $V_{\gamma 1}$  and that of a Si  $p$ - $n$  diode is  $V_{\gamma 2}$ , then
    - a)  $V_{\gamma 1} = V_{\gamma 2}$
    - b)  $V_{\gamma 1} < V_{\gamma 2}$
    - c)  $V_{\gamma 1} > V_{\gamma 2}$
    - d) none of these.
  - ii) The Fermi level of an  $n$ -type semiconductor lies
    - a) near the conduction band
    - ☒ b) near the valence band
    - c) at the middle of the forbidden gap
    - ☒ d) none of these.
  - iii) If temperature of the collector junction of the transistor increases to  $20^\circ\text{C}$ , the corresponding change in reverse saturation current
    - a) will become double
    - b) reduce to four times of its initial value
    - c) no change
    - d) becomes four times of its initial value.

- iv) The temperature coefficient of the Zener breakdown voltage is
  - a) positive
  - ☒ b) negative
  - c) zero
  - d) none of these.
- v) The ripple factor in the case of half-wave rectifier is
  - a) 0
  - b) 0.75
  - ☒ c) 1.21
  - d) 1.5.
- vi) Band gap of germanium is
  - a) 5.89 eV
  - b) 0.92 eV
  - c) 0.72 eV
  - ☒ d) 1.1 eV.
- vii) Avalanche breakdown primarily depends on the phenomenon of
  - ☒ a) particle collision
  - b) impurity doping
  - c) ionization
  - ☒ d) direct rupture of covalent.
- viii) Which one of the following BJT bias configurations is most stable ?
  - a) Fixed bias
  - b) Emitter stabilized bias
  - c) Voltage divider bias
  - ☒ d) Collector feedback bias.

**GROUP – B**

**( Short Answer Type Questions )**

Answer any *two* of the following  $2 \times 5 = 10$

2. a) Explain Fermi-Dirac function.  
b) "Semiconductor behaves as an insulator at 0 K". Interpret.  $3 + 2$
3. Construct the energy band diagram of a  $p-n$  junction diode when (i) unbiased (ii) forward biased (iii) reverse biased.
4. a) Differentiate between avalanche breakdown and Zener breakdown.  
b) Explain why a Zener diode is used as reference diode.  $4 + 1$
5. Draw and explain the input and output characteristics of a transistor in CE configuration.

**GROUP – C**

**( Long Answer Type Questions )**

Answer any *two* of the following.  $2 \times 10 = 20$

6. a) Explain the term 'transistor biasing'. What are the factors that effect bias stability of a transistor ?

- b) What is self bias ? Draw the circuit diagram showing the self bias of an  $n-p-n$  transistor in the CE configuration.  $2 + 3 + 2 + 3$

7. a) What is Q-point and what is its significance ?  
b) A full-wave rectifier uses a double diode, the forward resistance of each element being 200 ohm. The rectifier supplies current to a load resistance of 1000 ohm. The primary-to-total secondary turns ratio of the centre-tapped transformer is 1:3. The transformer primary is fed from a supply of 240 V(rms). Find (i) the  $dc$  load current, ii) the direct current in each diode, iii) the  $dc$  power output iv) the ripple voltage across the load resistance, v) the percentage regulation, vi) the efficiency of the rectification.  $5 + 5$
8. a) Derive an expression for conductivity of a semiconductor in terms of carrier concentrations.  
b) Pure silicon has an electrical resistivity of 3000  $\Omega\text{-m}$ . If both electron and hole concentration in the sample is  $5 \times 10^{22} \text{ m}^{-3}$  and electron mobility is three times that of hole mobility, evaluate the values of electron & hole mobilities.  $5 + 5$

9. Write short notes on any *two* of the following :  $2 \times 5 = 10$

- a) Self-biasing of BJT
  - b) Zener diode
  - c) Linear piecewise model of diode
  - d) BJT as an amplifier.
-