

2011

**CIRCUIT THEORY & NETWORKS**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.***GROUP – A****( Multiple Choice Type Questions )**

1. Choose the correct alternatives for the following :

 $10 \times 1 = 10$ i) For  $N$  no. of nodes and  $B$  no. of branches of a graph the rank is

a)  $N - B + 1$

b)  $N + B + 1$

c)  $N + 1$

d)  $N - 1$

ii) Laplace transform analysis gives

a) time domain response

b) frequency domain response

c) both (a) and (b)

d) none of these.

- <http://www.makaut.com>

viii) Condition for reciprocity of  $y$ -parameter is

- a)  $y_{11} = y_{12}$                       b)  $y_{12} = y_{21}$   
 c)  $y_{11} = y_{22}$                       d)  $y_{22} = y_{21}$ .

ix) Initial value theorem states that

- a)  $\lim_{s \rightarrow 0} F(s) = f(0)$                       b)  $\lim_{s \rightarrow 0} sF(s) = f(0)$   
 c)  $\lim_{s \rightarrow \infty} F(s) = f(0)$                       d)  $\lim_{s \rightarrow \infty} sF(s) = f(0)$ .

x) A dc voltage  $V$  is applied to a series R-L circuit. The steady state current is

- a)  $\frac{V}{R^2 + L^2}$                       b)  $\frac{V}{L}$   
 c) 0                      d)  $\frac{V}{R}$ .

### GROUP - B

#### ( Short Answer Type Questions )

Answer any *three* of the following.

3 × 5 = 15

2. Explain under what condition, an RC circuit behaves as  
 a) integrator      b) differentiator.
3. State and prove maximum power transfer theorem.
4. A shifted unit step function is expressed as  $f(t) = u(t - a)$ .  
 Obtain its Laplace Transform.

5. For a two port network, show that  $AD - BC = 1$ .
6. Draw the oriented graph of the network in the following figure (Fig. 1) and find the complete incidence matrix.

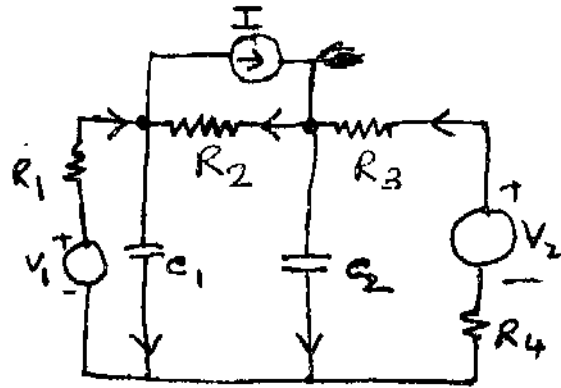


Fig. 1

**GROUP - C****( Long Answer Type Questions )**

Answer any *three* of the following.  $3 \times 15 = 45$

7. a) Explain series and parallel resonance with necessary circuits.
- b) Show that for an RLC series circuit the resonance frequency  $\omega_r = \sqrt{\omega_1 \omega_2}$ , where  $\omega_1$  and  $\omega_2$  are the half power frequencies.
- c) A coil is at resonance at 10 kHz with a capacitor. If the resistance and inductance of the coil are  $200 \Omega$  and 5 H, find Q-factor of the coil.  $5 + 5 + 5$
8. a) Find the total inductance of the three series connected coupled circuits. (Fig. 2)

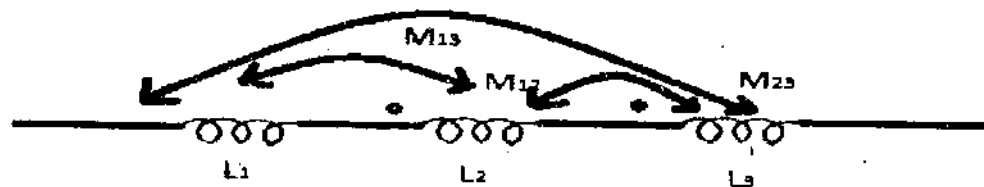


Fig. 2

Given,  $L_1 = 1 \text{ H}$ ;  $L_2 = 2 \text{ H}$ ;  $L_3 = 5 \text{ H}$

$M_{12} = 0.5 \text{ H}$ ;  $M_{23} = 1 \text{ H}$ ,  $M_{13} = 1 \text{ H}$

- b) In the network shown in the Fig. 3 below, find  $V$  such that the current through  $(3 + j4) \Omega$  impedance is zero. Use node voltage analysis.

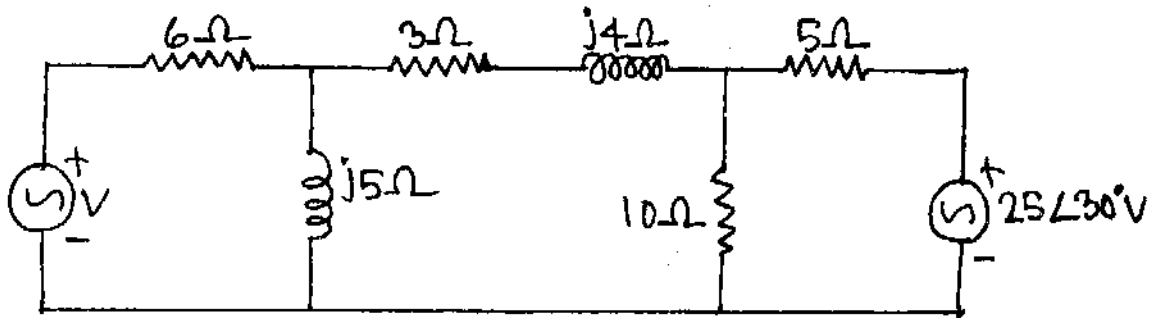


Fig. 3

- c) Find the current through  $R_L$  in the circuit shown in Fig. 4 below using Norton's theorem.

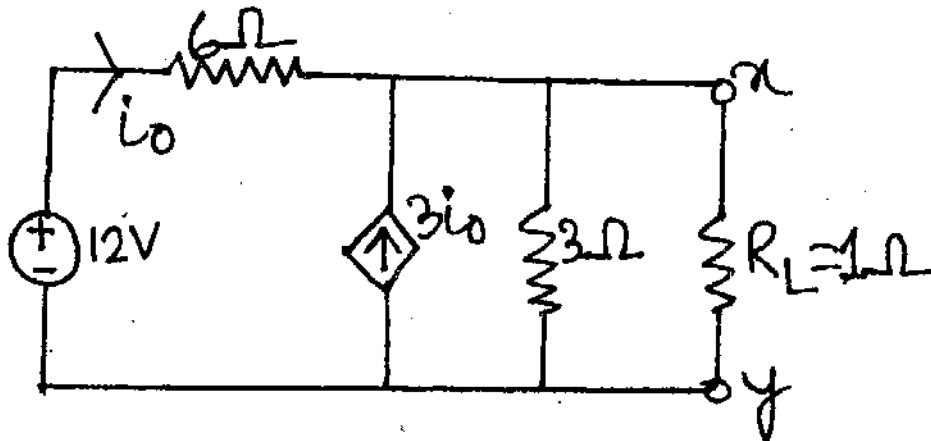


Fig. 4

5 + 5 + 5

9. a) Why are  $h$ -parameters called hybrid parameters? Find the  $h$ -parameters from the two port network given in Fig. 5. Is the network reciprocal or symmetric? Justify.

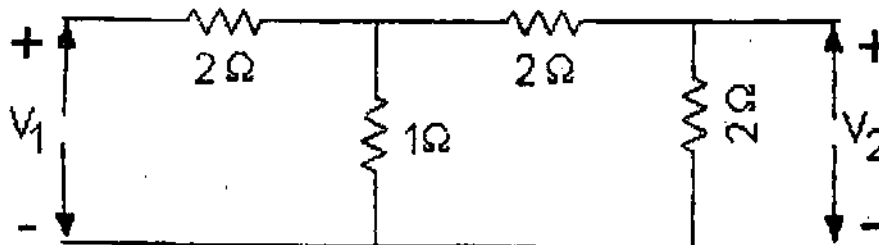


Fig. 5

- b) For an RL series circuit shown below with  $R = 2\ \Omega$ ,  $L = 1\text{H}$  and no initial current in the inductor, a voltage  $V = 4e^{-t}\text{V}$  is applied at  $t = 0$ . Find expression for the resulting current in the circuit for  $t \geq 0$  using Laplace transform method. (Fig. 6)

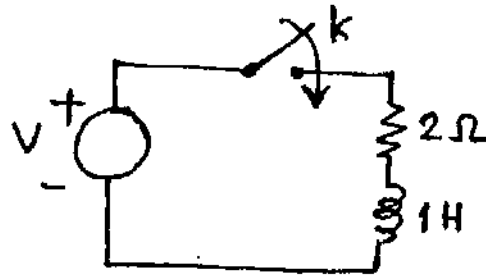


Fig. 6

- c) Find the inverse Laplace transform of the function

$$V(S) = \frac{10(S+4)}{S(S+3)(S+1)^2} \quad 5 + 5 + 5$$

10. a) State and explain superposition theorem.  
b) Find the net current flowing through 10 ohm resistor applying superposition theorem. (Fig. 7)

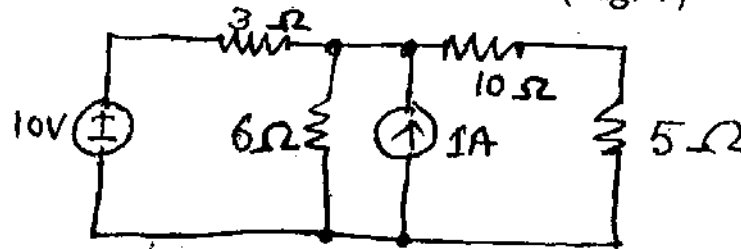


Fig. 7

- c) Find the equivalent delta connection of the given network (Fig. 8)

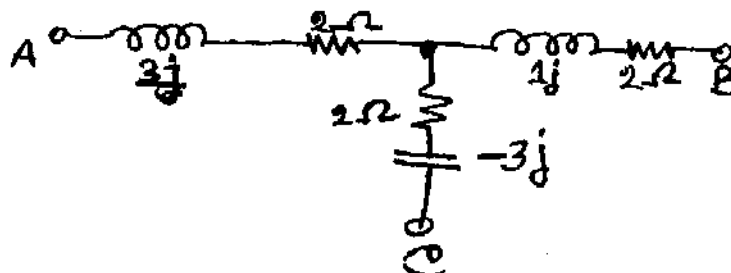


Fig. 8

5 + 5 + 5

CS/B.TECH (ECE-N)/SEM-3/EC-301/2011-12

11. Write short notes on any *three* of the following : 3 × 5

- a) Driving point impedance
  - b) Compensation theorem
  - c) Concept of complex frequency
  - d) Initial value theorem and final value theorem
  - e) Phasor diagrams.
-