



**ENGINEERING & MANAGEMENT EXAMINATIONS, DECEMBER - 2008**  
**CIRCUIT THEORY & NETWORKS**  
**SEMESTER - 3**

Time : 3 Hours ]

[ Full Marks : 70

**GROUP - A****( Multiple Choice Type Questions )**1. Choose the correct alternatives for any ten of the following : 10 × 1 = 10

i) Maximum power transfer occurs at efficiency of

- |         |         |
|---------|---------|
| a) 100% | b) 50%  |
| c) 25%  | d) 75%. |

ii) A periodic waveform possessing half-wave symmetry has no

- |                  |                   |
|------------------|-------------------|
| a) odd harmonics | b) even harmonics |
| c) cosine terms  | d) sine terms.    |

iii) The impedance of an ideal current source should be

- a) 0
- b) infinite
- c) greater than 0 but less than infinity
- d) none of these.


iv) In R-L circuit, the phase angle difference between voltage &amp; current is

- |         |                                       |
|---------|---------------------------------------|
| a) 30°  | b) 90°                                |
| c) 180° | d) greater than 0° but less than 90°. |

v) Unit step function is first derivative of

- a) ramp function                      b) impulse function  
c) gate function                      d) parabolic function.

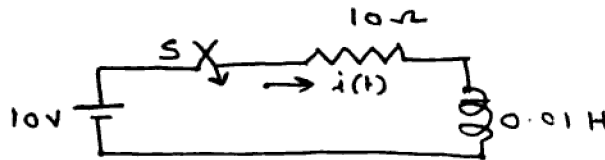vi) After closing the switch 's' at  $t = 0$ , the current  $i(t)$  at any instant 't' in the network shown



is given by

- a)  $10 + 10 e^{100t}$                       b)  $10 - 10 e^{100t}$   
c)  $10 + 10 e^{-100t}$                       d)  $10 - 10 e^{-100t}$

vii) When compared to a first order low pass filter, a second order low pass filter has

- a) lower voltage gain                      b) higher voltage gain  
c) faster drop in filter response                      d) higher cut-off frequency.

viii) A cut set schedule gives relation between






- a) branch currents & link currents  
b) branch voltages & tree branch voltages  
c) branch voltages & link voltages  
d) branch currents & tree currents.

ix) The equation  $Y = mx + c$  is

- a) linear                      b) non-linear  
c) parabolic                      d) none of these.



x) Graphical representation of  $u(a-t)$

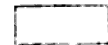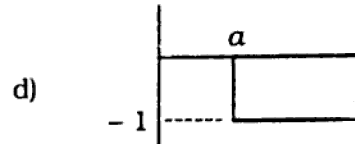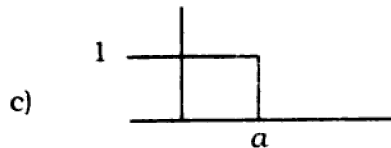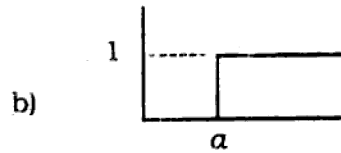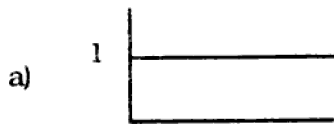

xi) A two port network is reciprocal if & only if

a)  $Z_{11} = Z_{22}$

b)  $BC - AD = -1$

c)  $Y_{12} = Y_{21}$

d)  $h_{12} = h_{21}$



xii) Given  $V_{TH} = 20\text{ V}$  &  $R_{TH} = 5\Omega$ , the current in the load resistance of a network is

a) 4A

b) more than 4A

c) 4A or less

d) less than 4A.



### GROUP - B

#### ( Short Answer Type Questions )

Answer any *three* of the following.

$$3 \times 5 = 15$$

2. For an  $RL$  series circuit shown in the figure 1 with  $R = 2\Omega$  &  $L = 1\text{H}$  and no initial current in the inductor. A voltage  $V = 4e^{-t}$  volts is applied at  $t = 0$ . Find expression for the resulting current in the circuit for  $t \geq 0$  using Laplace transform method.

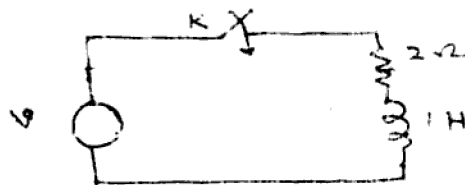


Figure 1

3. a) Define incidence matrix.  
b) For the graph shown in figure 2, find the complete incidence matrix.

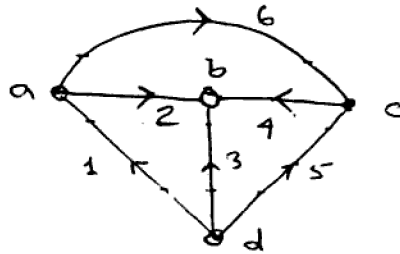


Figure 2

1 + 4

4. What should be the value of  $Z_2$  for maximum power to be delivered in the circuit shown in fig. 3

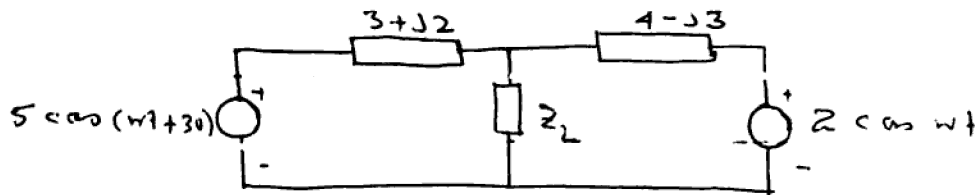


Figure 3

5. In a linear circuit consisting of  $R = 9\Omega$  &  $L = 8\text{ mH}$ , a current.  
 $i = 5 + 100 \sin(1000t + 45^\circ) + 100 \sin(3000t + 60^\circ)$  amps is flowing. Find the equation of applied voltage.  
6. Measurements were made on two terminal network shown in figure 4.

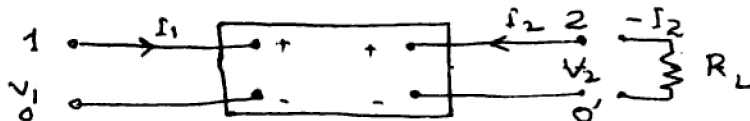



Figure 4

- a) With terminal pair 2 open, a voltage of  $100 \angle 0^\circ$  volts applied to terminal pair 1 resulted in  $I_1 = 10 \angle 0^\circ$  amps &  $V_2 = 25 \angle 0^\circ$  volts.  
b) With terminal pair 1 open, the same voltage applied to terminal pair 2 resulted in  $I_2 = 20 \angle 0^\circ$  amps &  $V_1 = 50 \angle 0^\circ$  volts.

Write the loop equations for this network and also find the driving point & transfer impedances.


**GROUP - C****( Long Answer Type Questions )**Answer any *three* of the following. $3 \times 15 = 45$ 

7. a) Solve the circuit current  $i$  shown in the figure 5 using Thevenin's theorem.

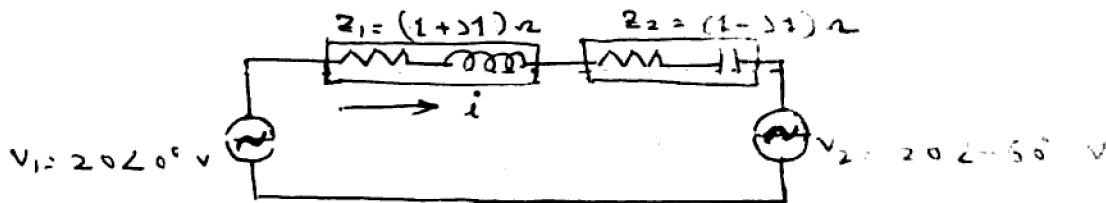**Figure 5**


Verify the result obtained by Norton's theorem.

- b) Obtain the output voltage  $V_0$  across X - Y terminal for the circuit shown in figure 6.

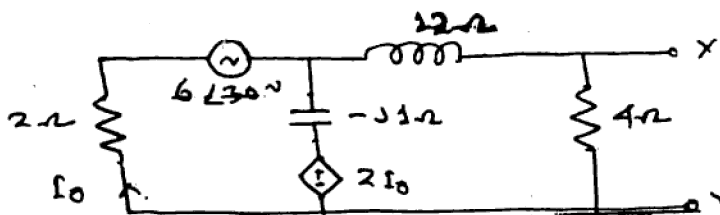**Figure 6**

10 + 5

8. a) Find the Fourier series for the square wave shown in figure 7.

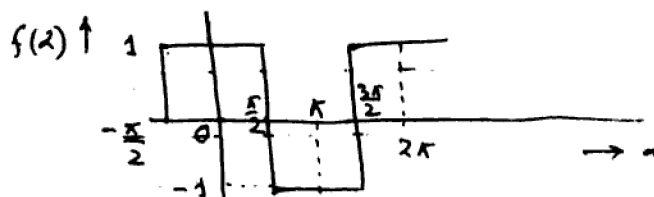**Figure 7**

- b) Find the Fourier transform of an exponential voltage waveform given by

$$v(t) = V_0 e^{-t} \text{ for } t \geq 0$$

$$= 0 \text{ for } t < 0.$$

10 + 5

9. a) What are transmission parameters? Where are they most effectively used?
- b) Calculate the ABCD parameters of the network shown in figure 8.
- c) Find the hybrid parameters of the circuit given in figure 9.

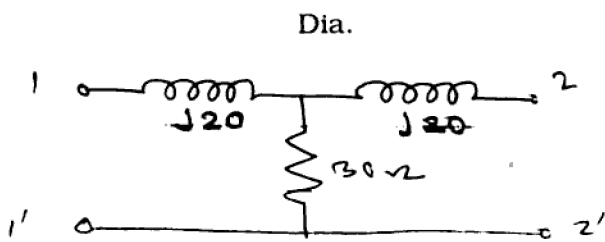


Figure 8

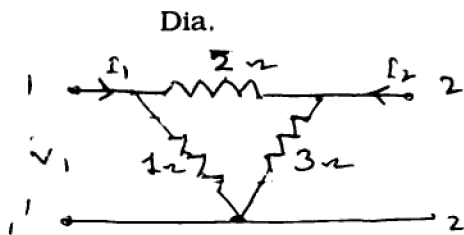


Figure 9

3 + 6 + 6

10. a) Differentiate between active and passive filters.
- b) Find out the cut-off frequency of the following low-pass second order active filter shown in figure 10.

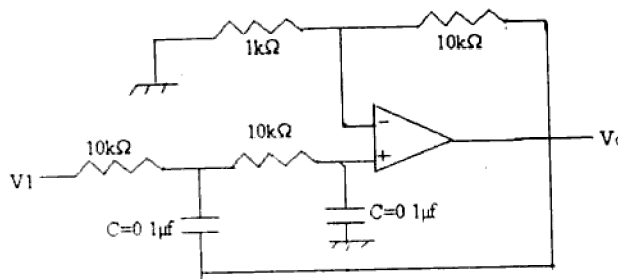


Figure 10

- c) Draw the circuit diagram of a first order high-pass active filter and find out the expression of the cut-off frequency.

5 + 6 + 4



11. a) State superposition theorem. For the network shown in figure 11, calculate current throughout the impedance  $(3 + j4)$  ohm using superposition theorem.
- b) In the given circuit of figure 12, find the reading of the voltmeter V. Interchange the current source and voltmeter and verify the Reciprocity theorem.

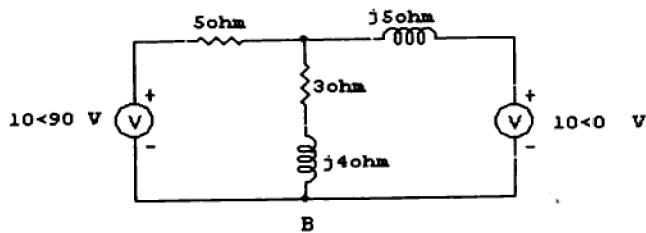


Figure 11

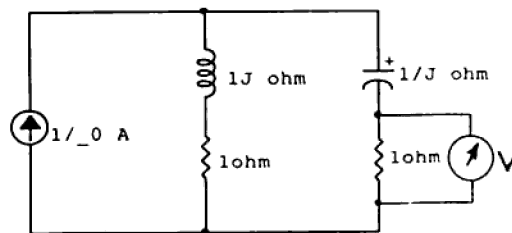


Figure 12

( 2 + 6 ) + 7

---

 END