



Name :

Roll No. :

Invigilator's Signature :

CS/B.TECH (EE) (Separate Supple)/SEM-7/EE-704A/2011

2011

POWER ELECTRONICS

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

GROUP – A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for the following :

10 × 1 = 10

- i) Why do we use chopper ?
 - a) To obtain variable dc voltage from a source of constant dc voltage
 - b) To obtain variable dc voltage from a source of constant ac voltage
 - c) To obtain variable ac voltage from a source of constant dc voltage
 - d) To obtain variable ac voltage from a source of constant ac voltage



- ii) Meaning of RCT.
 - a) Reverse Conducting thyristor
 - b) Random collection of thyristor
 - c) Repeated Conduction thyristor
 - d) Reverse Conducting Transistor
- iii) What is the function of inverter ?
 - a) To get variable ac voltage from dc voltage
 - b) To get ac voltage from dc voltage
 - c) To get variable dc voltage from ac voltage
 - d) To get variable ac voltage from ac voltage
- iv) What do you mean by the element SUS ?
 - a) Silicon Unilateral Switch
 - b) Silicon Unicorn Switch
 - c) Silicon Uni Switch
 - d) Silicon Unifateral Switch.
- v) The no of p-n junctions in a thyristor is
 - a) 1
 - b) . 2
 - c) . 3
 - d) . 4 .



GROUP – B

(Short Answer Type Questions)

Answer any *three* of the following. $3 \times 5 = 15$

2. Explain the two transistor analogy of thyristor.
3. How are the choppers classified ? Give diagrams.
4. Write the advantages and disadvantages of TRIAC.
5. Describe the V-I characteristics of SCR
6. How is dv/dt protection done of SCR ?

GROUP – C

(Long Answer Type Questions)

Answer any *three* of the following. $3 \times 15 = 45$

7. Design the Snubber circuit parameters dv/dt protection of an SCR. Briefly describe the turn-on methods of SCR. What are the problems of parallel connected SCRs & what are the remedies ?
8. Describe the R-C firing circuits with necessary waveforms for turn on of a thyristors. What do you mean by commutation of thyristors ? How many types of commutations are there in use ? Briefly describe the Class-D commutations with necessary waveforms.
9. Write down the differences between SCR, BJT & MOSFET. What is thermal turn on ?
10. How are the inverters classified ? Explain the single phase full-bridge inverter with the operation of Resistive Load along with the circuit analysis.