

2011

## ANALOG ELECTRONIC CIRCUITS

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

### GROUP - A

#### ( Multiple Choice Type Questions )

1. Choose the correct alternatives for any *ten* of the following :

$$10 \times 1 = 10$$

- i) An ideal op-amp has CMRR and slew rate respectively

- a) infinity and infinity      b) zero and infinity  
c) zero and zero      d) infinity and zero.

- ii) An astable multivibrator generates

- a) triangular waveform      b) sinusoidal waveform  
c) square waveform      d) none of these.

- iii) An op-amp is an open loop configuration which can be used as
- a) Comparator
  - b) Log amplifier
  - c) Integrator
  - d) Differentiator.
- iv) Schmitt trigger is a comparator using
- a) negative feedback
  - b) positive feedback
  - c) both positive and negative feedbacks
  - d) none of these.
- v) According to Barkhausen criteria in order to sustain the oscillations
- a) loop gain of the circuit must be negligible
  - b) loop gain of the circuit must be equal to unity
  - c) the phase shift around the circuit must be 180 degree
  - d) none of these.



- x) For a wide range of oscillations in the audio range, the preferred oscillator is
- a) Heartley
  - b) Phase shift
  - c) Wien-bridge
  - d) Hartley and Colpitt.
- xi) Astable multivibrator may be used as
- a) frequency to voltage converter
  - b) voltage to frequency converter
  - c) squaring circuit
  - d) comparator circuit.
- xii) Transformer couple class A power amplifier provides very high frequency because the
- a) collector voltage is stepped up
  - b) dc resistance in the collector circuit is low
  - c) large signal amplifier
  - d) none of these.
- xiii) To avoid false triggering of the NE 555 timer the RESET pin ( Pin 4 ) is generally connected to
- a) Pin 8
  - b) Pin 1
  - c) Pin 3
  - d) No connection ( NC ).

- xiv) Miller capacitance is generated in
- a) CB configuration                      b) CC configuration  
c) CE configuration                      d) All configurations.
- xv) The output gain of an emitter follower circuit is
- a) greater than 1                      b) equal to 1  
c) less than 1                      d) none of these.

**GROUP - B**

**( Short Answer Type Questions )**

Answer any *three* of the following.                       $3 \times 5 = 15$

2. Find out the ripple factor of a full-wave rectifier.
3. Find out the condition of an astable multivibrator so that its duty cycle would be less than 50% and draw the circuit diagram.
4. Explain how the bandwidth of an amplifier will be increased using negative feedback.
5. Draw the high frequency model of a transistor and define all parameters.
6. What is an instrumentation amplifier ? How a basic differential amplifier is modified to a grounded load instrumentation amplifier ?1 + 4
7. Explain the monostable operation of NE 555 with proper circuit diagram and waveform.

**GROUP – C**

**( Long Answer Type Questions )**

Answer any *three* of the following.  $3 \times 15 = 45$

8. a) Why hybrid parameters are so called ?
- b) Draw the equivalent circuit of a transistor using  $h$  parameters. Determine input impedance, current gain and voltage gain and output admittance in terms of  $h$  parameters.
- c) Obtain  $h$ -parameters of CE mode in terms of those of CB mode.  $2 + 8 + 5$
9. a) Explain how it is possible to achieve better Q-point stabilization by using self bias circuit. Assume relevant assumptions.
- b) Consider a self bias circuit with an npn silicon transistor, CE configuration. The circuit is designed in such a way that the  $I_C = 1.5 \text{ mA}$ ,  $V_{CE} = 10 \text{ V}$  and the stability factor is less than equal to 6. If  $V_{CC} = 20\text{V}$ ,  $V_{BE} = 0.7 \text{ V}$ ,  $\beta = 100$ ,  $R_C = 5\text{K}$ , calculate the values of  $R_E$ ,  $R_1$ ,  $R_2$ .
- c) How the operating point of a transistor can shift ? How will you define the stability factors for a transistor ?

10. a) Draw the circuit diagram of a Heartley oscillator and explain its operation.
- b) Draw the ac equivalent circuit of Heartley oscillator and determine the frequency of oscillation.
- c) The frequency of a Heartley oscillator is to vary from 60 kHz to 120 kHz. The tuning capacitor can be changed from 100 pF to 400 pF. The transistor employed in the circuit has  $h_{fe} = 90$  and  $\Delta_{he} = 0.2$ . Find the values of the inductances, neglecting the mutual inductance between them. 5 + 5 + 5
11. a) Draw the circuit diagram of a controlled transistor series regulator. Explain the circuit and the functionality of pass transistor. Write down the expression of output voltage. 2 + 1 + 1
- b) Design a complete + 15 V power supply starting from transformer and using 78XX series IC. 5
- c) Why does Q point of a transistor shift ? What are the different techniques for bias compensation ? Design suitable compensation circuit for variation of  $V_{BE}$  and  $I_{CO}$ . 1 + 1 + 4

CS/B.TECH(EIE-N)/SEM-3/EC(EI)-302/2011-12

12. a) What are the criteria of a good Instrumentation Amplifier ? Draw the circuit diagram of an Instrumentation Amplifier using transducer bridge and explain its operation.
- b) Explain the operation of an inverting Schmitt trigger circuit.
- c) Explain with circuit diagram the operation of voltage to current converter with grounded load. 7 + 4 + 4
13. Write short notes on any *three* of the following : 3 × 5
- a) Comparator
- b) Full-wave precision rectifier
- c) PLL
- d) VCO
- e) Phase shift oscillator.
-