



Time Allotted : 3 Hours

Full Marks : 70

The Figures in the margin Indicate full marks.

Candidate are required to give their answers in their own words as far as practicable

Group-A (Very Short Answer Type Question)

1. Answer any ten of the following :

[1 x 10 = 10]

- (i) What is the conduction angle of a class C power amplifier?
- (ii) What is the value of CMRR of an Ideal OP-Amp?
- (iii) What is the relation between I_{CEO} and I_{CBO} in a BJT?
- (iv) Where the bias point should be located on the dc load line of a series fed class-A power amplifier?
- (v) How many stable state are possible in a monostable multivibrator?
- (vi) According to Barkhausen criteria, what must be the closed loop gain of a feedback circuit in order to create a sustained oscillation?
- (vii) Use of negative feedback reduces the noise level in a amplifier system. True or False?
- (viii) The Q point (I_{CQ} , V_{CEQ}) is at the middle of the ac load line in a class-A transformer coupled power amplifier. Then what is the maximum possible peak to peak variation in the collector-emitter voltage.
- (ix) A full wave bridge rectifier with a 20 V (p-p) sinusoidal input has a load resistance of 1 K Ω . Determine the average dc output voltage. Assume ideal diode.
- (x) What are the operating regions of a BJT characteristics used when the BJT is intended to act as a switch?
- (xi) For a transistor $\alpha = 0.988$, $I_B = 10 \mu A$. Determine I_E .
- (xii) One differential amplifier has a differential gain 20000. Find out the common mode gain if CMRR = 80 dB.

Group-B (Short Answer Type Question)

Answer any three of the following

[5 x 3 = 15]

2. Describe piece wise linear diode model. Show the break down region in the I-V characteristics of an actual diode. [5]
3. Design a differentiator circuit using Op-Amp and other necessary circuit element so that it will have a time constant of 10^{-2} s and an input capacitance of 0.01 μF . Determine the voltage gain magnitude and phase of the designed circuit at 10 rad/s. [5]
4. Draw a high frequency model of a BJT. Define and give an expression of the parameters used in the model. [5]
5. Draw and explain the functioning of a current to voltage converter using OP-Amp. <https://www.makaut.com> [5]
6. Draw a differential amplifier using two npn transistor and a constant current source and other necessary circuit elements. Explain how it rejects the common mode input voltage. [5]


Group-C (Long Answer Type Question)

Answer any three of the following

[15 x 3 = 45]

7. (a) What is the difference between series voltage regulator and shunt voltage regulator? Describe the working principle of a shunt voltage regulator with a neat diagram. [12]
(b) Define the line and load regulation of a voltage regulator. [3]
8. (a) What is the difference between power amplifier and voltage amplifier. [3]
(b) Draw a circuit diagram of transformer coupled class-A power amplifier. Describe its operating principle. [8]
(c) Derive an expression for a power conversion efficiency of a power amplifier. Calculate the possible maximum efficiency of a transformer coupled class-A power amplifier. [4]
9. (a) What are the main factors which affects the stability of a Q point in BJT transistor. Define three stability factor associated with a BJT. [3]
(b) Draw a neat circuit diagram of a collector feedback biasing circuit using an NPN transistor in CE mode without emitter resistance. Find out its Q point (V_{CE} , I_C). [6]
(c) Calculate its stability factor $S(I_{CO})$. [6]

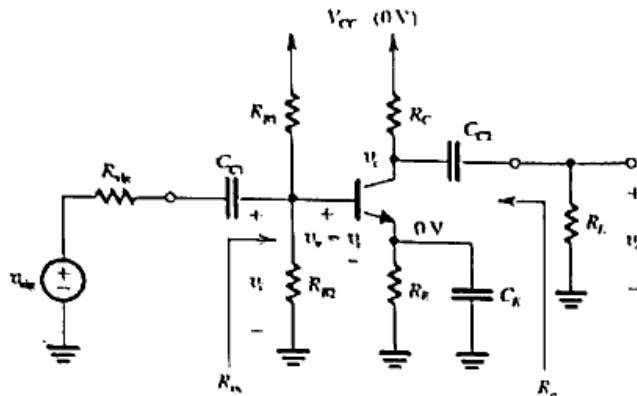10. (a) Draw an instrumentation amplifier using OP-Amp. Explain its functioning. [7]
 (b) Design and analyses an integrator using an OP-Amp. Describe how it behaves as an Integrator circuit. Draw the corresponding output if a triangular waveform is applied. [8]
 11. (a) Determine R_{in} , R_o and A_v of the following circuit by applying hybrid- π model of the transistor. [7]



- (b) A CE amplifier uses a BJT with $\beta = 100$ is biased at a collector current of 1 mA and has a collector resistance $R_C = 5 \text{ k}\Omega$. Find g_m , r_{π} , r_o . Assume $V_A = 100\text{V}$. [4]
 (c) Draw an emitter stabilized bias configuration circuit using pnp transistor in CE mode and other necessary circuit elements. Derive an expression for I_C . [4]

<https://www.makaut.com>

Whatsapp @ 9300930012

Send your old paper & get 10/-

अपने पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से