

Name :

Roll No. :

Invigilator's Signature :

CS/B.Tech (EIE)/SEM-4/EC-401(EI)/2010

2010

ANALOG INTEGRATED CIRCUITS

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

GROUP - A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any ten of the following : $10 \times 1 = 10$

i) An ideal Op-Amp has CMRR and slew rate respectively

- | | |
|--------------------------|-----------------------|
| a) infinity and infinity | b) zero and infinity |
| c) zero and zero | d) infinity and zero. |

ii) Astable multivibrator uses

- | |
|---|
| a) positive trigger |
| b) negative trigger |
| c) both positive & negative triggers simultaneously |
| d) no trigger at all. |

CS/B.Tech (EIE)/SEM-4/EC-401(EI)/2010

- iii) In an Op-Amp integrator circuit
- a) a highly resistive feedback path is used
 - b) a capacitive feedback path is used
 - c) no feedback is at all used
 - d) none of these.
- iv) Integrator is also called
- a) low-pass filter
 - b) high-pass filter
 - c) band-pass filter
 - d) band-gap filter.
- v) The centre frequency of a band-pass filter is always equal to the
- a) bandwidth
 - b) geometric average of the cut-off frequency
 - c) bandwidth divided by 2
 - d) 2 dB frequency.
- vi) In case of monostable operation using 555 timer, the formula for the pulse width is given as
- a) $W = 1.1 RC$
 - b) $W = 0.693 (RC)$
 - c) $W = 1/0.693 (RC)$
 - d) $W = 1.1/RC$
- vii) The Wien-bridge oscillator is useful
- a) at low frequency
 - b) at high frequency
 - c) with LC tank circuit
 - d) at small input signal.
- viii) Schmitt trigger is a comparator using
- a) negative feedback
 - b) positive feedback
 - c) both (a) & (b)
 - d) none of these.

CS/B.Tech (EIE)/SEM-4/EC-401(EI)/2010

- ix) What is standard value of the resistor used in the feedback path of an Op-Amp based buffer circuit ?
- a) $10\text{ k}\Omega$ b) $100\text{ k}\Omega$
c) $1\text{ M}\Omega$ d) none of these.
- x) An Op-Amp cannot be used to implement
- a) monostable multivibrator
b) bistable multivibrator
c) astable multivibrator
d) frequency doubler.
- xi) An instrumentation amplifier is an improvement over
- a) inverting amplifier b) non-inverting amplifier
c) differential amplifier d) voltage follower.
- xii) An 8-bit DAC has a maximum output voltage of 2 V. If $V_{in} = 1.5\text{ V}$, the digital output at the end of conversion will be
- a) 0001 1100 b) 0010 0011
c) 0110 0000 d) 1100 0000
- xiii) Second order active filter with damping coefficient $\alpha = 1.414$ is a
- a) low-pass filter b) high-pass filter
c) Butterworth filter d) Bessel filter.
- xiv) Which one is not an A/D converter circuit ?
- a) Successive approximation type
b) Weighted register type
c) Dual slope type
d) Flash type.


CS/B.Tech (EIE)/SEM-4/EC-401(EI)/2010

- xv) According to Barkhausen criteria in order to sustain the oscillations
- loop gain of the circuit must be negligible
 - loop gain of the circuit must be equal to unity
 - the phase shift around the circuit must be 180 degree
 - none of these.

GROUP - B
(Short Answer Type Questions)

Answer any *three* of the following. $3 \times 5 = 15$

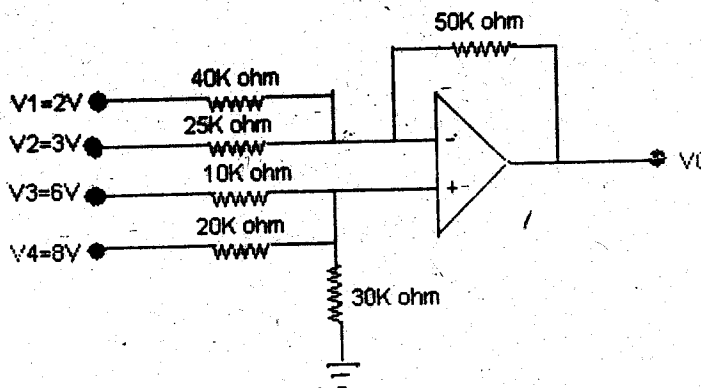- Define the following terms for an Operational Amplifier :
 - Input offset voltage
 - Input offset current
 - Slew rate
 - CMRR
 - Input resistance.
- Find V_o for the following circuit :



CS/B.Tech (EIE)/SEM-4/EC-401(EI)/2010

4. Draw the circuit of a subtractor using two Op-Amps and explain it.
5. Draw and explain a circuit that can be used to detect peak value of the non-sinusoidal waveforms.
6. What is the drawback of log amplifier ? How to overcome the drawbacks ?

GROUP - C**(Long Answer Type Questions)**Answer any three of the following. $3 \times 15 = 45$

7. a) Design a first order high-pass Butterworth filter at a cut-off frequency of 1 kHz with a pass band gain of 2. Derive the necessary working formula.
- b) Derive the slew rate equation for an Op-Amp.
- c) Design a differentiator to differentiate an input signal that varies in frequency from 10 Hz to about 1 kHz.

If a sine wave of 1 V peak a Hz is applied to the differentiator, what will be the output voltage ?

$$(4 + 2) + 3 + (3 + 3)$$

8. a) Draw and explain the working of Triangular wave generator using Op-Amp.
- b) Draw the circuit diagram of Antilog Amplifier and explain its operation.
- c) Explain how the operation of square rooting can be carried out using a multiplier IC. $5 + 5 + 5$

CS/B.Tech (EIE)/SEM-4/EC-401(EI)/2010

9. a) Describe the principle of a R-2R ladder type digital to analog converter.

b) Using LM 317, design an adjustable voltage regulator to satisfy the following specifications :

Output voltage $V_o = 5$ to 12 V

Output current $I_o = 1$ A


c) In the astable multivibrator, $R_A = 2.2$ k Ω , $R_B = 3.9$ k Ω and $C = 0.1$ μ F.

Determine the positive pulse width t_c , negative pulse width t_d , free running frequency f_o and % duty cycle.

7 + 4 + 4

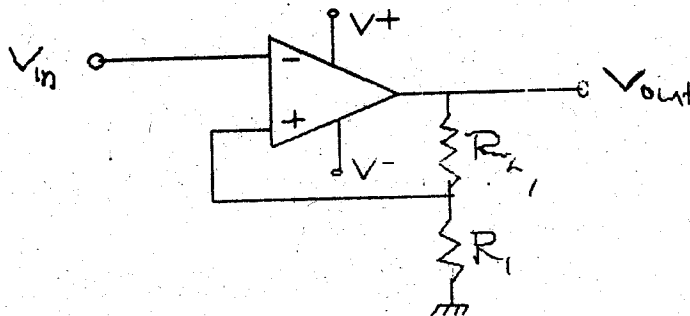10. Explain the operation of an inverting Schmitt trigger circuit. For the inverting Schmitt trigger circuit shown in the figure, calculate R_2 if $R_1 = 100$ k Ω and hysteresis voltage width = 4 V.

Assume saturation voltages to be + 14 V to - 14 V.



CS/B.Tech (EIE)/SEM-4/EC-401(EI)/2010

11. Write short notes on any three of the following : 3 × 5

- a) IC 555
 - b) Instrumentation Amplifier
 - c) Sample and Hold circuit
 - d) Full-wave precision rectifier
 - e) Voltage to current converter.
-