

Name : .....

Roll No. : .....

Invigilator's Signature : .....

**CS/B.Tech (NEW)/SEM-1/ES-101/2011-12**

**2011**

**BASIC ELECTRICAL &  
ELECTRONICS ENGINEERING – I**

Time Allotted : 3 Hours

Full Marks : 70

**THIS QUESTION BOOKLET CONSISTS OF 2 PARTS —  
PART I & PART II.  
TO ANSWER THE QUESTIONS USE SEPARATE ANSWER  
BOOKS FOR SEPARATE PARTS.  
DO NOT ANSWER BOTH THE PARTS IN THE SAME  
ANSWER-BOOK.**

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words  
as far as practicable.*

**PART – I**

**( Marks : 35 )**

**GROUP – A**

**( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any *five* of the following :

5 × 1 = 5

- i) The conductance  $G$  of a series  $R$ - $L$  circuit having a resistance  $R$  and inductive reactance  $X_L$  is given by

a)  $G = \frac{1}{R}$

b)  $G = \frac{R}{X_L}$

c)  $G = \frac{R}{R^2 + X_L^2}$

d)  $G = \frac{R^2}{R^2 + X_L^2}$

1258 (N)

[ Turn over

- GROUP – B**

Answer any *two* of the following.


Answer any *two* of the following.  $2 \times 5 = 10$

- 

2



3. Derive a mathematical expression for r.m.s. value of a sinusoidal voltage  $v = V_m \sin \omega t$ .
4. Two coils have self inductances  $L_1$  and  $L_2$  and mutual inductance between them is  $M$ . Derive a mathematical expression for co-efficient of coupling  $k$  for these coils.
5. Determine the value of  $R$  in Figure 2 such that  $4 \Omega$  resistor consumes maximum power.

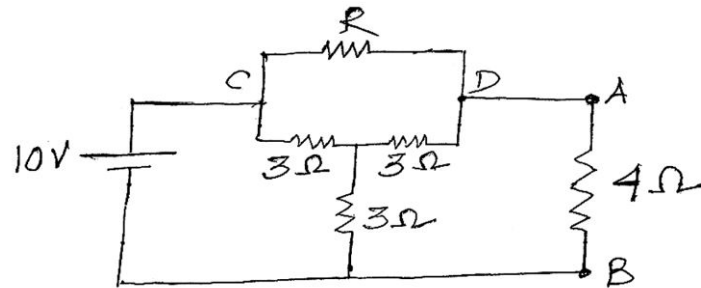


**Figure 2**

**GROUP – C**

**( Long Answer Type Questions )**

Answer any *two* of the following. 2 × 10 = 20

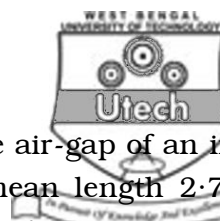
6. a) What is meant by the term “resonance” in a series R.L.C. circuit ? 3
- b) A  $20 \Omega$  resistor, a choke coil having some inductance and some resistance and a capacitor are connected in series across a 25 V variable frequency source. When frequency is 400 Hz, the current is maximum and its value is 0.5 A and the potential difference across the capacitor is 150 V. Calculate the resistance and the inductance of the choke coil and the capacitance of the capacitor. 7



7. a) A flux of  $0.0006 \text{ Wb}$  is required in the air-gap of an iron ring of cross-section  $5.0 \text{ cm}^2$  and mean length  $2.7 \text{ m}$  with an air-gap of  $4.5 \text{ mm}$ . Determine the ampere turns required. Six  $H$  values and corresponding  $B$  values are noted from the magnetisation curve of iron and given below. 6

$H \text{ ( AT/m )}$	200	400	500	600	800	1000
$B \text{ ( Wb/m}^2 \text{ )}$	0.4	0.8	1.0	1.09	1.17	1.19

- b) A circuit receives  $50 \text{ A}$  current at a power factor of  $0.8$  lag from a  $250 \text{ V}$ ,  $50 \text{ Hz}$ ,  $1\text{-ph}$  A.C. supply. Calculate the capacitance of the capacitor which is required to be connected across the circuit to make the power factor unity. 4
8. a) State and explain Thevenins theorem. 3
- b) Find the Thevenin equivalent of the circuit of Figure 3 as shown at terminal XY. 7

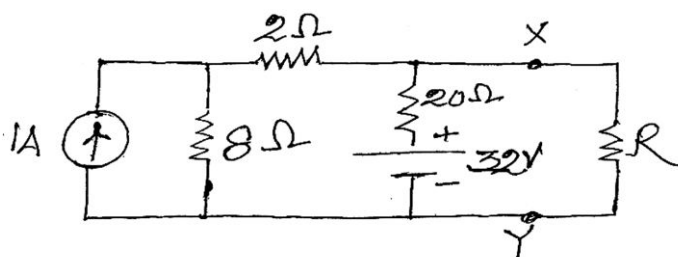

**Figure 3**


9. a) Derive a mathematical expression for the average real power delivered by a single phase a.c. source with an *e.m.f.* of  $e = \sqrt{2} E_m \sin \omega t$  when the source current is  $i = \sqrt{2} I_m \sin (\omega t - \theta)$ . 6
- b) Define power factor of an a.c. circuit. State the major disadvantages of poor power factor. 4

## PART – II

**GROUP – A**

1. Choose the correct alternatives for any *five* of the following :

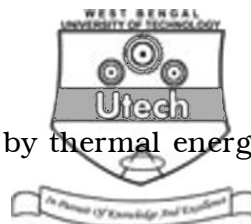- i) Fermi level of an  $n$ -type semiconductor lies
  - a) near the conduction band edge
  - b) near the valence band edge
  - c) at the middle of the band gap
  - d) none of these.
- ii) For an  $n p n$  transistor,  $I_{CBO}$  approximately doubles for temperature rise of every
  - a)  $5^{\circ}\text{C}$
  - b)  $7^{\circ}\text{C}$
  - c)  $10^{\circ}\text{C}$
  - d) none of these.
- iii) If  $\alpha$  of a BJT is 0.98, then the value of  $\beta$  is
  - a) 0.99
  - b) 99
  - c) 50
  - d) 49.
- iv) The power rating of a BJT is determined by which of the following ?
  - a) Collector base junction area
  - b) Base width
  - c) Heat sink
  - d) Emitter base junction area.



- v) It is easy to break the covalent bond by thermal energy in case of
- a) Carbon
  - b) Germanium
  - c) Arsenic
  - d) Silicon.
- vi) The temperature coefficient of Zener breakdown voltage is
- a) positive
  - b) negative
  - c) zero
  - d) either positive or negative.

### GROUP – B

#### ( Short Answer Type Questions )

Answer any *two* of the following.  $2 \times 5 = 10$

2. What do you mean by an intrinsic semiconductor ? Will it behave as an insulator at any temperature ? Explain.  $2 + 3$
3. Explain the mechanism of Zener breakdown in  $p-n$  junction and write how it differs from avalanche breakdown.  $3 + 2$
4. What is meant by  $d.c.$  operating point or  $Q$  point in the context of transistor characteristics ? What is load line ? Why is transistor biasing necessary ?  $2 + 1 + 2$
5. Explain the principle of operation of a varactor diode. Mention one application.  $4 + 1$



**GROUP – C**

**( Long Answer Type Questions )**

Answer any *two* of the following.

2 × 10 = 20

6. Consider an intrinsic silicon bar of cross-section  $5 \text{ cm}^2$  and length  $0.5 \text{ cm}$  at room temperature  $300\text{K}$ . An average field of  $20 \text{ V/cm}$  is applied across the ends of the silicon bar.

a) Calculate —

- i) electron and hole component of current density
- ii) total current in the bar
- iii) resistivity of the bar.

6

- b) If now donor impurity to the extent of 1 part in  $10^8$  atoms of Si is added, find the density of minority carriers and the resistivity.

4

Given :

Electron mobility =  $1400 \text{ cm}^2/\text{V-s}$

Hole mobility =  $450 \text{ cm}^2/\text{V-s}$

Intrinsic carrier concentration of Si

At room temperature (  $300\text{K}$  ) =  $1.5 \times 10^{10} / \text{cm}^3$


No. of Si atoms/  $\text{m}^3$  =  $4.99 \times 10^{28}$ .

7. a) Explain drift and diffusion of charge carrier in semi-conductors. Derive the expression for electric current due to drift and diffusion.

4 + 3

- b) With the help of energy-band diagram, differentiate among conductor, semi-conductor and insulator.

3

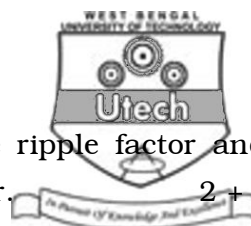


8. a) What is ripple factor ? Evaluate the ripple factor and efficiency of a full-wave bridge rectifier. 2 + 3

- b) A silicon diode with internal resistance  $R_F = 25 \Omega$  is used for half-wave rectification. The input a.c. voltage is  $V_i = 20 \sin \omega t$  and the load resistance is  $500 \Omega$ .

Find,

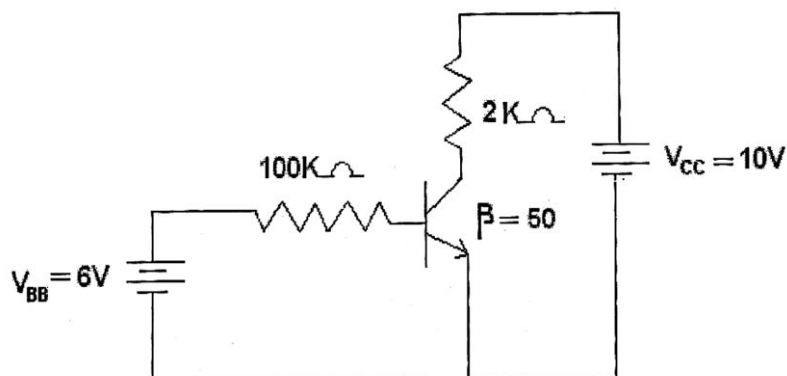- i) d.c. output voltage
  - ii) a.c. input power and
  - iii) efficiency of the rectifier. 2 + 2 + 1
9. a) Draw the circuit diagram for self-biased configuration considering an n-p-n transistor in CE configuration. Derive the expression for its stability factors. 3 + 2
- b) Calculate  $V_{CE}$  and  $I_C$  in the circuit below. Assume  $V_{BE} = 0.7 \text{ V}$ . 4



- c) What is the voltage gain of a transmitter circuit in CC configuration ? 1

=====