

CS/B.TECH/ECE/ODD SEM/SEM-7/EC-705D/2016-17



**MAULANA ABUL KALAM AZAD UNIVERSITY OF  
TECHNOLOGY, WEST BENGAL**

**Paper Code : EC-705D**

**POWER ELECTRONICS**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own  
words as far as practicable.*

**GROUP - A**

**( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any ten of the  
following : 10 × 1 = 10

i) In a thyristor, anode current is made up of

- a) electrons only
- b) holes only
- ☒ c) electrons and holes
- d) none of these.

CS/B.TECH/ECE/ODD SEM/SEM-7/EC-705D/2016-17

ii) When a power BJT is compared to power MOSFET

- a) BJT has lower switching losses but higher conduction losses
- b) BJT has higher switching losses but lower conduction losses
- c) BJT has lower switching losses and conduction losses
- ☒ d) BJT has higher switching losses and conduction losses.

iii) A single phase full converter can operate in

- a) 4 quadrants
- b) 3 quadrants
- ☒ c) 2 quadrants
- d) 1 quadrant.

iv) For an SCR,  $di/dt$  protection is achieved through the use of

- a) R in series with SCR
- ☒ b) RL in series with SCR
- c) L in series with SCR
- d) L across SCR.

CS/B.TECH/ECE/ODD SEM/SEM-7/EC-705D/2016-17

- v) Chopper control of DC motor provides variations in
- a) frequency
  - b) current
  - c) input voltage
  - d) ☒ all of these.
- vi) Reverse recovery current in a diode depends upon
- a) forward field current
  - b) ☒ storage current
  - c) temperature
  - d) PIV.
- vii) An IGBT has three terminals called
- a) collection, emitter and base
  - b) brain, source and base
  - c) drain, source and gate
  - d) ☒ collector, emitter and gate.
- viii) The most efficient gate-triggering signal for SCR is
- a) a steady DC level
  - b) a short duration pulse
  - c) ☒ a high-frequency pulse train
  - d) a low-frequency pulse train.

CS/B.TECH/ECE/ODD SEM/SEM-7/EC-705D/2016-17

- ix) The main reason for connecting a pulse transformer at the output stage of an SCR firing circuit is to
- a) amplify power of the triggering pulse
  - b) ☒ provide electric isolation
  - c) reduce the turn on time of SCR
  - d) avoid spurious triggering of SCR due to noise.
- x) Switched mode power supply ( SMPS ) is preferred over continuous types because SMPS
- a) is suitable for both CAN and DC
  - b) is suitable for low power circuits
  - c) is suitable for high power circuits
  - d) ☒ provides low power loss.

xi) In voltage source inverters

- a) load voltage waveform  $v_o$  depends on load impedance  $Z$ , whereas load current waveform  $i_o$  does not depend on  $Z$
- b) load voltage waveform  $v_o$  and load current waveform  $i_o$  depend on  $Z$
- c) load voltage waveform  $v_o$  does not depend on load impedance  $Z$ , whereas load current waveform  $i_o$  depend on  $Z$
- d) both  $v_o$  and  $i_o$  do not depend on  $Z$ .

xii) In a single phase full bridge VSI has inductor  $L$  as load. For a constant source voltage, the current through the inductor is

- a) square wave
- b) triangular wave
- c) sine wave
- d) pulse wave.

#### GROUP - B

##### ( Short Answer Type Questions )

Answer any *three* of the following.  $3 \times 5 = 15$

2. Draw and explain a boost DC-DC converter. Write the expression for output voltage. *step-up chopper*  $3 + 2$

3. A thyristor is used to feed a load resistance 8 ohms from a 230 V single phase supply. The ratings of thyristor are :

Repetitive peak current = 300A,  $(di/dt)_{max} = 40 \text{ A}/\mu\text{sec}$  and  $(dv/dt)_{max} = 150 \text{ V}/\mu\text{sec}$ . Design a snubber circuit for protection of thyristor.

4. What is commutation ? Explain current commutation and voltage commutation.  $2 + 3$

5. "SCR is self latching device." Explain the statement with the help of two transistor analogy of SCR.

6. Write a short note on TRIAC. ✓

#### GROUP - C

##### ( Long Answer Type Questions )

Answer any *three* of the following.  $3 \times 15 = 45$

7. a) Describe the construction of IGBT.  
 b) Explain its operation with the help of an equivalent circuit. State the advantages of IGBT.  
 c) How  $di/dt$  and  $dv/dt$  protections are achieved in SCR ?  
 d) Draw and explain non-isolated base drive circuit for BJT.  $2 + 4 + 6 + 3$

8. a) ✓ Why is a three phase bridge controlled rectifier called a six pulse converter ? Explain briefly with circuit diagram and output voltage waveform.
- b) A three phase six pulse converter is operated from a 3 phase star connected 400 V, 50 Hz supply and with  $RL$  load (  $R = 10 \text{ ohm}$  ). It is required to obtain an average output voltage equal to 50% of the maximum possible output voltage of the rectifier. Find out at this condition
- the firing angle
  - the average output voltage
  - the average current of each thyristor
  - PIV requirement of each thyristor.
- c) Explain how the above mentioned converter can act as rectifier and inverter. 6 + 6 + 3

9. ✓ a) Describe with the help of necessary voltage waveforms and circuit diagram, the operation of a three phase voltage source inverter with  $180^\circ$  conduction mode delivering power to star connected pure resistive load.
- b) ✓ A single phase half-wave inverter feeds a resistive load  $RL = 10 \Omega$ . Source voltage is 240V DC. Determine the r.m.s. voltage, output power and r.m.s. value of current. 10 + 5
10. a) Discuss any scheme of microprocessor based triggering angle control.
- b) Write a note on resonant converter. 7 + 8
- ✓ 11. Write short notes on any *three* of the following : 3 × 5
- ✓ Electronic ballast
  - Induction heating
  - ✓ UPS
  - Active front end converter
  - ✓ Need for power electronics converter.