



**MAULANA ABUL KALAM AZAD UNIVERSITY OF  
TECHNOLOGY, WEST BENGAL**

**Paper Code : ES-EE-101  
BASIC ELECTRICAL ENGINEERING**

**Time Allotted: 3 Hours**

**Full Marks: 70**

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words  
as far as practicable.*

*The questions are of equal value.*

**Group – A**

**(Multiple Choice Type Questions)**

1. Choose the correct alternative for *any ten* of the following questions: 1×10=10
- (i) If there are two bulbs connected in series and one blows out the following may happen:
- (a) The other bulb continues to glow with the same brightness
  - (b) The other bulb stops glowing
  - (c) The other bulb glows with increased brightness
  - (d) The other bulb also burns out
- (ii) If the applied voltage across a lamp is reduced by 50%, then the power consumption will reduce to
- |         |         |
|---------|---------|
| (a) 50% | (b) 75% |
| (c) 25% | (d) 40% |
- (iii) The form factor of a current waveform is 1. The shape of the waveform is
- |                |                |
|----------------|----------------|
| (a) sinusoidal | (b) triangular |
| (c) square     | (d) saw tooth  |

(iv) The DC motor needs a starter during starting to control

- (a) speed
- (b) voltage
- (c) current
- (d) flux

(v) DC voltage of 100V is applied to a circuit consisting of a resistance of  $10\Omega$  and inductance of 5 Henry connected in series. The time constant of the circuit is

- (a) 2S
- (b) 1S
- (c) 0.5S
- (d) 0.25S

(vi) The superposition theorem satisfies the principle of

- (a) Reciprocity
- (b) Duality
- (c) Linearity
- (d) Non-linearity

(vii) The ratio of output voltage to input voltage of a boost converter operating at a duty cycle 'D' is given by

- (a) D
- (b)  $1 - D$
- (c)  $\frac{1}{1-D}$
- (d)  $\frac{1}{D}$

(viii) Two alternating currents are represented by  $i_1 = \sin(\omega t - 30^\circ)$  and  $i_2 = \sin(\omega t + 30^\circ)$ .

- (a)  $i_1$  leads  $i_2$  by  $60^\circ$
- (b)  $i_1$  lags  $i_2$  by  $60^\circ$
- (c)  $i_2$  leads  $i_1$  by  $30^\circ$
- (d)  $i_2$  lags  $i_1$  by  $30^\circ$

(ix) The positive plates of nickel iron cell is made up of

- (a) Nickel hydroxide
- (b) Lead peroxide
- (c) Ferrous hydroxide
- (d) Potassium hydroxide

(x) The maximum efficiency of the transformer occurs at when

- |                                   |                                     |
|-----------------------------------|-------------------------------------|
| (a) Iron loss = Copper loss       | (b) Eddy current loss = Copper loss |
| (c) Hysteresis loss = Copper loss | (d) Iron loss > Copper loss         |

(xi) The frequency of emf induced in the rotor of a 3 phase, 50 Hz induction motor at standstill is

- |           |            |
|-----------|------------|
| (a) 0 Hz  | (b) 50 Hz  |
| (c) 25 Hz | (d) 100 Hz |

(xii) The field of a synchronous generator is excited by

- |                               |                                |
|-------------------------------|--------------------------------|
| (a) AC supply                 | (b) DC supply                  |
| (c) Either by AC or DC supply | (d) Composite AC and DC supply |

**Group – B**

**(Short Answer Type Questions)**

**Answer any three of the following.**


**5×3=15**

2. Explain the principle of working of a single phase induction motor.
3. A coil having a resistance of  $5\ \Omega$  and inductance of  $0.1\ \text{H}$  is connected in series with a  $50\ \mu\text{F}$  capacitor. A sinusoidal voltage of  $200\text{V}$  is applied to the circuit. At what frequency the current in the circuit will be maximum? Calculate this current & voltage across the capacitor at this frequency.
4. A series circuit consisting of a non-inductive resistor of  $R\ \Omega$  & a pure inductance of  $L\ \text{Henry}$  connected across a DC voltage source of  $V$  volts through a switch  $S$ . Derive the equation of the current in the circuit at any instant ' $t$ ' after closing the switch.

5. Find the average and rms voltage of the voltage waveform shown. What is the power dissipation across a  $9\ \Omega$  resistor. Supplied with voltage.



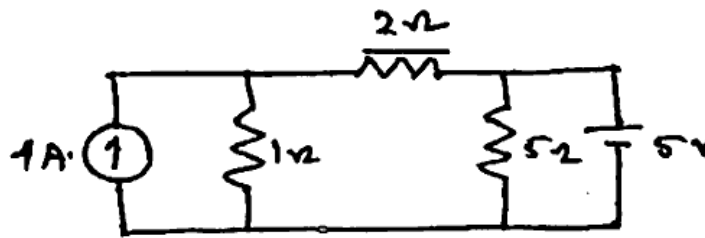6. Using superposition theorem find the current through the resistor  $5\ \Omega$  in the Circuit shown.  
<http://www.makaut.com>



**Group - C**

(Long Answer Type Questions)

Answer any three of the following.

15×3=45

7. (a) A 15 KVA, 1100/110V, 50 Hz single phase transformer has the following test results:

Open circuit test LV side: 110 V, 0.8 A, 90 W

Short circuit test HV side: 70 V, 12 A, 100 W

Determine the following

- (i) core loss of the transformer.

1


4

=


- (ii) equivalent resistance & leakage reactance referred to the HV side.
  - (iii) equivalent resistance and the leakage reactance referred to the LV side.
  - (iv) regulation of transformer at full load and half load of 0.8 pf lagging.
  - (v) efficiency of the transformer at full load and half load at 0.8 pf lagging.
- (b) Draw the connection and phasor diagram at the following two types of three phase transformers.  
Yy6 & Yd1 10+5=15

8. (a) Explain the meaning of phase and phase difference of sinusoidal quantities.
- (b) A coil of resistance of  $30\Omega$  and inductance  $320\text{ mH}$  is connected in parallel to a circuit consisting of a  $75\Omega$  resistor in series with  $150\mu\text{F}$  capacitor. The circuit is connected to a  $200\text{ V}$ ,  $50\text{ Hz}$  supply. Determine the supply current and circuit power factor.
- (c) At  $t = 0$ , the instantaneous value of  $50\text{ Hz}$  sinusoidal current is  $5\text{ A}$  and increase in magnitude further. Its rms value is  $10\text{ A}$ .
- (i) Write the expression of its instantaneous value.
  - (ii) Find the current at  $F = 0.01\text{ s}$  and  $t = 0.015\text{ s}$
  - (iii) Sketch the waveforms indicating these values.
- 2+8+5=15

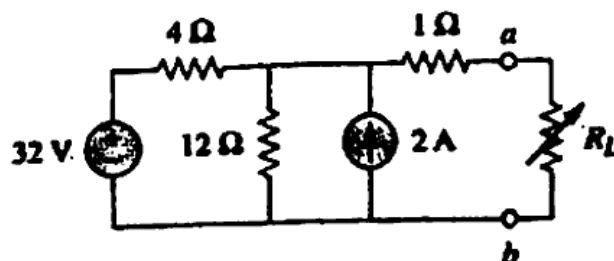9. (a) Find the Thevenin equivalent of the circuit across a – b, shown in the figure below:



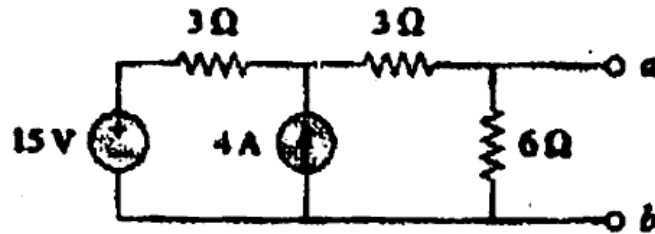(b) Determine the Norton equivalent of the circuit shown below:



(c) A balanced mesh connected load of  $(6 + j8)\Omega$  is connected across a 3 phase, 50 Hz, 230 V supply system. Calculate: 5+5+5=15

- (i) line current
- (ii) power factor
- (iii) active power

10. (a) A 3 phase 50 Hz induction motor has a full load speed of 1440 rpm. Calculate:

- (i) Slip
- (ii) No. of poles
- (iii) frequency of induced emf of rotor
- (iv) speed of rotor field with respect to rotor structure
- (v) speed of rotor field with respect to stator field

(b) Explain with relevant diagram the method of speed control of a separately excited DC motor. 8+7=15

11. Write notes on *any three* of the following:

3×5=15

- (a) Three phase voltage source inverter
  - (b) Method of power factor improvement
  - (c) Buck converter
  - (d) Auto transformer
- 

<http://www.makaut.com>

Whatsapp @ 9300930012

Your old paper & get 10/-

पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से