



**ENGINEERING & MANAGEMENT EXAMINATIONS, DECEMBER - 2007**  
**CIRCUIT THEORY & NETWORKS**  
**SEMESTER - 3**

Time : 3 Hours ]

(EIE)

[ Full Marks : 70

**GROUP - A**

**( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any *ten* of the following : 10 × 1 = 10

i) A four terminal network constitute a

- |                      |                     |
|----------------------|---------------------|
| a) one port network  | b) two port network |
| c) four port network | d) none of these.   |

ii) A capacitor C at time  $t = 0 +$  with zero initial charge acts as a


- |                   |                    |
|-------------------|--------------------|
| a) short circuit  | b) open circuit    |
| c) current source | d) voltage source. |

iii) Kirchhoff's law fail in case of

- |                                    |
|------------------------------------|
| a) Linear networks                 |
| b) Non-linear networks             |
| c) Dual networks                   |
| d) Distributed parameter networks. |

iv) The voltages  $v_1$  &  $v_2$  in the given circuit are


- |            |                   |
|------------|-------------------|
| a) 6v, 4v  | b) 4v, 6v         |
| c) 5v each | d) none of these. |

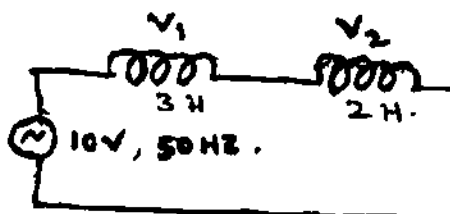




a)  $0^\circ$   
c)  $90^\circ$

a)  $2\Omega$   
c)  $1\Omega$

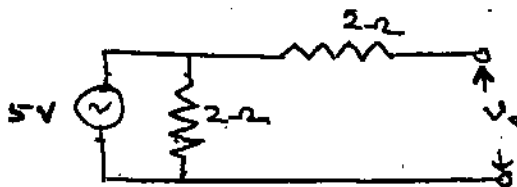


**Answer any three of the following.**

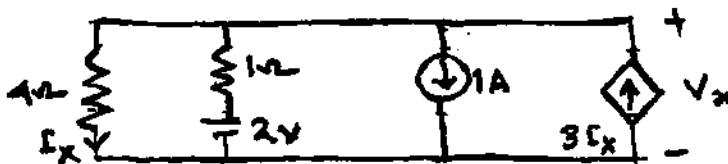2. Determine the value of  $I_x$  &  $V_x$ .




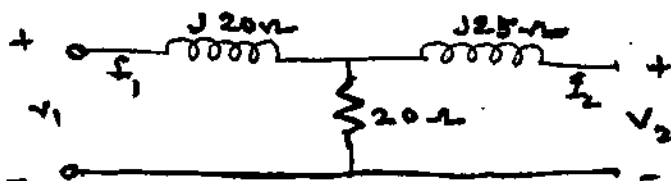4. Determine the Z-parameter of the network shown in the fig. Is it a reciprocal network?






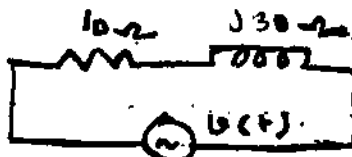5. In the circuit shown below, a voltage  $v(t) = 50 \sin(\omega t + 30^\circ)$  is applied. Determine the true power, reactive power & power factor.



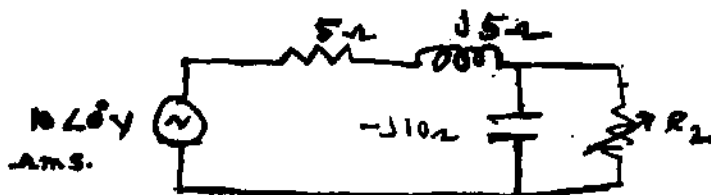6. In the network shown below, find  $R_L$  which will dissipate maximum power. Determine also maximum power.




### GROUP - C

#### ( Long Answer Type Questions )

Answer any three questions.

3 × 15 = 45

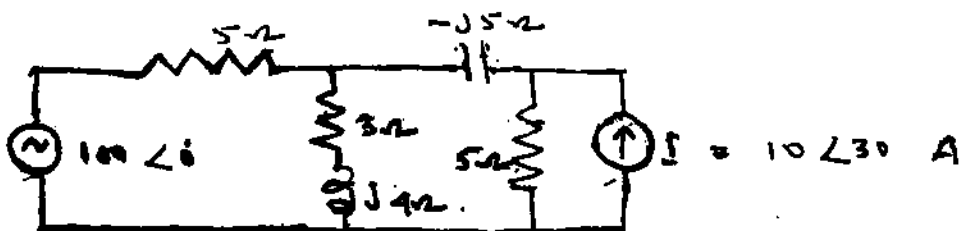7. a) State & explain superposition theorem.  
b) Find using superposition theorem, the current through the capacitor having reactions  $-j5 \Omega$ .




5 + 10

8. a) Describe the method of measuring reactive power.  
b) A three phase delta connected RYB system with effective voltage of 400 V, has a balanced load with impedance  $3 + j4 \Omega$ . Calculate  
i) phase current  
ii) line current  
iii) power in each phase.




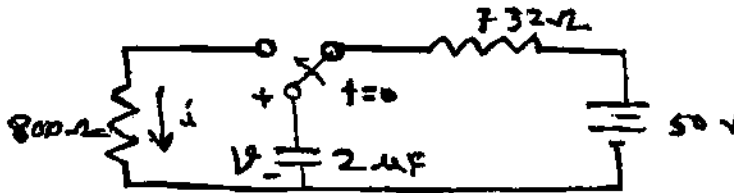- c) Determine  $V(0^+)$ ,  $i(0^+)$ ,  $i(2 \text{ ms})$  for the following circuit :




5 + 5 + 5

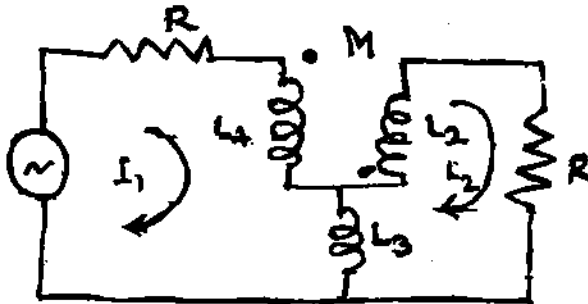9. a) Determine for a two-port network the condition of reciprocity & condition of symmetry in terms of  $h$ -parameters.
- b) Draw the voltage phases & current phases of a series R-L circuit. Draw also the impedance triangle.
- c) Find the ratio of  $I_1$  &  $I_2$  for the following circuit :



5 + 5 + 5

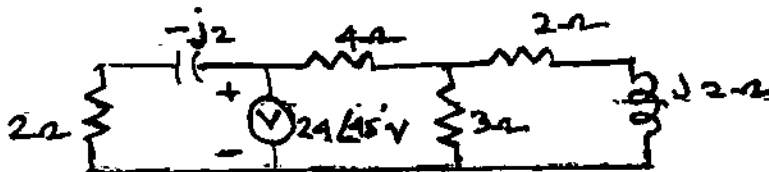10. a) Determine current in  $3\Omega$  resistor in the following figure :




- b) Find two elements of a series circuit having current  $i = 4.24 \cos(5000t + 45^\circ) \text{ A}$ , power 180 W & power factor 0.8 lagging.
- c) An RLC series circuit has  $R = 100\Omega$ ,  $L = 500 \text{ mH}$  &  $C = 40 \mu\text{F}$ . Calculate resonant, lower & upper half power frequency.

8 + 4 + 3



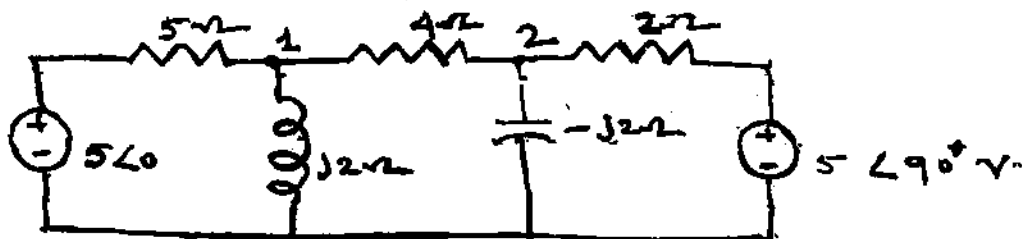11. a) For the network shown, determine the node voltages.



- b) Determine the step response of series R-L-C circuit. Draw the wave forms of the response.
- c) Determine  $Q$  factor of a series R-L-C circuit. 5 + 7 + 3

END